

--	--	--	--	--	--	--	--	--	--

**GANDHI INSTITUTE OF ENGINEERING AND TECHNOLOGY UNIVERSITY, ODISHA, GUNUPUR  
(GIET UNIVERSITY)**



Ph.D. (First Semester) Examinations, December – 2024  
**23SPPEEC1012 – Analog and Digital CMOS VLSI Design**  
(ECE)

Time: 3 hrs

Maximum: 70 Marks

**The figures in the right hand margin indicate marks.**

**Answer ANY FIVE Questions.**

**(14 x 5 = 70 Marks)    Marks**

- |      |   |    |
|------|---|----|
| 1.a. | Explain the basic structure of a Metal-Oxide-Semiconductor (MOS) transistor and its characteristics with applied bias of ( $V_g > 0$ , $V_g < 0$ ).                 | 8  |
| b.   | What are the key quality metrics in digital design, and how does each metric impact the overall performance of a circuit?   | 6  |
| 2.   | Discuss the static and dynamic characteristics of CMOS inverter, and how to evaluate its switching threshold, noise margin and power consumption?                   | 14 |
| 3.a. | Define a stick diagram, and draw the stick diagram for an CMOS inverter and discuss its importance in the layout design process.                                    | 7  |
| b.   | Explain the process of clock tree synthesis (CTS) and its importance in digital design.   | 7  |
| 4.   | Compare and contrast static CMOS design, ratioed logic, and pass transistor logic.  | 14 |
| 5.   | Explain the bi-stability principle in static latches and registers. Describe dynamic latches and registers, including their advantages and disadvantages            | 14 |
| 6.a. | What is pipelining, and how does it enhance the performance of sequential circuits?   | 7  |
| b.   | Discuss the challenges posed by short channel effects in advanced MOS technologies.   | 7  |
| 7.   | Explain the concept of logic effort in the context of static CMOS and dynamic logic design. How does it influence the speed and power dissipation of dynamic gates? | 14 |
| 8.   | Discuss the frequency response of different amplifier stages (CS stage, source follower, common gate stage) and their implications for circuit design.              | 14 |

---End of Paper---