

GANDHI INSTITUTE OF ENGINEERING AND TECHNOLOGY, ODISHA, GUNUPUR (GIET UNIVERSITY)



B. Tech (Third Semester - Regular) Examinations, November – 2024

23BEC23001 - ANALOG ELECTRONICS CIRCUITS

(Electronics and Communication Engineering)

Time: 3 hrs

Maximum: 60 Marks

Answer ALL questions

(The figures in the right-hand margin indicate marks)

PART – A

(2 x 5 = 10 Marks)

Q.1. Answer **ALL** questions

- a. What are the ideal characteristics of operational amplifier?
- b. Draw the terminal characteristics of a Zener diode.
- c. For the transistor circuit shown in Fig.A. find the value of V_C if $V_{BE}=0.7V$ and $\beta=100$.

CO # Blooms
 Level

CO5 K1

CO1 K1

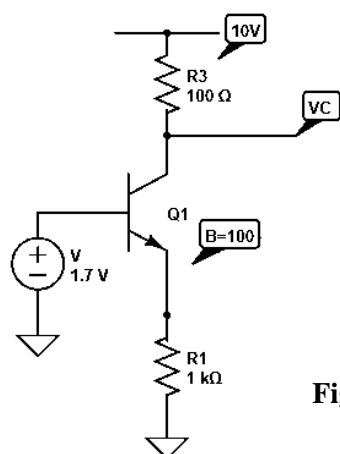


Fig. A

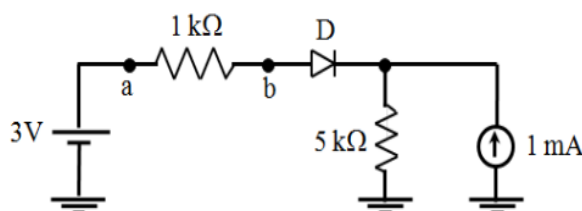


Fig. B

CO2 K2

- d. Describe about the saturation and ohmic region of operation of a JFET.
- e. For the ideal diode circuit as shown in Fig B. find the value of V_{ab} .

CO3 K1

CO1 K2

PART – B

(10 x 5 = 50 Marks)

Answer **ALL** the questions

2. a. Describe about the working of a bridge type full wave rectifier with proper diagram.
 - b. How a two-level clipper circuit works explain with proper diagram.
- (OR)
- c. Design an integrator circuit using operational amplifier and find the expression of its output.
 - d. Design a differentiator circuit using operational amplifier and find the expression of its output.
- 3.a. Draw the circuit diagram of a common collector amplifier.
 - b. For the transistor circuit shown in figure find the gain if $V_T=26$ mV, $V_{BE}=0.7$ V and $\beta=100$.

Marks CO # Blooms
 Level

5 CO1 K2


5 CO1 K2

5 CO5 K2

5 CO5 K2


3 CO3 K1

7 CO3 K3

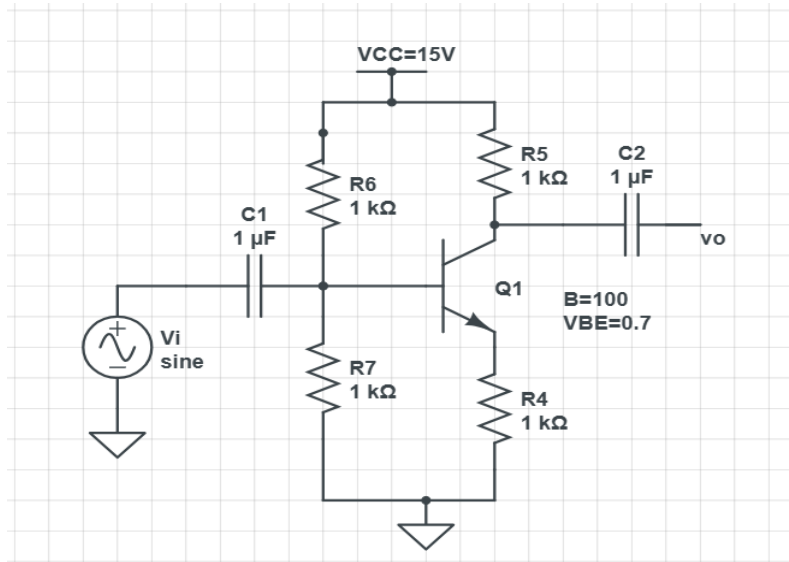


(OR)

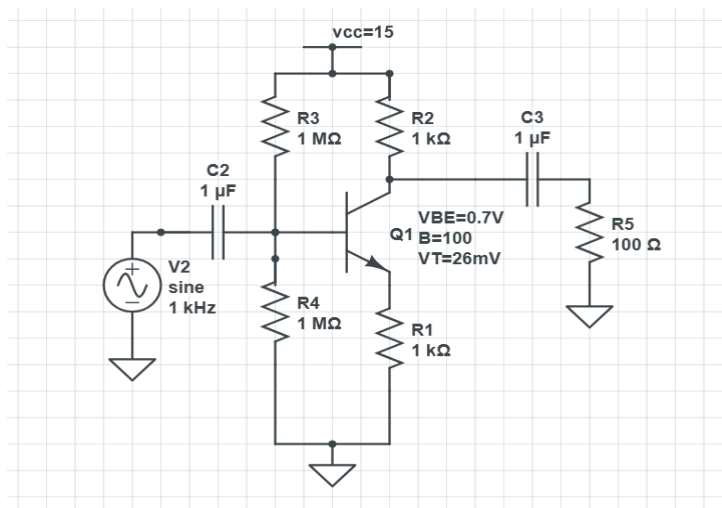- c. Find the expression for transconductance (g_m) of an n channel MOSFET. 3 CO4 K1
- d. For BJT circuit shown in figure draw the box model, where $V_T = 26\text{mV}$, $V_{BE} = 0.7\text{V}$ and $\beta = 100$. 7 CO3 K3



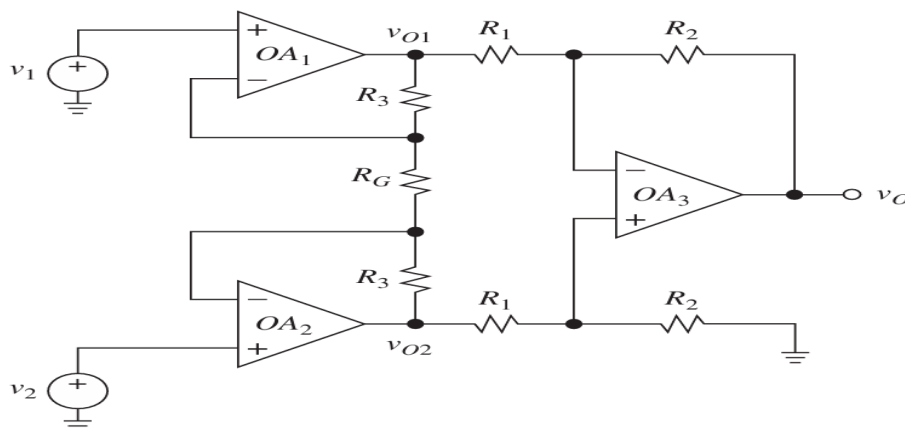
- 4.a. Find the expression of output v_o for the instrumentation amplifier circuit shown in figure. 5 CO5 K3



- b. Draw the circuit of an active low pass filter and find the expression of its cutoff frequency. 5 CO5 K2

(OR)


- | | | | |
|---|---|-----|----|
| c. How an inverting Schmitt trigger works explain with proper diagram? | 5 | CO5 | K2 |
| d. Find the value of output voltage generated by the differential amplifier as shown in figure. | 5 | CO5 | K3 |

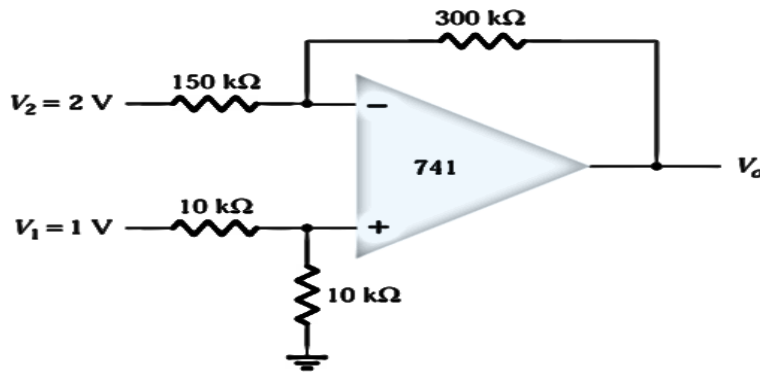

- | | | | |
|--|----|-----|----|
| 5.a. Explain about the working of an n channel JFET with proper diagram. | 10 | CO4 | K3 |
|--|----|-----|----|


(OR)

- | | | | |
|---|----|-----|----|
| b. Explain about the working of p channel MOSFET with proper diagram. | 10 | CO4 | K3 |
| 6.a. What are the different regions of operation of BJT? and also Explain about switching characteristics of BJT. | 5 | CO1 | K2 |
| b. For the diode circuit shown in figure draw waveform for $V_d(t)$, assume that capacitor is initially uncharged. | 5 | CO1 | K3 |

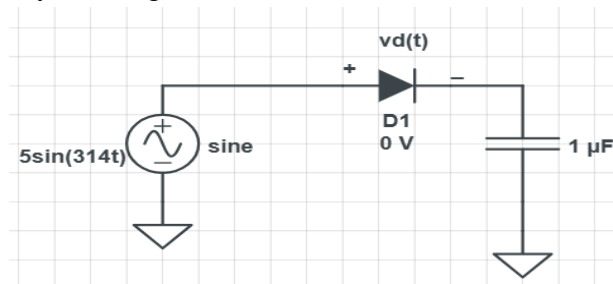

(OR)

- | | | | |
|---|---|-----|----|
| c. Explain about the conditions of oscillation in positive feedback system. | 3 | CO5 | K1 |
| d. For the JFET circuit shown in figure find the value of V_{GS} and V_{DS} . | 7 | CO5 | K3 |

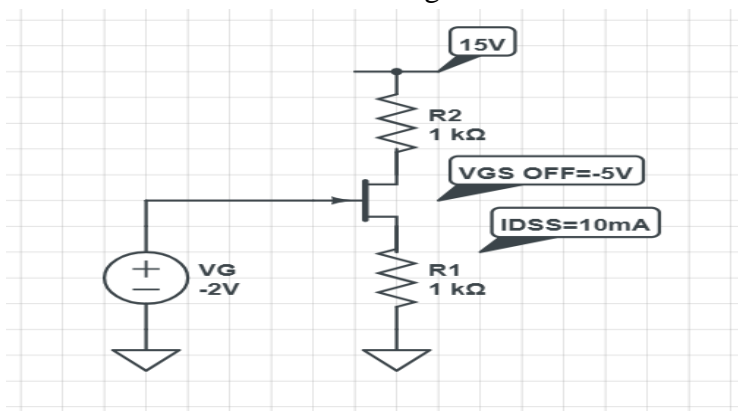

--- End of Paper ---