

# GANDHI INSTITUTE OF ENGINEERING AND TECHNOLOGY, ODISHA, GUNUPUR (GIET UNIVERSITY)



B. Tech (Third Semester - Regular) Examinations, November – 2024

## 23BEEPC23002 - NETWORK THEORY

(EE/EEE)

Time: 3 hrs

Maximum: 60 Marks

(The figures in the right hand margin indicate marks)

### PART – A

(2 x 5 = 10 Marks)




Q.1. Answer **ALL** questions


	CO	Blooms Level
a. State Kirchhoff's current and voltage Law ?	CO1	K1
b. State the superposition Theorem?	CO1	K1
c. Explain the reciprocity condition for a two-port network?	CO1	K2
d. What is the purpose of a filter in a network?	CO2	K2
e. What is the Laplace Transform of $\sin bt$ and $\cos bt$ ?	CO1	K1

### PART – B

(10 x 5 = 50 Marks)

Answer <b>ALL</b> the questions		Marks	CO #	Blooms Level
2. a.	<p>By using Thevenin's Theorem calculate the current flowing through between terminal A &amp; B?</p>	5	CO1	K2
b.	Different between Thevenin's Theorem and Norton's Theorem?	5	CO1	K2
(OR)				
c.	<p>By using superposition Theorem Calculate the voltage 'V' in the given circuit?</p>	5	CO1	K2
d.	<p>Find the value of load resistance for which the maximum power will be transfer to the circuit?</p>	5	CO1	K2

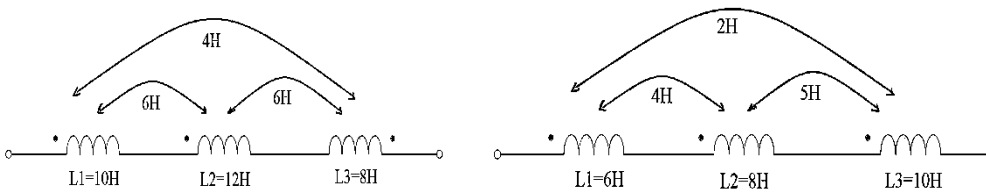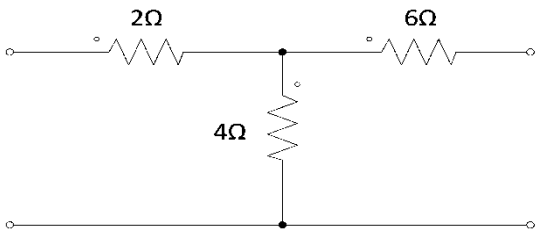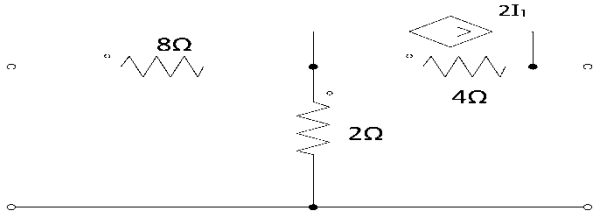3.a.	<p>A series RLC Circuit has the following parameters values. Resistance- 10 ohm , Inductance- 0.014 H, Capacitance – 100 <math>\mu</math>F</p> <p>Compute the following</p> <ol style="list-style-type: none"> <li>1. Resonant Frequency in rad/sec.</li> <li>2. Quality Factor of the circuit.</li> <li>3. Band width.</li> <li>4. Lower and upper frequency point of the bandwidth.</li> </ol>	5	CO4	K2
b.	What is the Resonance Frequency and derive the condition for resonance Frequency?	5	CO3	K3
(OR)				
c.	Explain Bandwidth of Series R-L-C circuit and Quality Factor?	5	CO4	K1
d.	Determine the resonant Frequency, Bandwidth and Quality Factor of the series RLC circuit with $R=10\Omega$ , $L=0.1H$ , $C=10\mu F$ .	5	CO4	K2
4.a.	<p>i) How does the co-efficient of coupling affected the mutual inductance of two coils?</p> <p>ii) If two coils have self-inductance of <math>L_1=4H</math> and <math>L_2=9H</math>, and their mutual inductance =6H calculate the co-efficient of coupling?</p>	5	CO3	K2
b.	Find the total inductance from the given two circuits.	5	CO3	K2
				
(OR)				
c.	State the Laplace transform of an exponential function?	5	CO3	K3
d.	How does inductive reactance change with frequency in a resonance circuit?	5	CO2	K2
5.a.	Find the Z-Parameter of the below given 2-port network?	5	CO2	K2
				
b.	Find the Y parameter of the given 2-port network?	5	CO2	K2
				
(OR)				
c.	A function in Laplace domain is given by $F(s) = \left[ \frac{2}{s} - \frac{1}{s+3} \right]$ obtain its initial value and final value Theorem?	5	CO3	K2
d.	Explain the types of Filter.	5	CO5	K1
6.a.	State and explain the maximum power transfer theorem.	5	CO1	K2

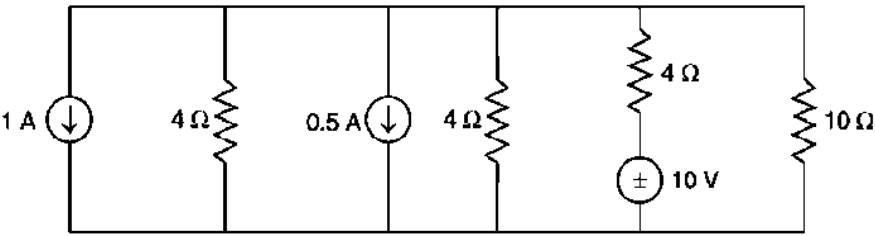b.	Calculate the current through $10\Omega$ and voltage drop across it for the circuit shown in fig by using Milliman's Theorem.	5	CO1	K4
				
(OR)				
c.	Derive the Transient Response of series RL-circuit with D.C excitation.	5	CO3	K2
d.	Derive the condition for maximum resonant frequency.	5	CO3	K2

--- End of Paper ---