

GANDHI INSTITUTE OF ENGINEERING AND TECHNOLOGY, ODISHA, GUNUPUR (GIET UNIVERSITY)



B. Tech (Third Semester - Regular) Examinations, November – 2024

23BEEPC23002 – Network Theory

(ECE)

Time: 3 hrs

Maximum: 60 Marks

Answer ALL questions


(The figures in the right hand margin indicate marks)

PART – A

(2 x 5 = 10 Marks)

Q.1. Answer **ALL** questions

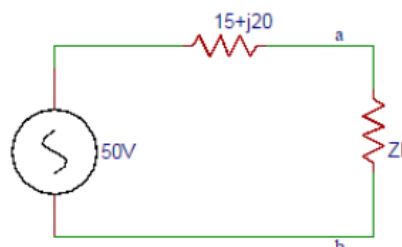- a. Define the following terms tree and co-tree.
- b. A two-port device is defined by the following pair of equations $I_1 = 5V_1 + 2V_2$, $I_2 = 3V_1 + 4V_2$. Write its impedance parameters Z_{11} , Z_{12} , Z_{21} , and Z_{22} .
- c. In the circuit shown below, find the value of load impedance for which source delivers maximum power.



- d. If the value of resonant frequency is 50 kHz in a series RLC circuit with a bandwidth of about 1 kHz, then what would be the value of the quality factor?
- e. Define the coefficient of coupling.


CO #	Blooms Level
CO1	K1
CO4	K3
CO1	K3
CO2	K3
CO5	K1

PART – B


(10 x 5 = 50 Marks)

Answer **ALL** the questions

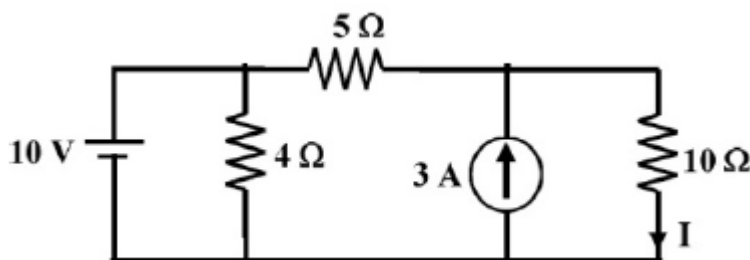2. a. Find the current I using superposition theorem



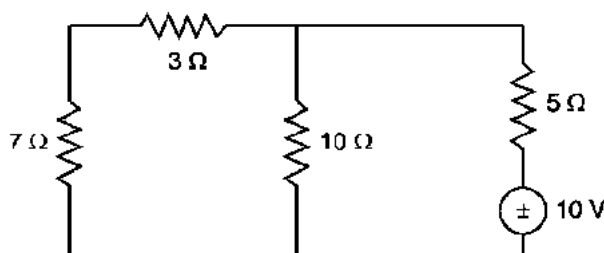- b. Determine current through 7Ω resistor for the circuit shown in fig. Verify Reciprocity theorem.




(OR)

- c. State and explain the maximum power transfer theorem.
- d. Calculate the current through 10Ω and voltage drop across it for the circuit

5	CO1	K2
5	CO1	K4

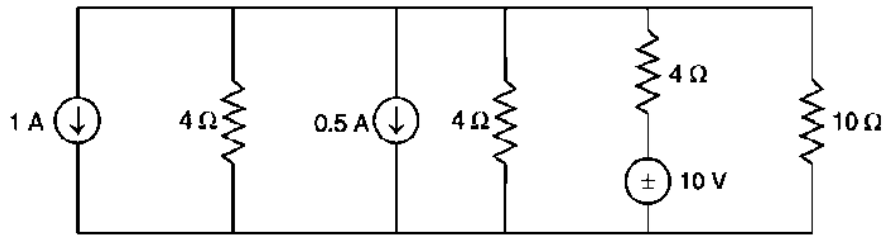shown in fig by using Milliman's Theorem.



- 3.a. An AC circuit is composed of a serial connection of: a resistor with resistance $50\ \Omega$, a coil with inductance $0.3\ \text{H}$, and a capacitor with capacitance $15\ \mu\text{F}$. The circuit is connected to an AC voltage source with amplitude $25\ \text{V}$ and frequency $50\ \text{Hz}$. Determine the amplitude of electric current in the circuit and a phase difference between the voltage and the current, total power of the circuit.
- b. Explain about RLC Series resonance with phasor diagrams and find resonant frequency.

6 CO2 K3


4 CO2 K2

(OR)

- c. Write short notes on Resonance and Q factor. A pure resistor, a pure capacitor and a pure inductor are connected in parallel across a 50Hz supply; find the impedance of the circuit as seen by the supply. Also find the resonant frequency.
- d. What do you mean by dynamic impedance of a parallel resonance circuit? Calculate the value of R_C in the circuit as shown in Fig. to yield resonance.


5 CO2 K3

5 CO2 K3

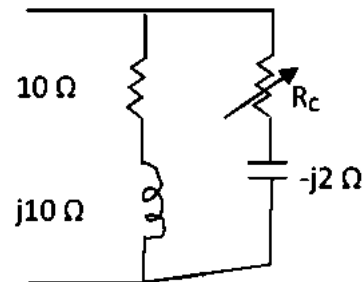

- 4.a. At $t=0$. Switch 1 in the figure is closed and switch 2 is closed 4 secs later. Find $i(t)$ for $t>0$. Calculate I for $t=2$ secs and $t=5$ secs.

6 CO3 K3

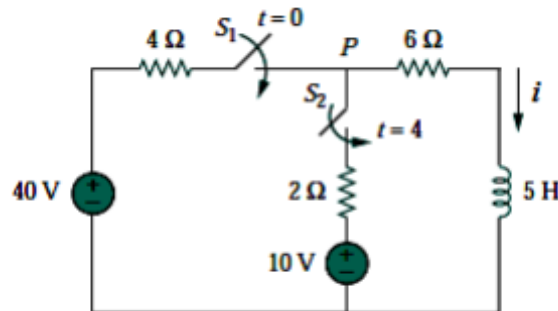


- b. Derive the Transient Response of series RL-circuit with D.C excitation.

4 CO3 K2

(OR)

- c. For the three coupled coils shown in figure. Calculate the total inductance.

6 CO5 K4

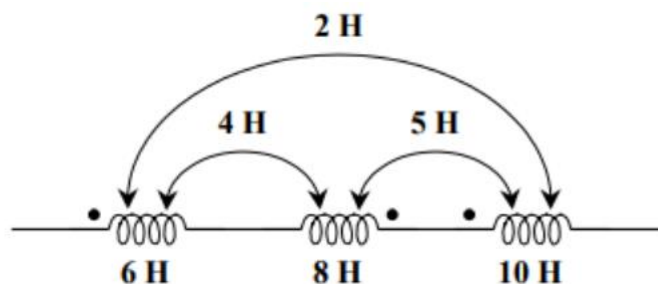


- d. Two inductors of 10mH respectively are connected together in a series combination so that their magnetic fields aid each other giving cumulative coupling. Their mutual inductance is given as 5mH . Calculate the total

4 CO5 K3

inductance of the series combination.


- 5.a. Find Z-parameter of a given circuit as shown in Fig 1:

5 CO4 K3

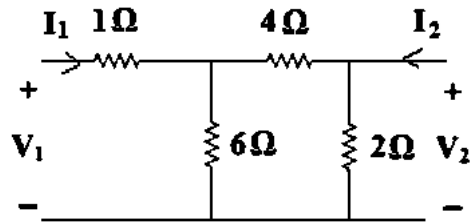

- b. Find hybrid parameter of the given circuit shown in figure.


5 CO4 K3

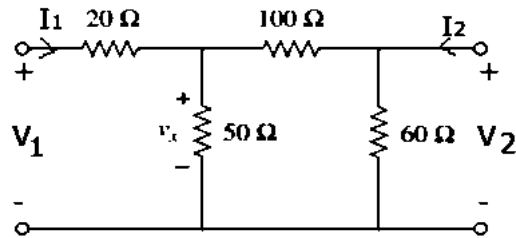

(OR)

- c. Find Y-parameter of a given circuit as shown in figure:

6 CO4 K3

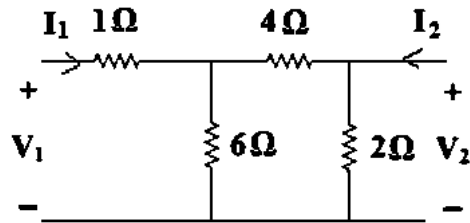

- d. Obtain Y- and h- parameter, if the other parameters are given below $A=2$, $B=-1$, $C=3$, and $D=-2$.
- 6.a. Derive the Incidence Matrix for a given graph as shown in fig 1.

4 CO4 K3

5 CO1 K3

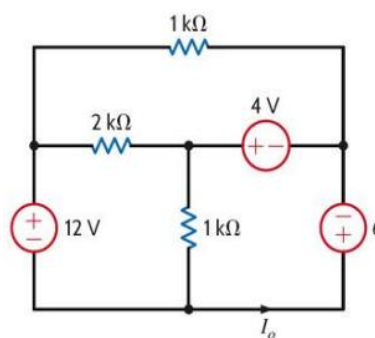
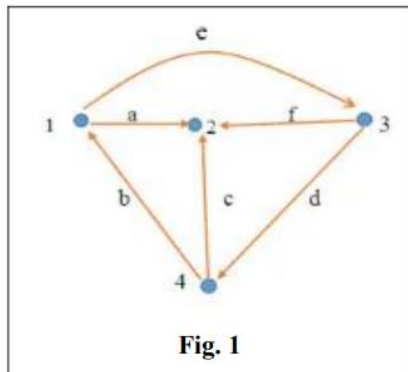


Fig.2

- b. Derive the Tie set Matrix for a given graph as shown in Fig 2.

5 CO1 K4

(OR)

- c. Compare the Incidence Matrix, Tie-Set Matrix, and Cut-Set Matrix in terms of their Applications.
- d. i) How does the co-efficient of coupling affected the mutual inductance of two coils?
- ii) If two coils have self-inductance of $L_1=4H$ and $L_2=9H$, and their mutual inductance $=6H$ calculate the co-efficient of coupling?

5 CO1 K2

5 CO5 K3

--- End of Paper ---