

# Gandhi Institute of Engineering and Technology University, Odisha, Gunupur (GIET University)



B. Tech (Sixth Semester - Regular) Examinations, April 2025

## 21BECPC36001 – Digital VLSI Design

(ECE)

Time: 3 hrs

Maximum: 70 Marks

**Answer ALL questions**  
(The figures in the right hand margin indicate marks)

### PART – A

(2 x 5 = 10 Marks)

Q.1. Answer **ALL** questions

- |  | CO # | Blooms Level |
|--|------|--------------|
| a. Define Moore's Law.   | CO1  | K1           |
| b. Define accumulation and inversion region in MOS capacitor.          | CO1  | K1           |
| c. Basic difference between a static CMOS and a dynamic CMOS .         | CO4  | K2           |
| d. What is the significance of CMOS technology in digital VLSI design? | CO4  | K2           |
| e. Define the noise margin and write the expression noise margin high. | CO3  | K2           |

### PART – B


(15 x 4 = 60 Marks)

Answer **ALL** the questions


- |   | Marks | CO # | Blooms Level |
|---|-------|------|--------------|
| 2. a. Explain the various VLSI design methodologies. Compare and contrast the Full-Custom, Semi-Custom, and Programmable Logic design approaches in terms of design time, flexibility, performance, and cost.   | 8     | CO2  | K4           |
| b. Explain the structural decomposition of a 4-bit adder. Illustrate the different levels of hierarchy involved in combining individual 1-bit full adders to form the 4-bit adder.  | 7     | CO3  | K4           |
| (OR)  |       |      |              |
| c. Describe the fabrication process flow for manufacturing a VLSI (Very-Large-Scale Integration) chip. Discuss the various steps involved, from wafer preparation to packaging.   | 8     | CO1  | K1           |
| d. Explain the behavior of a MOS (Metal-Oxide-Semiconductor) system under external bias. Derive the expressions for the threshold voltage and discuss the effects of various external biases (gate, drain, and source) on the operation of the MOS transistor.  | 7     | CO1  | K1           |
| 3.a. Consider a MOS structure comprising a n-type doped silicon substrate, a silicon dioxide layer, and a metal gate. The equilibrium Fermi potential of the doped silicon substrate is $\phi_{Fn} = 0.2$ eV. Electron affinity of silicon and the metal are 4.15 and 4.1eV respectively. Calculate the built-in potential difference across the MOS system. Draw the Energy band diagrams of the components that make up the MOS system. | 8     | CO1  | K1           |
| b. Draw the stick diagram of $Y = \overline{(A + B)} + C$   | 7     | CO2  | K3           |
| (OR)  |       |      |              |
| c. Design the combinational logic circuit $Y = \overline{A.B.C}$ using CMOS technology  | 5     | CO4  | K6           |
| d. Write the code of SR FF using Verilog code   | 10    | CO4  | K6           |
| 4.a. Explain working principle of CMOS transmission gate and find effective resistance of three different region  | 8     | CO4  | K4           |
| b. Derive the values of $V_{IH}$ and $V_{OH}$ for a CMOS inverter.  | 7     | CO3  | K4           |

(OR)

- |    |   |   |     |    |
|----|---|---|-----|----|
| c. | Consider a CMOS inverter circuit with the following parameters: $V_{DD} = 3.3 \text{ V}$<br>$V_{T,n} = 0.6 \text{ V}$ , $V_{T,p} = -0.7 \text{ V}$ $k_n = 200 \mu\text{A/V}^2$ $k_p = 80 \mu\text{A/V}^2$ (5.83) (5.84) Calculate<br>the noise margins of the circuit.. | 8 | CO3 | K4 |
| d. | Find the Elmore delay at node 1 node 7  | 7 | CO3 | K4 |

 


- |      |  |    |     |    |
|------|--|----|-----|----|
| 5.a. | Draw the CMOS SR-Latch circuit based on NAND gate and explain its function and write the corresponding truth table   | 10 | CO4 | K2 |
| b.   | Find an equivalent $(W/L)_p$ and $(W/L)_n$ of CMOS inverter circuit for simultaneous switching of all inputs, assuming that $(W/L)_p = 5$ for all pMOS transistors and $(W/L) = 6$ for all nMOS transistors. | 5  | CO3 | K3 |

 

(OR)

- |    |   |    |     |    |
|----|---|----|-----|----|
| c. | Explain the voltage bootstrapping method and discuss the need for bootstrapping, illustrate the working with a suitable circuit diagram, and derive the expression for the capacitor ratio $\frac{C_{boot}}{C_x}$ .                                 | 10 | CO3 | K4 |
| d. | Observe the given circuit and find the voltage $V_1$ , $V_2$ , $V_3$ , $V_4$ , and $V_5$ . Consider the threshold voltage for nMOS transistor M1, M2, M3, M4, and M5 as $V_{TH1}$ , $V_{TH2}$ , $V_{TH3}$ , $V_{TH4}$ , and $V_{TH5}$ respectively. | 5  | CO3 | K4 |

 

--- End of Paper ---