

Gandhi Institute of Engineering and Technology University, Odisha, Gunupur
(GIET University)



B. Tech (Sixth Semester - Regular) Examinations, April 2025
22BEEPC36001 – Electrical and Electronics Measurement
(EE/EEE)

Time: 3 hrs

Maximum: 70 Marks

Answer ALL questions**(The figures in the right hand margin indicate marks)****PART – A****(2 x 5 = 10 Marks)**Q.1. Answer **ALL** questions

- State types of Error.
- Explain benefits of IEEE Measurement standards.
- Draw the block diagram of Transducer.
- What is Q- Meter.
- Write down two advantages of current Transformer.

CO #	Blooms Level
CO1	K1
CO1	K1
CO2	K2
CO3	K2
CO4	K1

PART – B**(15 x 4 = 60 Marks)**Answer **ALL** questions.

- A PMMC has an internal moving-coil resistance of $100\ \Omega$ and gives full-scale deflection for 3 mA. Calculate the value of shunt resistance required to convert the PMMC meter into a DC ammeter with a range of 0 to 5 amperes.
 - Briefly explain LVDT with neat diagram.

(OR)

 - Two wattmeters are connected to measure the input power to a balanced 3-phase load by the two-wattmeter method. If the instrument readings are 8kW and 4kW, determine (i) the load power factor. (ii) Reactive power
 - Obtain B-H curve of a ring specimen.
- Draw the circuit diagram of Wein's Bridge, Derive the condition for balancing the Bridge and finding the unknown parameter. Determine the equivalent parallel resistance and capacitance that causes a Wien bridge to null with the following component values: $R_1 = 3.1\ k\ \Omega$, $C_1 = 5.2\ mF$, $R_2 = 25\ k\ \Omega$, $R_4 = 100\ k\ \Omega$ and $f = 2.5\ kHz$.
 - Explain how to measure pressure using capacitive type transducer.

(OR)

 - Explain the construction of Anderson's bridge. Derive the unknown quantities at balance condition. Also write its advantage and disadvantages.
 - Determine the insulation resistance of a short length of cable in which voltage falls from 125 to 100V in 25 seconds. The capacity of the condenser is $600 \times 10^{-12} F$
- Briefly explain about D' Arsonval type of galvanometer & Discuss about different galvanometer constants and its response under different damping conditions.
 - What is the Influence of Resistance on Damping? Explain in detail.

(OR)

Marks	CO #	Blooms Level
8	CO3	K2
7	CO2	K2
8	CO2	K2
7	CO2	K2
10	CO2	K3
5	CO2	K1
10	CO3	K2
5	CO4	K2
10	CO5	K2
5	CO5	K1

- | | | | | |
|------|--|---|-----|----|
| c. | Draw the sketch of Gall Tinsley AC potentiometer and describe how it standardized. | 8 | CO5 | K3 |
| d. | Describe the Construction, Theory and Principle of operation of Vernier potentiometer. | 7 | CO5 | K2 |
| 5.a. | With a block diagram, explain the working of digital CRO | 8 | CO6 | K3 |
| b. | Describe the working of different frequency distortion analysers with the help of block diagram. | 7 | CO4 | K2 |

(OR)

- | | | | | |
|----|--|----|-----|----|
| c. | Explain about the working principle of a CT and solve the following question
A 1000/5 A, 50 Hz CT has a secondary load burden comprising of non-inductive impedance of 1.6 ohm. The primary winding has 1 turn, iron loss is 1.5W, m.m.f = 100AT. Calculate the flux in the core and the ratio error. | 10 | CO4 | K2 |
| d. | Give the comparison between CT and PT. | 5 | CO6 | K2 |

--- End of Paper ---