



**GANDHI INSTITUTE OF ENGINEERING AND TECHNOLOGY UNIVERSITY,  
ODISHA, GUNUPUR  
(GIET UNIVERSITY)**

M. Sc. (Third Semester) Regular Examinations, December- 2024

**22PHPE302– Electronics**

(M.Sc. Physics)

Time: 3 hrs

Maximum: 60 Marks

(The figures in the right hand margin indicate marks.)

**PART – A**


**(2 x 10 = 20 Marks)**

Q.1. Answer **ALL** questions

- Determine the trans conductance of a JFET if its amplification factor is 96 and drain resistance is 32 k $\Omega$ .
- Define pinch off voltage in FET.
- Define cascading amplifier.
- Draw the graph of gain verses frequency
- What is the characteristic of Ideal OPAMP
- For the non-inverting amplifier given that input voltage is 5V and  $R_1=1k\Omega$  and  $R_f=5k\Omega$ . Calculate the output voltage.
- Derive the Boolean expression for the logic circuit shown below:


CO #      Blooms  
Level

CO1	K1
CO1	K1
CO1	K1
CO1	K2
CO1	K2
CO2	K2
CO3	K2

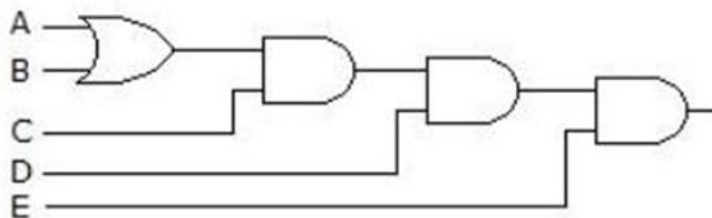

- Explain the frequency response of two-stage RC coupled amplifier.
- Write the truth table of JK-Flip Flop.
- Calculate potential difference between x and y

CO2	K2
CO2	K1
CO3	K2

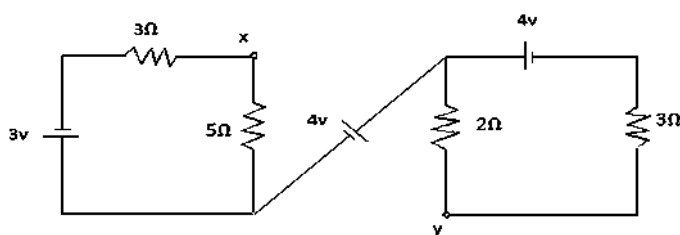

**PART – B**

**(10 x 5 = 50 Marks)**


Answer **ANY FIVE** questions

- Explain H Parameters in CB, CE and CC Hybrid model of Transistor.
- Explain construction and working principle of FET.
- With the neat diagram explain the working principle of two-stage transformer-coupled amplifier


Marks      CO #      Blooms  
Level

5	CO1	K1
5	CO1	K1
7	CO1	K2

- |       |  |   |     |    |
|-------|--|---|-----|----|
| b.    | Explain Depletion Mode of MOSFET. Write I-V characteristic of MOSFET.  | 3 | CO2 | K1 |
| 4. a. | Explain the Wein Bridge Oscillator in detail.  | 5 | CO1 | K1 |
| b.    | With the neat circuit diagram explain the working of phase shift oscillator  | 5 | CO1 | K2 |
| 5.a.  | Determine the amount of current from point A to point B in this circuit, and also the output voltage of the operational amplifier: | 7 | CO3 | K2 |

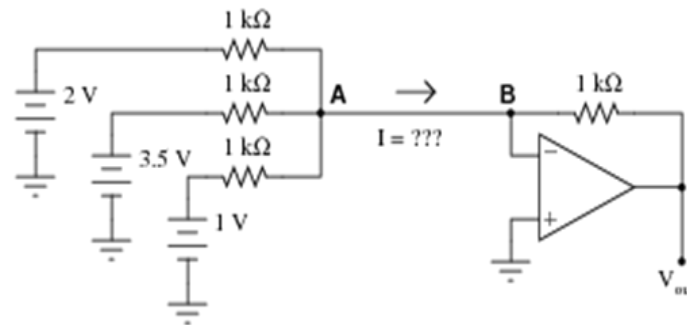

- |    |  |   |     |    |
|----|--|---|-----|----|
| b. | Derive the Boolean expression for the logic circuit shown below: | 3 | CO2 | K2 |
|----|--|---|-----|----|

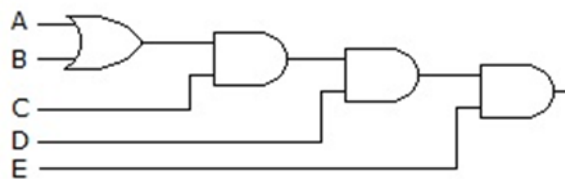

- |       |  |   |     |    |
|-------|--|---|-----|----|
| 6. a. | Explain the action of TTL NOT gate.                          | 5 | CO1 | K2 |
| b.    | With a label diagram explain AC analysis.                    | 5 | CO2 | K1 |
| 7.a.  | Simplify the following expression and draw the logic circuit | 5 | CO3 | K2 |

I.  $Y = [A\bar{B}(C + BD) + A\bar{B}]C$

II.  $Y = (A + B)(\bar{A} + C)(B + C)$

- |       |   |   |     |    |
|-------|---|---|-----|----|
| b.    | Construct All Gates with the help of NOR Gate   | 5 | CO2 | K2 |
| 8. a. | State and Explain Thevenins theorem   | 5 | CO1 | K1 |
| b.    | Calculate the current through the resistor of resistance $6\ \Omega$ using Thevenins theorem. | 5 | CO3 | K2 |

