

**Gandhi Institute of Engineering and Technology University, Odisha, Gunupur
(GIET University)**



M.Tech. (First Semester - Regular) Examinations, January – 2026
24MISPC11003 – Electrical Technology and Safety in Electrical System

Time: 3 hrs

Maximum: 60 Marks

**Answer ALL questions
(The figures in the right hand margin indicate marks)**

PART – A **(2 x 5 = 10 Marks)**

	CO #	Blooms Level
Q.1. Answer <i>ALL</i> questions		
a. Give one example of a DC source.	CO1	K1
b. How many conductors are used in a single-phase system?	CO1	K2
c. What happens to resistance when temperature increases?	CO2	K1
d. What type of energy is stored in a capacitor?	CO2	K2
e. State the principle of operation of an electric motor.	CO3	K2

PART – B **(10 x 5 = 50 Marks)**

	Marks	CO #	Blooms Level
<u>Answer ALL the questions</u>			
2. a. Three resistors of 4 Ω, 6 Ω, and 12 Ω are connected in parallel across a 24 V supply. Find: Equivalent resistance, Total current, Current through each resistor	5	CO1	K2
b. Explain Kirchhoff’s laws and explain their physical significance.	5	CO1	K2
(OR)			
c. Discuss the relationship between current, voltage and resistance with a suitable circuit diagram.	5	CO1	K2
d. Compare AC and DC with advantages and disadvantages.	5	CO1	K1
3.a. Analyze the transient response of an RC circuit for DC excitation. Derive the expressions for charging and discharging of a capacitor and explain the significance of time constant.	5	CO2	K1
b. Explain the transient and steady-state response of an RL circuit. Derive expressions for current growth and decay and discuss energy storage.	5	CO2	K2
(OR)			
c. Explain the operation of a series RLC circuit. Derive the condition for resonance and discuss bandwidth, quality factor, and frequency response.	5	CO2	K2
d. State and prove Norton’s theorem. Develop the Norton equivalent circuit for a given linear network and explain its advantages in network analysis.	5	CO2	K1
4.a. In the circuit below, determine the current through a load resistance of 6 Ω using Thevenin’s theorem .	5	CO3	K1
<ul style="list-style-type: none"> • A 20 V source in series with 4 Ω • In parallel with a 10 V source in series with 2 Ω Load resistance 6 Ω connected across the output terminals			
b. Using Norton’s theorem , find the current through a 8 Ω load resistor connected across the terminals of a network containing:	5	CO3	K2
<ul style="list-style-type: none"> • A 24 V source in series with 6 Ω • A parallel branch of 12 Ω 			

(OR)

- | | | | | |
|------|---|---|-----|----|
| c. | Discuss the working principle and construction of a transformer. | 5 | CO3 | K2 |
| d. | Discuss the construction, working principle, and characteristics of an electrical fuse. | 5 | CO3 | K1 |
| 5.a. | A single-phase transformer has a turns ratio of 5:1.
Primary voltage = 2500 V, primary current = 10 A.
Efficiency = 90%.
Calculate: Secondary voltage, Output power, Secondary current | 5 | CO3 | K2 |
| b. | Compare the operation, applications, and protective features of fuses and circuit breakers in electrical power systems. | 5 | CO3 | K1 |
| (OR) | | | | |
| c. | A DC generator has 6 poles, 720 conductors, and runs at 600 rpm.
The flux per pole is 25 mWb. The armature is lap wound.
Calculate the generated EMF. | 5 | CO3 | K2 |
| d. | A fuse is rated at 10 A and has a fusing factor of 1.5 .
Find:
1. Minimum fusing current
2. Power dissipated in the fuse if fuse resistance is 0.02 Ω | 5 | CO3 | K2 |
| 6.a. | A single-phase load takes 12 A from a 230 V supply at a power factor of 0.6 lagging. Find: Apparent power, Reactive power. | 5 | CO1 | K2 |
| b. | Discuss power, power factor, and losses in a single-phase AC circuit. | 5 | CO1 | K1 |
| (OR) | | | | |
| c. | A delta-connected load has phase impedance 20 Ω and is supplied at 420 V .
Find: Phase current, Line current | 5 | CO1 | K2 |
| d. | Discuss the construction and working of a single-phase AC system with a neat diagram. | 5 | CO1 | K2 |

--- End of Paper ---