

**Gandhi Institute of Engineering and Technology University, Odisha, Gunupur
(GIET University)**



B. Tech (Fourth Semester – Regular/Supplementary) Examinations, April 2026

23BECPC24001 - Digital System Design

(ECE)

Time: 3 Hours

Maximum: 60 Marks

Answer ALL Questions.

(The figures in the right hand margin indicate marks.)

PART – A (Short Answer Questions)

(2 × 5 = 10 Marks)

Q.1. Answer ALL Questions.

- | | | |
|--|-----|-----|
| | CO# | BTL |
| a. Convert $(634)_8$ to binary, hexadecimal, and decimal. | CO1 | K3 |
| b. What is Gray code? Convert $(100110101)_2$ into Gray code. | CO2 | K3 |
| c. State DeMorgan's theorem. | CO2 | K1 |
| d. Write a characteristic equation and excitation table for the D flip-flop. | CO3 | K2 |
| e. Differentiate between static and dynamic RAM. | CO5 | K2 |

PART – B (Long Answer Questions)

(10 × 5 = 50 Marks)

Answer ALL Questions.

- | | | | |
|---|-------|-----|-----|
| | Marks | CO# | BTL |
| 2. a. Carry out the following additions: | 6 | CO1 | K3 |
| (i) $(+13, -11)$ using 1's complement notation. | | | |
| (ii) $(-15, +9)$ using 2's complement notation. | | | |
| b. Simplify the following Boolean functions to a minimum number of literals. | 4 | CO2 | K3 |
| (i) $x(x' + y)$ | | | |
| (ii) $xy + x'z + yz$ | | | |
| (OR) | | | |
| c. Express -3.75 as a floating point number using IEEE single precision. | 6 | CO1 | K3 |
| d. Construct logic circuit using AND, OR, and NOT gate for the following Boolean function: | 4 | CO2 | K4 |
| (i) $Y = (A + B)(A' + B')$ | | | |
| (ii) $Y = (A + B)(C' + D')(A' + C)$ | | | |
| 3.a. Simplify the following Boolean function using a four-variable K-map: | 6 | CO2 | K3 |
| $F(A, B, C, D) = \sum (0, 1, 3, 4, 5, 7, 9, 11, 15)$ | | | |
| and then, realize the simplified functions using logic gates. | | | |
| b. Express the Boolean function $f = xy + x'z$ in a product of maxterms. | 4 | CO2 | K3 |
| (OR) | | | |
| c. Implement the following Boolean function with NOR gates. | 6 | CO2 | K4 |
| $F = (AB' + A'B)(C + D')$ | | | |
| d. Reduce the Boolean expression $A + B[AC + (B + \overline{C})D]$ | 4 | CO2 | K3 |
| 4.a. What is a full adder circuit? Draw its truth table. Design a full adder circuit using two half adder circuits and an 'OR' gate. | 6 | CO3 | K4 |
| b. Implement the Boolean function $F(x, y, z) = \sum (1, 2, 6, 7)$ with a multiplexer. | 4 | CO3 | K4 |
| (OR) | | | |
| c. Design a combinational circuit which will convert a 4-bit binary number to a 4-bit Gray code. | 6 | CO3 | K4 |
| d. Construct a 4-to-16-line decoder with two 3-to-8-line decoders with enable. | 4 | CO3 | K4 |
| 5.a. Design a counter with the following repeated binary sequence: 0, 1, 2, 4, 6. | 6 | CO5 | K4 |


Use *D* flip-flops.

- b.** Describe the construction and operation of a master-slave flip-flop. 4 CO4 K2
(OR)

- c.** With a neat logic diagram explain how a *T* flip-flop can be converted to a *D* flip-flop. 6 CO4 K4

- d.** What is a shift register? Explain the principle of a 4-bit serial-in, serial-out, shift register. 4 CO5 K2

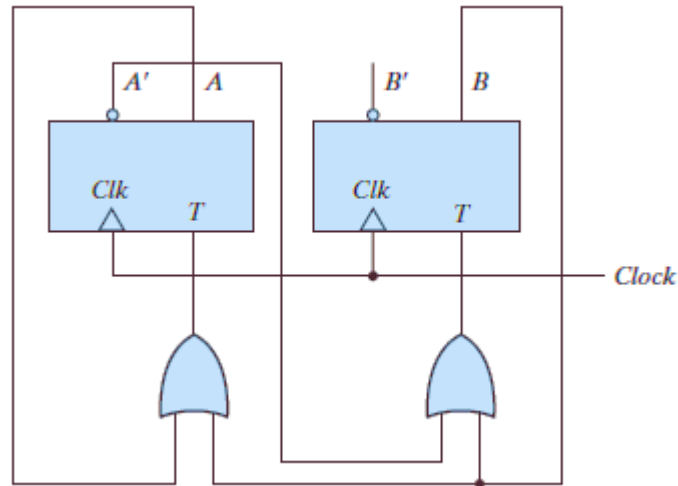
- 6.a.** Derive the state table and the state diagram of the sequential circuit shown in the figure. 6 CO4 K4



- b.** Design a combinational circuit using a ROM. The circuit accepts a 3-bit binary number and generates an output binary number equal to the square of the input number. 4 CO5 K4

(OR)

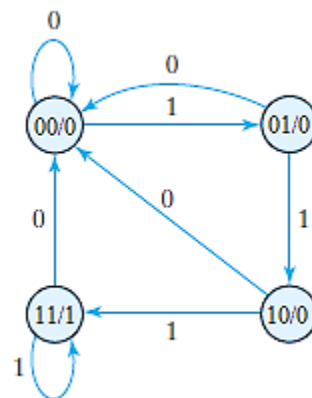- c.** Design the sequential circuit specified by the state diagram of the figure using *D* flip-flops. 6 CO4 K4



- d.** A 3-input majority circuit produces the output as '1' when the number of 1's is more than the number of 0's at the input. Implement it using ROM. 4 CO5 K4

--- End of Paper ---