

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages:

**M.TECH**  
**P2VDCC09**

**2<sup>nd</sup> Semester Regular Examination 2016-17**

**RF AND MIXED SIGNAL INTEGRATED CIRCUIT**

**BRANCH: COMMUNICATION ENGG, COMMUNICATION SYSTEMS, ELECTRONIC & COMM. ENGG, ELECTRONIC AND TELECOMMUNICATION ENGG, SIGNAL PROCESSING**

**Time: 3 Hours**

**Max Marks: 100**

**Q.CODE:Z845**

**Answer Part-A which is compulsory and any four from Part-B.  
The figures in the right hand margin indicate marks.**

**Part – A (Answer all the questions)**

- Q1** Answer the following questions: **Short answer type** (2 x 10)
- a) Write the different types of amplifier configuration in RFIC design? Which one is the most efficient among them?
  - b) What is coupling capacitor? What is coupling coefficient?
  - c) What is SDFR?
  - d) Draw the block diagram for super heterodyne receive?
  - e) Write the difference between passive and active components?
  - f) Derive the expression for the gain constant of SR-Flip-flop which act as a phase detector?
  - g) What is Shanon Formulation?
  - h) What is skin effect?
  - i) Find out the gain of CS amplifiers having load resistance  $R_L$ .
  - j) What are negative resistance oscillators?

**Part – B (Answer any four questions)**

- Q2**
- a) Explain how one can increase bandwidth of amplifiers Neutralization and unilateralization? (10)
  - b) A rectangular aluminum line has width  $20\mu\text{m}$ , a thickness of  $3\mu\text{m}$  and length of  $100\mu\text{m}$ . Compute the resistance of line at DC and at 5 HZ. Assuming that all the current flows in an area of skin depth from the surface. Assume that aluminum has a resistivity of  $3\mu\Omega\text{cm}$ . (5)
  - c) Explain bandwidth shrinkage in cascade amplifiers and also derive the expression for optimum gain per stage? (5)
- Q3**
- a) Briefly explains about Bandwidth estimation technique in the method of open circuit time constant and short circuit time constant? (10)
  - b) Given polysilicon Resistor with the value is given,  $W = 0.08\mu\text{m}$ ,  $L = 20\mu\text{m}$ . Calculate the values of  $\rho_s$  (in  $\Omega/\square$ ), no. of squares of resistance and resistance. Assume that  $\rho$  for polysilicon is  $9 \times 10^{-4}$  (10)
- Q4**
- a) Explain IP3. State and explain methods for estimating IP3? (10)
  - b) Discuss the CMOS compatible band gap reference circuit? (5)
  - c) What is Passive component? Briefly explains about woven capacitor? (5)
- Q5**
- a) Briefly explain about PLL architecture? (10)

- b) Briefly explains about the charge pump in PLL models? (10)
- Q6** a) What is Noise Factor? Derive the expression for noise factor in terms of  $F_{\min}$  and source admittance in classical two-port noise theory. (10)
- b) Explain the operation of start-up network? (10)
- Q7** **Write short notes (any four)** (5x4)
- i) Tuned oscillator
  - ii) Skin depth
  - iii) Class E and Class F amplifiers
  - iv) Diode Ring Mixer
  - v) AM-PM conversion