

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

M.TECH
PEPC103

1st Semester Back Examination – 2016-17
ELECTRIC DRIVE - 1
BRANCH(S): Power Electronics & Drives
Time: 3 Hours
Max marks: 70
Q.CODE:Y894

Answer Question No.1 which is compulsory and any five from the rest.
The figures in the right hand margin indicate marks.

- Q1 Answer the following questions: (2 x 10)
- Give an example, where electric drive is operated at rated torque and zero speed.
 - What are the characteristics of active load? How does it differ from passive load?
 - A single phase uncontrolled rectifier is feeding a resistive load. Draw the input and output current waveform with a common reference axis.
 - A motor having moment of Inertia J_o is connected to the load having moment of inertia J_m through a set of gear having a teeth ratio $N_1 : N_2$. Calculate the equivalent Moment of Inertia referred to the load side.
 - Derive the normalized torque equation for a chopper controlled dc motor drive.
 - Draw the circuit diagram for a voltage-controlled induction motor drive.
 - How regenerative braking can be applied to an Induction Motor drive?
 - Draw the output voltage, armature current and supply current waveform of the first quadrant operation of chopper circuit feeding the armature of a separately excited dc motor drive.
 - A 3-phase fully controlled rectifier is feeding a resistive load. Draw the output phase and line voltage with a common reference axis.
 - Draw the gating pulses for a three-phase thyristor converter fed to a resistive load.
- Q2
- Determine the stable operating speed of a three phase Induction Motor drive for (i) constant torque load and (ii) Fan load torque. (5)
 - Give an example of a mechanical load, where torque is negative but speed is positive. Justify. (5)
- Q3
- Derive the expression for normalized torque of the three phase converter controlled by the DC motor drive in steady state. (5)
 - Consider a motor drive with $R_{an}=0.1$ p.u., $\phi_{fn}=1$ p.u., $V_n=1.1$ p.u. and extreme load operating point $T_{e1(\min)} = 0.1$ p.u., $w_{mn(\min)} = 0.1$ p.u., $T_{e2(\max)} = 1$ p.u., and $w_{mn(\max)} = w_{mn2} = 1$ p.u. Find the normalized control voltage to meet these operating points. (5)
- Q4 Derive the output current equation for a chopper controlled dc motor drive in (10)

just-continuous conduction mode.

- Q5 a) Explain with the suitable block diagram the control circuitry for a four quadrant dc motor drive. (5)
- b) A dc motor is driven from a chopper with a source voltage of 24V dc and at a frequency of 1kHz. Determine the variation in duty cycle required to have a speed variation of 0 and 1 p.u. delivering a constant 2 p.u. load. The motor details are as follows
1hp, 10V, 2500rpm, 78.5% efficiency, $R_a=0.01\Omega$, $L_a=0.003H$, $K_b=0.038V/rad/sec$.
The chopper is one-quadrant, and the on-state drop voltage across the device is assumed to be 1V regardless of the current variation. (5)
- Q6 a) Explain with a suitable block diagram, how to decouple the inner current loop from the dc motor-inherent induced-emf loop. (5)
- b) Explain the working of a unipolar sinusoidal pulse width modulated –VSI feeding an induction motor drive for a modulation index = 1 and modulating frequency = 7. (5)
- Q7 a) Derive the output current equation of a 3-phase converter feeding a dc motor drive in steady state. Neglect the commutation effect. (5)
- b) Explain the speed control of 3-phase Induction motor drive using constant volts/Hz control. (5)
- Q8 Answer any two. (5 x 2)
- a) Slip-power recovery scheme.
- b) Variable frequency VSI Drives
- c) Efficient braking in an Induction motor drive.