

Registration No:

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Total Number of Pages: 02

M.TECH

P1EEBC03,P1ELBC03,P1IPBC03

1st Semester Regular Examination 2016-17
POWER CONVERSION DEVICES AND DRIVES

BRANCH: EPS,EE,PET,PE,PSE,PS,ESE,PEET,PEPS,PEES,PEE,IPCT(PT),EEE

Time: 3 Hours

Max Marks: 100

Q.CODE:Y950

Answer Question No.1 which is compulsory and any FOUR from the rest.
The figures in the right hand margin indicate marks.

Q1 Answer the following questions: **Short answer type** (2 x 10)

- What is damper winding and why it is used in synchronous machine ?
- Draw the basic diagram for Kron's primitive machine with two pole ?
- Which coils are called "Pseudo stationary " ? Explain with example ?
- Power input to 3 phase induction motor is 50kW.If the stator copper loss is 1kW What is the rotor copper loss if motor is running with a slip of 4% ?
- What is the minimum value of firing angle above which the output current supplied to a purely resistive load fed from a three phase half wave controlled rectifier becomes discontinuous?
- What are the advantages of circulating current mode dual converter over non-circulating current mode dual converter?
- What is four quadrant dc-dc converter? Give its circuit diagram.
- Derive the steady state stability criteria for electric drive.
- Discuss the criteria of matching between the motor and power electronic converter.
- What is the difference between static Kramer drive and static Scherbius drive?

Q2 a) Deduce Park's Transformation relating to 3 phase currents of a synchronous machine to its corresponding d-q axis currents ? (10)

b) A 11 kV, 3 phase star connected synchronous motor draws a current of 45 A .The effective resistance and synchronous reactance per phase are 0.9Ω and 28Ω respectively. Calculate the power supplied to motor and the induced e.m.f for a power factor of 0.8(lag) ? (10)

Q3 a) Derive the expression for Synchronous Inductance (L_s) in terms of space fundamental component and leakage inductance for 3 phase cylindrical rotor machine ? (10)

b) Explain the complete torque speed characteristic of 3 phase induction motor ? (10)

Q4 a) The following data referred to a 10 pole ,400 V ,50Hz 3 phase Induction (10)

motor $R_1=1.75 \Omega$, $X_1=5.5 \Omega$ R_2' (Rotor resistance referred to stator) $=2.25 \Omega$, X_2' (Rotor stand still reactance referred to stator) $= 6.6 \Omega$
 When the motor is tested on no load it takes 3.8 A (Line Current) and the total core loss is 310W. Use approximate equivalent circuit at 4% slip, Calculate a) Rotor Current referred to stator b) Mechanical Power developed ?

b) Explain the working of a three phase ac voltage regulator with relevant circuit diagram and wave forms. Give one of its important application. **(10)**

Q5 a) Derive the expression for the average and rms output voltage of a three phase semi-converter. Also draw the waveform of voltage across any SCR of the three phase semi-converter. **(10)**

b) A single phase full wave controlled rectifier feeds R-L load with $R= 10 \Omega$ and $L= 50 \text{ mH}$. The ideal sinusoidal voltage supplied is $v_s=240\sqrt{2} \sin \omega t$ at 50 Hz **(10)**

Calculate the average and rms load currents, the power dissipation and the power factor at the supply terminals, if the thyristor firing angle $\alpha =45^\circ$

Q6 a) Describe the soft starting of induction motor with suitable diagram & discuss the disadvantage of Stator voltage control scheme. Explain the impact of non-sinusoidal excitation on induction motor. **(10)**

b) Discuss variable frequency control of induction motor drive. Explain the closed loop control of variable frequency PWM-VSI fed Induction Motor drive with suitable diagram and give a comparison between Square wave VSI and PWM-VSI drive. **(10)**

Q7 a) What is slip power recovery scheme? Explain Static Kramer drive with neat circuit diagram and derive the electromagnetic torque produced under this scheme. **(10)**

b) A 400V, 50Hz, 970 rpm, 6 pole, Y-connected wound rotor induction motor has following parameters referred to stator, $R_s=0.1\Omega$, $R_r'=0.08 \Omega$, $X_s=0.3\Omega$, $X_r'=0.4\Omega$. Stator to rotor turns ratio $n=2$. Motor speed is controlled by static Kramer drive. The drive is designed for a speed range of 25% below synchronous speed. Maximum value of firing angle is 165° and resistance of DC link inductor is 0.01Ω . Calculate (i) Transformer turns ratio (ii) Torque for a speed of 780 rpm and firing angle of 140° . (iii) firing angle for half the rated torque and speed of 800 rpm **(10)**