

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

**M.TECH**  
**PEPC201/PPPC201**

**2<sup>nd</sup> Sem M Tech Regular/ Back Examination – 2015-16**

**POWER CONVERTER-II**

**PED/POWER ELECTRONICS/**

**POWER ELECTRONICS AND POWER SYSTEM**

**Time: 3 Hours**

**Max marks: 70**

**Q.CODE:W759**


**Answer Question No.1 which is compulsory and any five from the rest.  
The figures in the right hand margin indicate marks.**

- Q1 Answer the following questions: (2 x 10)
- What is the difference between unipolar and bipolar switching in PWM?
  - A filter at the input stage is required in a buck converter where as in boost converter a input filter may not be required, why?
  - How the current and source inverters are different?
  - In SVM why two consecutive voltage vectors are selected for synthesizing the reference voltage vectors?
  - Draw the circuit diagram of two-transistor flyback converter.
  - What will happen in forward converter if we select tertiary turns equal to primary turns and duty ratio greater than 0.5?
  - What is total harmonic distortion and how it is related to distortion factor?
  - Draw the characteristics showing the effect of parasitic elements on the voltage conversion ratio in a buck-boost converter.
  - What is the difference between PWM and SVM?
  - Draw the basic circuit of L-type and M-type resonant converter switch.
- Q2
- What is switch mode rectifier? Describe the operation of a single phase switch mode rectifier. What will happen if the inductor is moved from load side to source side? (5)
  - Explain the operation of series inverter with diagram and waveforms. What are disadvantages and how they are overcome? (5)
- Q3
- Describe the operation of 5-level flying capacitors multilevel inverter with diagrams and the switching states in a table. (6)
  - What is reactive power compensation using multilevel inverter? Explain using phasor diagrams. (4)
- Q4 For three phase SVM Based inverter, derive the expressions of durations for which the consecutive voltage vectors are to be applied in order to synthesize  $V_{ref}$ , in case the reference vector is lying in sector one. What do you mean by pulse of appropriate polarity? (7+3)
- Q5
- Derive the expression for output voltage of Boost converter by considering a non-ideal inductor that is the inductor has a finite resistance 'r'. (5)

- b) In a step down converter, consider all components to be ideal.  $V_0$  is held constant at 5V by controlling the switch duty ratio  $D$ . calculate the minimum inductance  $L$  required to keep the converter operation in continuous conduction mode under all conditions if  $V_d(\text{input})$  is 10-40V,  $P_0$  greater than equal to 5W and  $f_s=50\text{kHz}$ . (5)


- Q6 a) Explain the working of an L-type zero current switch resonant converter with circuits and waveforms. (5)

- b) (5)

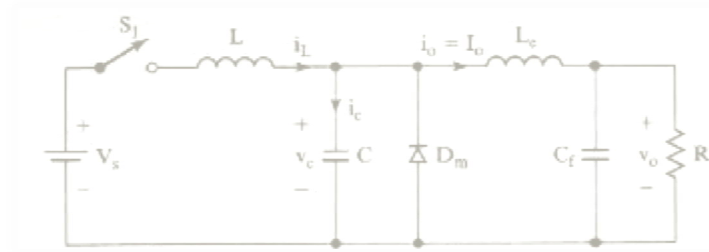

The ZCS resonant converter shown above delivers a maximum power of  $P_L=400\text{mW}$  at  $V_0=4\text{V}$ . The supply voltage is  $V_s=12\text{V}$ . The maximum operating frequency is  $f_{\text{max}}=50\text{kHz}$ . Determine the values of  $L$  and  $C$ . Assume the mode I and mode III time intervals  $t_1$  and  $t_3$  are negligible and  $x=1.5$ , where  $x=I_m/I_0$ .

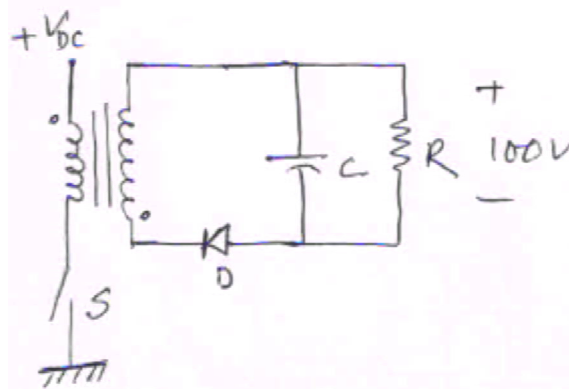- Q7 Find the turns ratio of the transformer such that output voltage required is 100V at  $D=0.5$  for nominal input voltage of 12V in the below mentioned circuit. (10)



- Compute the minimum and maximum value of  $D$  if input is varied from 10V to 14V, keeping  $V_0$  constant.
- Compute the value of  $L_s$  on the secondary side so that  $i_2$  is just continuous at minimum value of  $D$ .
- Find the value of ' $C$ ' for output voltage ripple of 1% at  $D=D_{\text{max}}$ . Take  $V_D=0.8\text{V}$ , voltage across the switch ' $S$ '= $0.8\text{V}$ ,  $f_s=2\text{kHz}$ .

- Q8 Answer any two (5 x 2)

- Forward converter
- Current regulated PWM voltage source inverter
- Sepic converter
- Three Phase Series Inverter.