

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 2

M.TECH
PEPC103

1st Semester M.Tech Regular/Back Examination – 2015-16
ELECTRIC DRIVE - 1

BRANCH(S): Power Electronics & Drive

Time: 3 Hours

Max marks: 70


Q.CODE:T1097

Answer Question No.1 which is compulsory and any five from the rest.
The figures in the right hand margin indicate marks.

Q1 Answer the following questions:

(2 x 10)

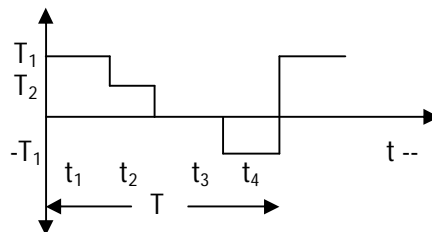- a) An electric train's torque is shown in figure below for one cycle. Determine the effective electromagnetic torque.



- b) What is the difference between active and passive load? Give an example of active and passive load.
- c) A single phase fully controlled rectifier is feeding a highly inductive load. Draw the input and output current waveform with a common reference axis.
- d) A motor having moment of Inertia J_o is connected to the load having moment of inertia J_m through a set of gear having a teeth ratio $N_1 : N_2$. Calculate the equivalent Moment of Inertia referred to the motor side.
- e) Derive the normalized torque equation for a chopper controlled dc motor drive.
- f) Draw the circuit diagram for a reversible phase-controlled induction motor drive.
- g) Can a slip-energy controlled induction motor be reversed in speed? How is it done?
- h) Draw the output voltage, armature current and supply current waveform of the second quadrant operation of chopper circuit feeding the armature of a separately excited dc motor drive.
- i) A 3-phase fully controlled rectifier is feeding a resistive load. Draw the output current and input (any one line current waveform) with a common reference axis.
- j) Draw the gating pulses for a three-phase thyristor converter fed to a resistive load.

Q2 a) A separately excited dc motor with the following parameters: $R_a=0.5\Omega$,

(5)

$L_a=0.004\text{H}$, and $K_b=0.8\text{V/sec}$ is driving a load of $J=0.0167\text{kg-m}^2$, $B_1=0.01\text{ N.m/rad/sec}$ with a load torque of 100Nm . Its armature is connected to a dc supply voltage of 210V and is giving the rated field current. Find the speed of the motor.

- b) If the separately excited dc motor with the specification above is started directly from a 210V dc supply with no load. Find the mathematical equation of its starting speed. (5)
- Q3 a) Derive the expression for normalized torque of the three phase converter controlled by the DC motor drive in steady state. (5)
- b) Consider a motor drive with $R_{an}=0.1\text{p.u.}$, $\phi_{fn}=1\text{ p.u.}$, $V_n=1.1\text{ p.u.}$ and extreme load operating point $T_{e1(\text{min})} = 0.1\text{ p.u.}$, $w_{mn(\text{min})}=0.1\text{ p.u.}$, $T_{e2(\text{max})} = 1\text{ p.u.}$, and $w_{mn(\text{max})} = w_{mn2}=1\text{p.u.}$ Find the normalized control voltage to meet these operating points. (5)
- Q4 Derive the output current equation for a chopper controlled dc motor drive in continuous conduction mode. (10)
- Q5 a) Explain with the suitable block diagram the control circuitry for a four quadrant dc motor drive. (5)
- b) A dc motor is driven from a chopper with a source voltage of 24V dc and at a frequency of 1kHz . Determine the variation in duty cycle required to have a speed variation of 0 and 1 p.u. delivering a constant 2 p.u. load. The motor details are as follows
 1hp , 10V , 2500rpm , 78.5% efficiency, $R_a=0.01\Omega$, $L_a=0.003\text{H}$, $K_b=0.038\text{V/rad/sec}$.
 The chopper is one-quadrant, and the on-state drop voltage across the device is assumed to be 1V regardless of the current variation. (5)
- Q6 a) Explain with a suitable block diagram, how to decouple the inner current loop from the dc motor-inherent induced-emf loop. (5)
- b) Draw the gate pulses for a bipolar sinusoidal pulse width modulated – VSI feeding an induction motor drive for a modulation index = 1 and modulating frequency = 7. (5)
- Q7 a) Derive the output current equation of a 3-phase converter feeding a dc motor drive in steady state. Neglect the commutation effect. (5)
- b) Explain the speed control of 3-phase Induction motor drive using constant volts/Hz control. (5)
- Q8 Answer any two. (5 x 2)
- a) Steady state stability of a drive depends on relative characteristic of the motor and load and not just on motor (or load) characteristic.
- b) Rectifier-inverter power stages for slip-power recovery scheme.
- c) Variable frequency CSI Drives
- d) Impact of Non-Sinusoidal excitation on Induction motor.