

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 01

**M.TECH**  
**EEPE 201**

**2<sup>nd</sup> Semester M Tech Examination – 2015**

**HVDC TRANSMISSION AND FACTS**

**BRANCH(S): POWER ELECTRONICS/POWER ELECTRONICS AND  
DRIVES/POWER ELECTRONICS AND ELECTRICAL DRIVES/ POWER SYSTEM  
ENGINEERING**

**Time: 3 Hours**

**Max marks: 70**

**Q.CODE:T287**

**Answer Question No.1 which is compulsory and any five from the rest.  
The figures in the right hand margin indicate marks.**

- Q1 Answer the following questions: (2 x 10)
- a) What is the importance of surge impedance loading?
  - b) Explain the operation of converter when overlap angle is greater than  $60^\circ$ .
  - c) Compare ROW for DC And AC Transmission.
  - d) Compare reliability of DC Transmission as compared AC system.
  - e) What is commutating emf?
  - f) Show the configuration of double tuned filter; also give its impedance characteristics as a function of frequency.
  - g) What is a Synchronous condenser?
  - h) Give the steady state V-I characteristic of the SVC and STATCOM.
  - i) Give the basic Thyristor controlled series Capacitor scheme.
  - j) Midpoint shunt compensation can significantly increase the transmittable power. Explain.
- Q2 Explain two and three valve conduction mode of a converter. Derive the expression for average output voltage. (5+5)
- Q3 a) Compare power transfer capability of bipolar DC line with 3-Phase AC line. (5)  
b) Explain the operation of 12 pulse converter and show the output waveform. (5)
- Q4 a) How harmonics can be eliminated in HVDC Transmission. (5)  
b) Derive the equivalent circuit of an inverter. (5)
- Q5 a) For a 3 phase bridge circuit, the secondary voltage on transformer side is 400kV rms with reactance  $X=40\Omega$ . find the DC output voltage, overlap angle if output current is 2000A and firing angle  $\alpha=15^\circ$ . (6)  
b) What are different types of HVDC links? (4)
- Q6 Explain about power flow and dynamic stability consideration of a transmission interconnection. (10)
- Q7 Explain the operating principle of TSC-TCR type compensator. (10)
- Q8 Write short notes on any two (5 x 2)
- a) Generation of harmonics by Converters
  - b) UPFC
  - c) TCSC
  - d) STATCOM