

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.TECH

B.TECH 1ST SEMESTER REGULAR EXAMINATIONS, DECEMBER 2017

BASICS OF ELECTRONICS

Subject Code:BBSES1041

Time: 3 Hours

Max Marks : 100

The figures in the right hand margin indicate marks.

PART-A**(10X1 = 10 MARKS)**

Answer all questions.

- The Ripple factor value of Full wave rectifier is ?
- The expression of β in terms of α is.....?
- The expression I_{RMS} for HWR is?
- BJT acts as a switch in -----region of operation.
- When $V_{DS}=V_{GS}-V_T$, Enhancement Mosfet is working in ----- mode.
- Lissajous pattern is mostly used for measuring-----.
- The binary number 10101 is equivalent to decimal number
- For display of signal pattern voltage is applied to the horizontal plates of a CRO
- The form factor value of full wave rectifier is?
- To design Ex-OR gate, minimumno.of NAND gates are required ?

PART-B**(15 x 2 = 30 MARKS)**

Answer any fifteen questions from the following.

- Write down the difference of Si, Ge, and GaAs
- Explain in neat sketch the energy band diagram of p-n junction.
- Explain the characteristics and equivalent model representation ideal diode
- What are the applications of diode and in neat sketch diagram explain the concept of si diode clipping of input of 5v peak to peak to at positive 2v.
- Derive the ripple factor of half wave rectifier.
- Explain the output characteristics of CE configuration with neat sketch.
- Derive the relationship between α , β , γ ?
- Define modulation and mention the basic types of modulation?
- Why BJT is called so current controlled device ?
- State and explain about zener diode ?
- Sketch the symbol of P-channel D-MOSFET ?
- What is the difference between analog and digital signal?
- Find out the 1's and 2's complement of the binary number $(1011101101)_2$?
- Simplify the given Boolean expression ?
 $Y = (A'B + A'B'C)'$
- Bring the differences between BJT and FET ?
- A Lissajous pattern on a CRO has 5 horizontal tangencies & 2 vertical tangencies. The frequency of horizontal input is 1Khz. What is the frequency of vertical input?
- Write down the differences between clipper and clamper circuit .

18. Write down the expressions for depletion width in forward biasing and Reverse biasing of PN junction diode .
19. What is Shockley's equation ?
20. Draw the circuit diagram for Sweep generator .

PART-C

(6 x 5 = 30 MARKS)

Section-i

Answer any Six questions


1. Derive the output current and output voltage expressions of FWR ?
2. Explain with suitable diagram the working operation of transistor act as an amplifier ?
3. Explain the PN junction under biasing.
4. Explain the construction of n-channel D-MOSFET ?
5. Find out the maxterms from the function below?
 $F(W,X,Y,Z) = (X'+Z')(W+Y)$
6. Write the short notes on transistor act as a switch ?
7. Convert the following expressions to POS form:
 $A + AB + \overline{AC}$ ii) $AB + B\overline{C} + \overline{AC}$
8. Describe the operation of any one of Full wave rectifier with the current flow direction .

Section-ii


Answer any Two questions

(2 x 15 = 30 MARKS)

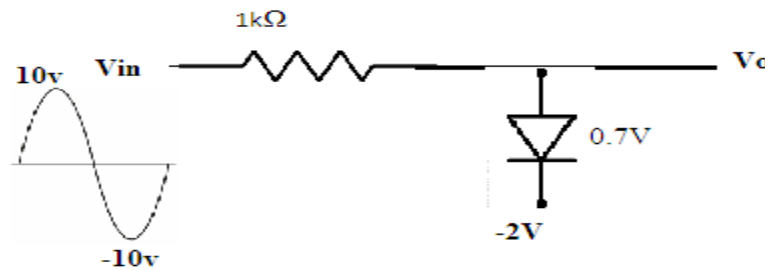1. What is the need of adder circuit and Explain the Half adder and Full adder circuit with minimum number of logic gates?
2. A bridge type FWR uses four diodes with internal resistance of each diode is (R_f) of 100 ohms if input AC signal is 220v RMS and load resistance of 1kilo ohms and the turn ratio is 9:1 .Determine
 (i) I_M, I_{DC}, I_{RMS} (ii) PIV (iii) V_{DC}, V_{AC}
 (iv) Form factor, (v) P_{OUT}, P_{IN} (vi) Efficiency
3. Determine the output voltage for the following diagrams:i)



And ii)

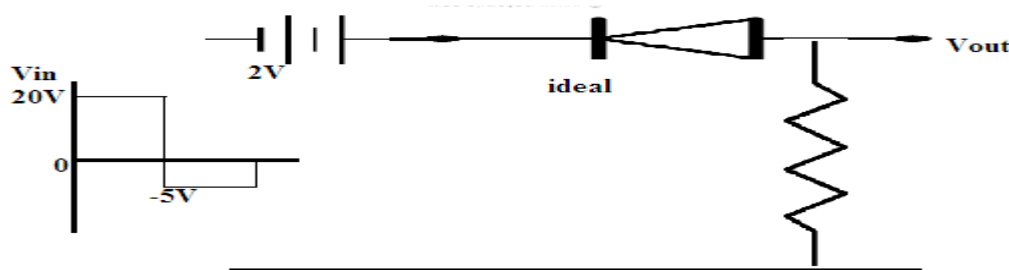

4. What is standard form of Boolean expression? If the Boolean expression is represented as $F(P,Q,R,S) = P'QR + RS + Q'R'$, Find out the standard POS form of the expression?