

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech
PEEI5404

8th Semester Regular / Back Examination 2016-17

ANALOG VLSI DESIGN

BRANCH(S):CSE, IT, ITE

Time: 3 Hours

Max Marks: 70

Q.CODE:Z398

**Answer Question No.1 which is compulsory and any five from the rest.
The figures in the right hand margin indicate marks.**

- Q1 Answer the following questions: (2 x 10)**
- a) With the aid of a diagram show the various Levels of Abstraction.
 - b) Draw the circuit of the Common Source Stage with its small signal equivalent.
 - c) How can the gain of a Common Source stage be maximized?
 - d) Draw the circuit configuration and the input output characteristics of a Common Source stage with a diode connected load.
 - e) Mention one advantage and one drawback of the CS Stage with Triode Load?
 - f) What is the shielding property?
 - g) What is a folded cascode?
 - h) Draw a basic differential pair. Mention some of its use.
 - i) What is a Gilbert Cell? Mention its use.
 - j) Draw a Common Gate stage at high frequency and mention one important property of the same.
- Q2 a) Discuss the effect of Loading in two port networks. (8)**
b) The output resistance increase due to use of source degeneration? Explain. (2)
- Q3 a) Draw the equivalent circuit for the Colpitts Oscillator topology. Calculate the voltage gain of the same. (3)**
b) What is a VCO? What are the important parameters of VCO? (7)
- Q4 Calculate the input and output impedance of a Source Follower. (10)**
- Q5 a) Define PSRR. Calculate the PSRR for the given circuit in Figure Q5 (a). (5)**

 


Figure Q5 (a)

b) Discuss the effect of Slewing in OPAMPs. (5)

Q6 a) Find the voltage gain of the common-source amplifier of Figure Q6 (a) with $V_{DD} = 5V$, $R_D = 5k\Omega$, $k' = \mu_n C_{ox} = 100 \mu A/V^2$, $W = 50 \mu m$, $L = 1 \mu m$, $V_{Tn} = 0.8V$, $L_d = 0$, $X_d = 0$, and $\lambda = 0$. Assume that the bias value of V_i is 1 V. (5)

 


Figure Q6 (a)

b) For the given circuit in Figure Q6 (b), calculate the g_m and A_v . Also draw its small signal equivalent model. (5)

 


Figure Q6 (b)

Q7 What is the objective of Reference generation? What are the different (10)

design issues in Bandgap Reference?

Q8 Write short answer on any TWO: (5 x 2)

- Common-Source Stage with Resistive Load
- Differential Pair with MOS Loads
- Different types of Amplifier Configurations
- LC Oscillator and Ring Oscillator