

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech
PEEI5404

8th Semester Regular / Back Examination 2016-17

ANALOG VLSI DESIGN

BRANCH(S):ECE, ETC

Time: 3 Hours

Max Marks: 70

Q.CODE: Z265

**Answer Question No.1 which is compulsory and any five from the rest.
The figures in the right hand margin indicate marks.**

Q1 Answer the following questions: (2 x 10)

- a) What is the need for Amplification in Analog Circuit design?
- b) What do you mean by **Common Source** in Common Source Amplifier?
- c) Write the expression of the output of a Common Source Stage when the transistor goes into the deep triode region. Also give the gain of such an arrangement.
- d) Draw the circuit configuration of a CS stage with current- source load? Where do this circuit find their applications?
- e) What type of circuit can you see in Figure Q1 (e)?

 


Figure Q1 (e)

- f) How important is common mode to differential conversion?
 - g) What is a Variable Gain Amplifier? Mention its use.
 - h) Differential between a transimpedance and a transconductance amplifier.
 - i) What is a “diode connected” device? Draw the small signal equivalent circuit for a diode connected NMOS device.
 - j) Mention some drawbacks of a simple one stage OPAMP topology.
- Q2 a) For a CS stage with source degeneration derive the voltage gain, equivalent transconductance of the circuit under both large and small signal conditions. (8)**
- b) Does the output resistance increase or decrease due to use of source degeneration for (a)? (2)**
- Q3 a) Define a VCO with proper illustrations. (3)**
- b) A VCO senses a small sinusoidal control voltage $V_{cont} = V_m \cos \omega_m t$. Determine the output waveform and its spectrum. (7)**
- Q4 Discuss different Feedback topologies. (10)**
- Q5 a) For the given circuit in Figure Q5 (a) calculate the transfer function with $\lambda=0$ and explain why Miller effect vanishes as C_{DB} increases (5)**

 


Figure Q5 (a)

- b) Compute the transfer function of the common gate stage with parasitic capacitance in the following circuit in Figure Q5 (b). Neglect channel length modulation. (5)

 


Figure Q5 (b)

- Q6 a) Mention some useful properties of differential signalling. Give a modification that can resolve the issues faced by the simple differential circuit shown in Figure Q6 (a). (5)

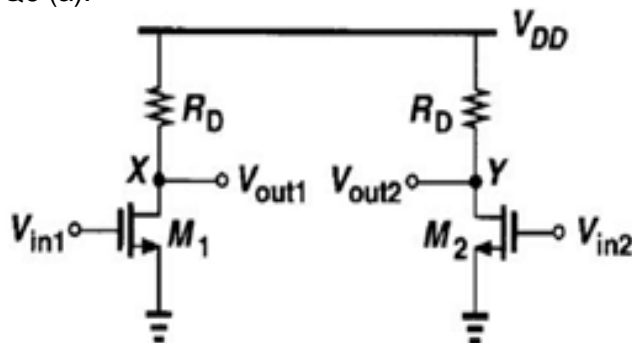


Figure Q6 (a)

- b) Discuss the Differential pair operation with MOS loads. (5)
- Q7 What is a Source Follower? Discuss about its input output characteristics and also derive its small signal gain. (10)
- Q8 Write short answer on any TWO: (5 x 2)
- Active Current Mirrors
 - CS Stage with Source Degeneration
 - Temperature-Independent References
 - Slew Rate and Power Supply Rejection in OPAMP