

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech
PEEI5404

8th Semester Regular / Back Examination 2016-17

ANALOG VLSI DESIGN

BRANCH(S): AEIE, BIOMED, EIE, IEE

Time: 3 Hours

Max Marks: 70

Q.CODE: Z144

**Answer Question No.1 which is compulsory and any five from the rest.
The figures in the right hand margin indicate marks.**

- Q1 Answer the following questions: (2 x 10)**
- a) What is the importance of level of abstraction in Analog VLSI Design?
 - b) What aspects of the performance of an amplifier are important?
 - c) Write the expression of the output of a Common Source Stage when the transistor goes into (i) triode region and (ii) saturation region.
 - d) What is a Diode-connected NMOS? Mention some of its properties.
 - e) Mention the drawbacks of a Source Follower.
 - f) What is a cascode topology? Draw a basic configuration.
 - g) Differentiate between single ended and differential ended signals. Which is better?
 - h) Why Gilbert Cell can work as an Analog Voltage Multiplier?
 - i) What is a current mirror? Why is it called so?
 - j) Enlist different Feedback topologies.
- Q2 a) Differential between a transimpedance and a transconductance amplifier. (2)**
b) For a differential pair with MOS connected load calculate the small signal voltage gain. What is the major drawback of this topology? Give one method to alleviate the same. (8)
- Q3 a) For large value of load resistance, R_D the effect of channel length modulation in the common source stage increases. How? (5)**
b) Explain the linear behaviour of a Common Source stage with a diode connected load. (5)
- Q4 a) For the given circuit in Figure Q4 (a), calculate the g_m and A_v . Also draw its small signal equivalent model. (5)**

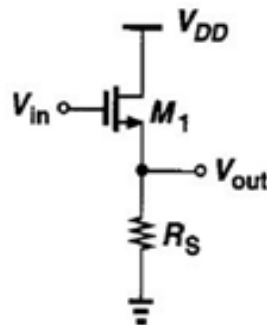


Figure Q4 (a)

- b) Suppose in the Source Follower circuit given in Figure Q4 (b) $\left(\frac{W}{L}\right)_1 =$ (5)
 $\frac{10}{0.5}$, $I_1 = 100 \mu A$, $V_{TH0} = 0.9 V$, $2\phi_F = 0.7 V$, $\mu_n C_{ox} = \frac{50 \mu A}{V^2}$ and $\gamma = 0.3 V^2$.
 Calculate V_{out} for $V_{in} = 1.5 V$. If I_1 is implemented as M_2 as seen in Figure Q4 (c), find the minimum value of $\left(\frac{W}{L}\right)_2$ for which M_2 remains in saturation.

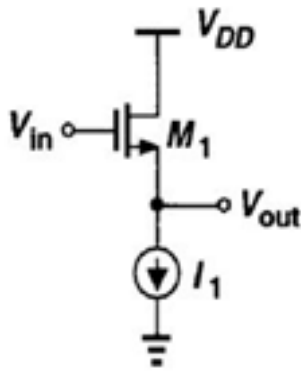


Figure Q4 (b)

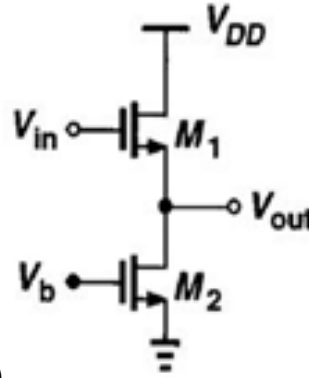


Figure Q4(c)

- Q5 a) For the Differential Pair with Current Source Load shown in Figure Q5 calculate G_m and R_{out} . (5)

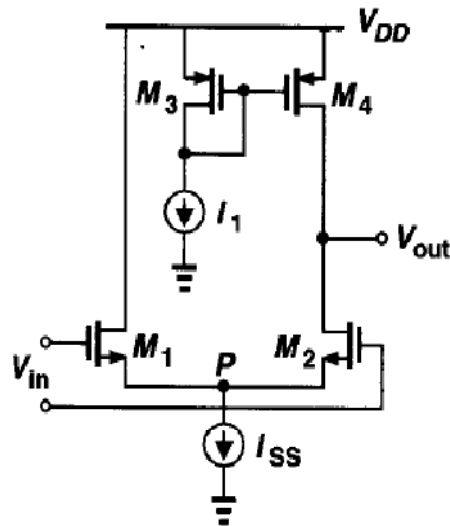


Figure Q5

- b) Calculate V_{out}/V_{in} for the above circuit in Figure Q5. (5)
- Q6 a) What are the properties of Feedback circuit? (5)
 b) Discuss the effect of Loading in Voltage-Voltage Feedback. (5)
- Q7 Discuss the performance parameters of OPAMP. (10)
- Q8 Write short answer on any TWO: (5 x 2)
 a) Band gap Reference
 b) Voltage-Controlled Oscillators
 c) Cascode Current Mirrors
 d) Miller Effect