

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech
BE2101

1st Semester Back Examination 2016-17
BASIC ELECTRONICS

BRANCH: ALL

Time: 3 Hours


Max Marks: 70

Q.CODE: Y513

Answer Question No.1 which is compulsory and any five from the rest.
The figures in the right hand margin indicate marks.

Q1 **Answer the following questions:** **(2 x 10)**

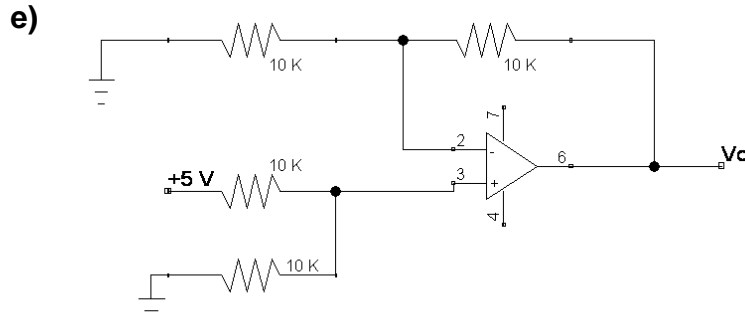- a) What do you mean by barrier potential across a P-N junction?
- b) Discuss the advantages of negative feedback.
- c) Differentiate between β_{ac} and β_{dc} .
- d) Explain virtual ground concept in OPAMP.




Find the output voltage V_o . Assume $\pm V_{sat} = \pm 12\text{ V}$ for Op-amp.

- f) Perform the following subtraction using 2's complement method
 $(18)_{10} - (29)_{10}$
- g) What is the difference between a latch and a flip flop?
- h) Mention the Barkhausen criteria of oscillation.
- i) A Lissajous pattern on a CRO has six horizontal tangencies and two vertical tangencies. The frequency of the horizontal input waveform is 3 KHz. Find the frequency of the vertical input waveform.
- j) Define noise margin of an inverter.

Q2 **What is base width modulation effect?** **(2+8)**

Mention its consequence on the input and output characteristics of common base and common emitter configuration.

Q3 a)

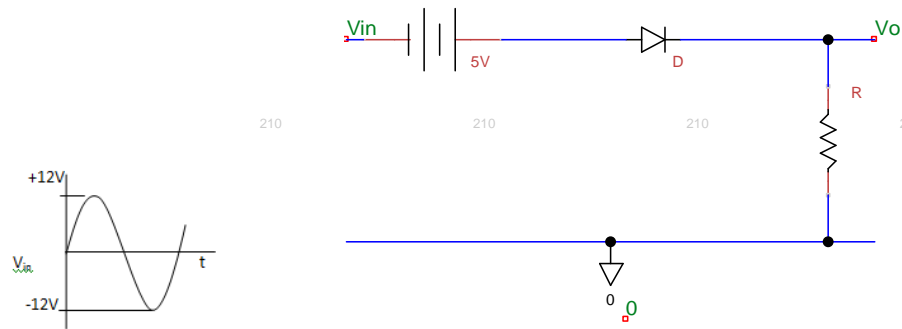

(5)

Draw the output waveform V_o for the clipper circuit shown in the figure. Assume the diode to be ideal one.

b) What is the need of biasing in a transistor amplifier? Draw and explain the circuit of a voltage divider bias CE amplifier. (5)

Q4 a) Implement the following function using NAND gates only. (5)
 $F(A,B,C,D) = A\bar{B} + \bar{A}B$

b) Implement the following function using multiplexor. (5)
 $F(A,B,C) = \sum m(1,4,6,7)$

Q5 a) Draw and explain a basic integrator circuit using op-amp. What are its limitations and these are overcome? (5)

b) What is CMRR in an op-amp? What is its significance? (5)
The CMRR of an op-amp is 80 dB and the common mode gain is 0.5. Find the differential mode gain of the op-amp.

Q6 a) Explain how input impedance, output impedance, voltage gain and bandwidth changes when negative feedback is used in the amplifier circuit. (5)

b) A common emitter amplifier has a mid band frequency of 300. The upper and lower 3 dB frequency of the amplifier is 20KHz and 100 Hz respectively. A negative feedback of 10% is applied to the amplifier circuit. Find the new gain and bandwidth after feedback. (5)

Q7 With the help of block diagram showing essential components explain the working of CRO. (10)

Q8 Write short answer on any TWO: (5 x 2)

- Zener breakdown
- Instrumentation amplifier
- Differentiate between static and dynamic RAM.
- RC phase shift oscillator