

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech.  
PCEE4204

**3<sup>rd</sup> Semester Back Examination 2017-18**  
**ELECTRICAL AND ELECTRONICS MEASUREMENT**  
**BRANCH : AEIE, ECE, EIE, ETC, IEE, EEE, ELECTRICAL**

**Time: 3 Hours**

**Max Marks: 70**

**Q.CODE: B722**

**Answer Question No.1 which is compulsory and any five from the rest.**

**The figures in the right hand margin indicate marks.**

**Q1 Answer the following questions: (2 x 10)**

- What do you understand by accuracy and precision of measurement.
- Why an ammeter should have a low resistance value?
- Why in D'Arsonval galvanometer, an iron core is usually used between the permanent magnet pole faces?
- How compensation for static friction is provided in an induction type energy meter?
- Why the secondary of a CT is never left open circuited.
- How the errors in current transformers can be reduced while designing?
- Explain why a true rms reading voltmeter uses two thermocouples.
- The deflection of an electron beam on a CRT screen is 10mm. Suppose the pre-accelerating anode voltage is halved and the potential between deflecting plates is doubled. Find the deflection of the electron beam in mm.
- Why Maxwell Bridge is limited to the measurement of medium – Q coils?
- What do you mean by “standardisation” in slide wire potentiometer?

**Q2 a) Derive the equation of balance of a Schering Bridge. Draw the phasor diagram under null conditions and explain how loss angle of capacitor can be calculated. (5)**

**b) The circuit for measurement of effective resistance and self-inductance of an iron cored coil is as follows: arm  $ab$ , the unknown impedance; arm  $bc$ , a pure resistance  $R_3$ ; arm  $cd$ , a lossless capacitor  $C_2$ ; arm  $da$ , a capacitor  $C_1$  in series with a resistance. Under balance conditions:  $R_3=10\ \Omega$ ,  $R_2=842\ \Omega$ ,  $C_2=0.135\ \mu\text{F}$  and  $C_1=1\ \mu\text{F}$ . (5)**

Calculate the value of effective resistance and self-inductance at a supply frequency of 100 Hz. Derive the equations of balance and draw the phasor diagram under balanced condition.

**Q3 a) Describe the construction & working of a ballistic galvanometer. Explain the different in constructional details of a ballistic galvanometer & a D'Arsonval galvanometer. (5)**

**b) In a dynamometer wattmeter the moving coil has 500 turns of mean diameter 3cm. Estimate the torque if the axis of the field & the moving coils are at (i)  $60^\circ$  (ii)  $90^\circ$  when the density in the field coil is  $15\ \text{mWb/m}^2$ , the current in the moving coil is 0.5A and the power being measured has a power factor of 0.866. (5)**

**Q4 a) Explain the term standardisation of a potentiometer. Describe the procedure of standardization of a d.c. potentiometer. (5)**

**b) The following readings were obtained during the measurement of a low resistance using a potentiometer. (5)**

Voltage drop across a  $0.1\ \Omega$  standard resistance = 1.0235V

Voltage drop across the low resistance under test = 0.4221V

Calculate the value of unknown resistance, current and power lost in it.

- Q5** a) A potential transformer , ratio 1000/100 volt, has the following constants: (5)  
Primary resistance= 94.5Ω, secondary resistance=0.86Ω,primary reactance=66.2 Ω, Total equivalent reactance referred to primary side=110Ω,no load current=0.02 A at 0.4 power factor.  
Calculate:(i) phase angle error at no load (ii) burden in VA at unity power factor at which the phase angle will be zero.
- b) Draw the phasor diagram of a CT & discuss the effect of variation of power factor of the secondary burden upon the performance. (5)
- Q6** a) Describe briefly with neat sketches about true r.m.s reading voltmeter. (5)  
b) In a CRT, the anode to cathode voltage is 2000 V. The parallel deflector plates are 1.5 cm long and spaced 5 mm. The screen is 50 cm from the centre of the deflection plates. Find the following (i) The beam speed (ii) The deflection sensitivity of the tube. (5)
- Q7** a) With suitable block diagram, explain the working of Basic spectrum Analyzer. (5)  
b) A PMMC instrument has a coil of dimensions 15mm X 12mm. The flux density in the air gap is  $1.8 \times 10^{-3} \text{ wb/m}^2$  and spring constant is  $0.14 \times 10^{-16} \text{ N-m/rad}$ . Determine the number of turns required to produce angular deflection of  $90^\circ$  when 5A current is flowing the coil. (5)
- Q8** Write short answer on any TWO: (5 x 2)  
a) Kelvin's double bridge  
b) Power factor meter  
c) Frequency Counters  
d) Mutual inductance method for testing of CT