

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech.
PEL31102

3rd Semester Regular / Back Examination 2017-18

ANALOG ELECTRONIC CIRCUITS

BRANCH: EEE

Time: 3 Hours

Max Marks: 100

Q.CODE: B779

**Answer Question No.1 and 2 which are compulsory and any four from the rest.
The figures in the right hand margin indicate marks.**

Q1 Answer the following questions: *multiple type or dash fill up type* (2 x 10)

- a) In a common emitter, unbypassed resistor provides
- Voltage shunt feedback
 - Current series feedback
 - Negative voltage feedback
 - Positive current feedback
- b) A CC amplifier has the highest
- Voltage gain
 - Power gain
 - Current gain
 - Output impedance
- c) The effective channel length of a MOSFET in a saturation decreases with increase in:
- Gate voltage
 - Drain voltage
 - Source voltage
 - Body voltage
- d) The ideal OP-AMP has the following characteristics:
- $R_i = \infty, A = \infty, R_o = 0$
 - $R_i = 0, A = \infty, R_o = 0$
 - $R_i = \infty, A = \infty, R_o = \infty$
 - $R_i = 0, A = \infty, R_o = \infty$
- e) If the feedback signal is returned to the input in series with the applied voltage, input impedance:
- Decreases
 - Increases
 - Does not change
 - Becomes infinity
- f) The maximum possible collector circuit efficiency of an ideal class power amplifier is:
- 15%
 - 25%
 - 50%
 - 75%
- g) The 'slew rate' of an operational amplifier indicates:
- how fast its output current can change
 - how fast its output impedance can change
 - how fast its output power can change
 - how fast its output voltage can change
- h) The large signal bandwidth of an op-amp is limited by:
- loop gain
 - slew rate
 - output impedance
 - input frequency
- i) The feedback factor β at the frequency of oscillation of a Wien bridge oscillator is:

- a) 3
b) 1/3
c) 1/29
d) 3/29
- j) The only drawback of using negative feedback in amplifiers is that it involves:
a) Gain sacrifice
b) Gain stability
c) Temperature sensitivity
d) Frequency dependence
- Q2 Answer the following questions: Short answer type (2 x 10)**
- Differentiate between BJT and FET.
 - Calculate β for two transistors for which $\alpha = 0.99$ and 0.98 . For collector current of 10 mA , find the base current of each transistor.
 - Discuss about load line in BJT biasing circuit.
 - Among the various biasing circuits which one is commonly used and why.
 - Discuss about the series and parallel configurations of semiconductors diodes.
 - Whether the output of a CE configuration is in phase or out of phase with the input? Justify.
 - Differentiate between small-signal amplifier and large-signal amplifier.
 - What is the role of bypass capacitor in an amplifier circuit?
 - What are the advantages and disadvantages of negative feedback in an amplifier?
 - State and explain Barkhausen criteria of self oscillation.
- Q3**
- Explain the effect of coupling capacitor and bypass capacitor on the low frequency response of BJT amplifier. **(10)**
 - Compare the properties of CB, CE, CC configurations of BJT and explain which configuration is suitable for use in cascade amplifier stages. Justify your answer. **(5)**
- Q4**
- Determine the lower cut-off frequency for the voltage divider bias BJT amplifier with $C_S = 10\mu\text{F}$, $C_E = 20\mu\text{F}$, $R_S = 1\text{K}\Omega$, $R_1 = 10\text{K}\Omega$, $R_2 = 10\text{K}\Omega$, $R_E = 2\text{K}\Omega$, $R_C = 4\text{K}\Omega$, $R_L = 2.2\text{K}\Omega$, $\beta = 100$, $r_o = \infty$, $V_{CC} = 20\text{V}$. **(10)**
 - Draw and explain the principle of operation of an emitter follower circuit. Justify its name. Derive expressions for its input and output impedances and the voltage gain **(5)**
- Q5**
- Describe the Hybrid parameters of a BJT and hence develop the Hybrid model and the simplified Hybrid model of the transistor. **(10)**
 - A BJT used in CE configuration with following parameters: $R_L = 10\text{K}\Omega$, $R_S = 2\text{K}\Omega$, $h_{ie} = 1\text{K}\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 50$ and $h_{oe} = 25\mu$. Calculate the values of A_i , R_i , A_v , A_{vs} and Z_o . **(5)**
- Q6**
- For voltage series feedback amplifier topology, obtain expression for A_v and R_{if} . Also explain the principle of voltage amplifier used in feedback amplifiers. **(10)**
 - Sometimes an amplifier using negative feedback oscillates. Give reason for its oscillation. **(5)**
- Q7**
- Obtain an expression for frequency of oscillation in Colpitt's Oscillator. **(10)**
 - Explain the concept of positive feedback used in oscillator. **(5)**
- Q8**
- Draw the JFET common drain configuration(source-follower) circuit. Derive Z_i , Z_o , A_v , using small signal model. Write its characteristics. **(10)**
 - Explain the structure of depletion mode MOSFET. **(5)**
- Q9**
- What do you mean by power amplifier? Draw circuit diagram of push pull amplifier using a pair of complementary transistors and explain its operation. **(10)**
 - Explain comparator Circuit with neat diagram. **(5)**