

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
BE 2102

First Semester Back Examination – 2014

BASIC ELECTRICAL ENGINEERING

BRANCH(S) : AEIE, AERO, AUTO, BIOTECH, CHEM, CIVIL, CSE, EC, EEE, EIE, ELECTRICAL, ENV, ETC, FASHION, FAT, IEE, IT, MANUFACT, MANUTECH, MECH, MINERAL, MINING, MM, MME, PLASTIC, TEXTILE

QUESTION CODE : L 354

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any five from the rest.

The figures in the right-hand margin indicate marks.



1. Answer the following questions :

2 × 10

- Define a controlled current source.
- What is r.m.s value of a AC waveform ?
- What do you understand by coercivity ?
- Explain the significance of Power Factor.
- What is the time constant of a RC circuit having $R = 10 \Omega$ and $C = 0.3F$?
- Two resistances of 10Ω , 15Ω are connected in parallel and this combination is connected across a 210V supply DC source. Find the current flowing in 15Ω resistor.
- Describe various losses occurring in a DC machine.
- A 3 phase, 4 pole, 50Hz, 440 V induction motor runs at 1440 rpm. What is the slip speed and slip ?
- Discuss the disadvantages of noise signals.
- What do you understand by rotating magnetic field ?

P.T.O.

2. (a) A series circuit has $R=10\Omega$, $L=50\text{mH}$, and $C=100\mu\text{F}$ and is supplied with 200V, 50Hz AC supply Find 5

- (a) Impedance of the circuit ?
 (b) Total Current and power factor of the circuit ?
 (c) Active power consumed ?

- (b) Using Super position theorem find the voltage V_x across 4Ω resistor as shown in Fig (1). 5

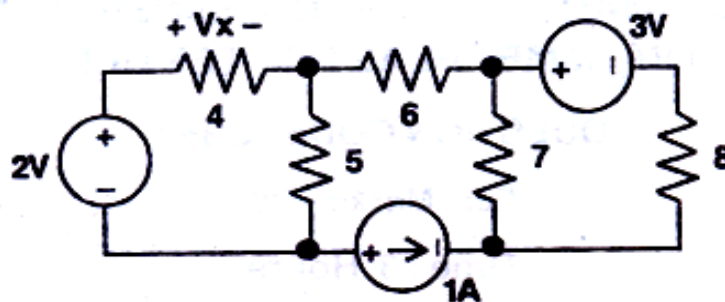


Fig (1)

3. (a) An iron ring with mean length of magnetic path of 30cm and of small cross section has an air gap of 2mm. It is wound uniformly with a coil of 660 turns. A current of 2 amp in the coil produces flux density of $24\pi \text{ mWb/m}^2$. Calculate the relative permeability of iron.

(Assume $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$) 5

- (b) Explain the characteristics of Open and Short circuit in electrical network by drawing a circuit diagram. 5

4. (a) Three equal impedances are star connected to a 3 phase, 440 V 50 Hz supply. If the inductive reactance and resistance of each branch are 8Ω and 6Ω respectively Find the 5

- (a) Impedance of each phase ?
 (b) Line current ?
 (c) Active power consumed ?

- (b) What is complex power, apparent power, real power and reactive power in a single phase AC circuit ? Explain by drawing power triangle. 5

5. (a) A capacitor is charged from a DC supply of 200V through a resistor in series having a resistance of $100\ \Omega$. If the time constant for the given set up is 15ms, Calculate the value of the capacitance. Also calculate the time requirement for the capacitor to acquire 85% of the steady state charge assuming zero initial charge on the capacitor. 5
- (b) A 6 pole DC shunt motor the flux per pole is 8 mWb. There are 96 conductors lap connected. Find out the back emf developed in the motor if the armature rotates at a speed of 25 revolutions / second. 5
6. (a) Derive the e.m.f equation of single phase two winding transformer from first principle. 5
- (b) A 50 Hz, 4-pole, 3-phase induction motor has a rotor current of frequency 2 Hz. Determine 5
- (a) the slip ?
- (b) Speed of the motor ?
7. (a) What is a thermocouple ? How the temperature measurement can be done by it ? 5
- (b) What is a transducer ? Explain its working by giving a suitable example. 5
8. Answer any **two** of the following : 5 x 2
- (a) Maximum Power Transfer theorem
- (b) AC power distribution network
- (c) Principle of operation of 3 phase induction motor.

