

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
BE 2101

First Semester Back Examination – 2014

BASIC ELECTRONICS

BRANCH(S) : AEIE, AERO, AUTO, BIOTECH, CHEM, CIVIL, CSE, EC, EEE, EIE, ELECTRICAL, ETC, FAT, IEE, IT, MANUFACT, MANUTECH, MECH, MINING, MM, MME, PLASTIC, TEXTILE

QUESTION CODE : L 351

Full Marks – 70

Time – 3 Hours

*Answer Question No. 1 which is compulsory and any five from the rest.
The figures in the right-hand margin indicate marks.*



1. Answer the following questions :

2 × 10

- What diffusion theorem is in related with PN junction ?
- How transistors act as switch ? Justify.
- What is clipping in signal ? Draw a simple diode clipper.
- What is bandwidth of an amplifier ? How bandwidth of an amplifier can be increased ?
- Mention two conditions that must be fulfilled in an amplifier for self sustained oscillation.
- What is the ideal impedance of a voltage amplifier ? Justify.
- Give four characteristics of a cathode ray oscilloscope.
- What should be the radix of the numbers used in the following addition ?

$$11 \times 12 = 66$$

P.T.O.

- (i) What is the difference between combinational and sequential circuits ?
- (j) Which logic circuits is called as data selector circuits and why ?
2. Derive the expression for ripple factor of a half wave rectifier circuits. 10
3. (a) Explain CB, CE and CC connection of transistor amplifier. Discuss their merits and demerits. 5
- (b) (i) What happens when peak amplitude of the signal is greater than DC Biasing voltage of transistor ? Explain with necessary diagram.
- (ii) Draw a transistor amplifier circuit used as switch and explain. 5
4. (a) Explain the frequency response of an single stage transistor amplifier. 3+3
- (b) Derive the voltage gain, input impedance of a CE transistor amplifier. Use simplified hybrid model. 4
5. (a) Draw and find the transfer function of OPAMP based integrator circuit. Also draw the output wave form when a 2 V peak to peak square wave voltage is given. 5
- (b) Derive the gain expression of an amplifier when -ve feedback is used State the assumptions you used. 5
6. (a) What is a full adder circuits. With logic gates, construct a full adder circuit. Also find its characteristics equation and truth table. 5
- (b) Implement the following function using NAND gate only : 5
- $$F(A,B,C,D) = (A + C)(B + D)$$
7. (a) Explain the principle of 4-bit binary counter. 5
- (b) Simplify the following Boolean function using K-maps 5
- $$F(A, B, C, D) = \sum m(0, 2, 4, 7, 8, 9).$$
- And then, realize the simplified functions using logic gates.

8. Write short notes on any **two** of the following :

5×2

- (a) Universal logic gates
- (b) Principle of oscillator
- (c) Emitter follower circuits
- (d) Instrumentation amplifier.


