

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech  
BENG 1102

First Year Special Examination – 2014

**BASIC ELECTRICAL ENGINEERING**

**BRANCH(S) : AEIE, BIOTECH, CSE, EC, EEE,  
ELECTRICAL, IEE, IT**

**QUESTION CODE : G 510**

**Full Marks – 70**

**Time : 3 Hours**

*Answer Question No. 1 which is compulsory and any five from the rest.  
The figures in the right-hand margin indicate marks.*



1. Answer the following questions : 2 × 10
- Write down the equation of a sinusoidal source voltage of 40 Hz frequency having a RMS value of 240 V.
  - A  $5 \Omega$  resistor is connected across a Potential difference of 30 V. Calculate the power dissipated in the resistor.
  - Explain briefly the term MMF.
  - What is Form Factor ?
  - What do you understand by resonance in AC circuit ?
  - Write down the principle of DC Generator.
  - A three phase balanced load supplied from 440 V, 50 Hz supply takes a current of 20 A and draws a power of 10 KW. What is the p.f. of the circuit ?
  - What do you mean by 'slip' of a three phase induction motor ?
  - What is the relation between phase and line current in three phase star connected circuit ?
  - What are the conventional ways of electrical power generation ?

P.T.O.

2. (a) Explain the terms 'effective value' and 'average value' for a sinusoidal alternating quantity. 5
- (b) Find the equivalent resistance of the circuit shown below in Fig (1) also. Find out the current flowing in the  $3\ \Omega$  resistor. 5


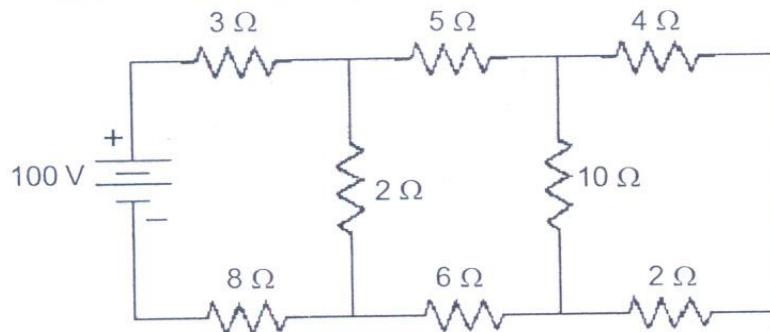


Fig. (1)

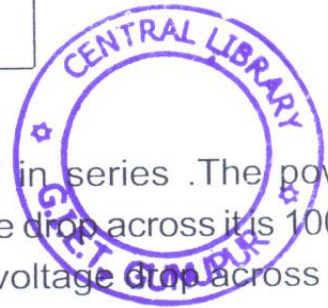

3. (a) A circuit consists of pure resistance and a coil in series. The power dissipated in the resistance is 600 W and voltage drop across it is 100 V. The power dissipated in the coil is 200 W and voltage drop across it is 60 V. Determine the resistance and reactance of the coil and also the supply voltage. 5
- (b) An iron ring with mean length of magnetic path of 30cm and of small cross section has an air gap of 2mm. It is wound uniformly with a coil of 660 turns. A current of 2 amp in the coil produces flux density of  $24\ \pi\ \text{m Wb/m}^2$ , calculate the relative permeability of iron. 5
4. (a) A capacitor with capacitance of  $500\ \mu\text{F}$  and a resistance of  $100\ \Omega$  is suddenly switched across a 30 V DC supply of negligible internal resistance. Determine the initial and final currents, time constant of the circuit and instantaneous value of voltage across the capacitor after 500 ms. 5
- (b) State and Explain Thevenin's Theorem by giving a suitable example. 5
5. (a) A DC shunt motor rotating at 1500 rpm is fed by 220V DC source. The line current drawn by the motor is 22 A and the shunt field resistance is  $100\ \Omega$ . Find :  
 (i) Back emf  
 (ii) Mechanical power  
 (iii) Torque developed.  
 Assuming that armature resistance is  $0.1\ \Omega$ . 5
- (b) State the merits and demerits of Moving iron instruments. 5

6. (a) Briefly explain the EMF equation of a single phase transformer. 5  
(b) The Primary of a single phase transformer is connected to a 220 V, 50 Hz supply. If the peak flux in the core is 20 m Wb, what is the no. of turns in the Primary ? How many no of turns are required in the secondary to obtain a voltage of 110 V ? 5
7. (a) Compare between the operation of hydel power plant and nuclear power plant. 5  
(b) Write down various industrial uses of electricity. Also calculate the resistance of the heating element of a heater of rating 1500 W and 250 V. 5
8. Write short notes on any **two** : 5×2  
(a) Complex Power  
(b) Transmission and Distribution of electric energy  
(c) Single Phase Induction Motor

