

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
BE 2101

First Semester Regular Examination – 2014

BASIC ELECTRONICS

BRANCH : B. TECH

QUESTION CODE : H 455

Full Marks – 70

Time : 3 Hours



*Answer Question No. 1 which is compulsory and any five from the rest.
The figures in the right-hand margin indicate marks.*

1. Answer the following questions : 2 × 10
- (a) What is dynamic resistance (R_d) of a diode? How R_d is related with diode forward current ?
 - (b) Can a transistor be used as clipper circuit ? Justify.
 - (c) What is bandwidth of an amplifier ? How bandwidth of an amplifier can be increased ?
 - (d) Mention the basic four basic sections of an operational amplifier circuits.
 - (e) Mention two conditions that must be fulfilled for self sustained oscillation.
 - (f) What should be the input impedance of an electronics instrument for measuring voltage ? Justify.
 - (g) The time base voltage of a CRO is given to Y axis and the sinusoidal voltage to be measured is given to X axis. Explain the problems associated with such measurement.
 - (h) What should be the radix of the numbers used in the following addition ?

$$34 + 15 = 50$$

P.T.O.

- (i) What is the difference between combinational and sequential circuits ?
- (j) Draw the block diagram of a 8×1 MUX.
2. A sinusoidal signal $V(t) = 100 \sin(314t)$ is given to the input of a full wave bridge rectifier with a load resistor of $1.5 \text{ k}\Omega$.
- Determine
- (A) The DC output voltage available at the load if silicon diodes are used.
- (B) Determine required PW rating of each diode
- (C) the output ripple frequency
- (D) AC input and output power and efficiency 10
3. (a) With a neat block diagram explain the principle of a time base generator used in CRO. 5
- (b) With a neat block diagram explain the principle of a function generator. 5
4. (a) (i) What happens when peak amplitude of the signal is greater than DC Biasing voltage of transistor ? Explain with necessary diagram. 3
- (ii) Draw a transistor amplifier circuit used as switch and explain. 3
- (b) Derive the voltage gain, input impedance of a CE transistor amplifier. Use simplified hybrid model. 4
5. (a) What is a Differentiator circuit ? Draw and find the transfer function of OPAMP based Differentiator circuit. Also draw the output wave form when a 2V peak to peak square wave voltage is given. 5
- (b) How bandwidth, gain and distortion changes when a -ve feed back is used in the amplifier circuits ? 5
6. (a) What is MUX ? Implement the following Boolean function using 4×1 MUX.

$$F = A'B'C' + ABC + AB'C + A'BC'$$
 5
- (b) Implement the following function using NOR gate only.

$$F(A,B,C,D) = (A + C)(B + D).$$
 5

7. (a) Establish the following identities of Boolean algebra :
- (1) $A + AB = A$
 - (2) $(A + B)(A + C) = A + BC$ 5
- (b) (i) Perform the following subtraction using 1's and 2's complement method
- $(51)_{10} - (17)_{10}$ 3
- (ii) Justify, which method is best suitable for digital circuit implementation. 2
8. Write short notes on any two : 5 × 2
- (a) Demultiplexers
 - (b) RC phase shift oscillator
 - (c) Diode as Clipper
 - (d) Instrumentation amplifier.

