

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
BE 2101

First Year Special Examination – 2014

BASIC ELECTRONICS

BRANCH(S) : AEIE, AUTO, BIOTECH, CHEM, CIVIL, CSE, EC,
EEE, ELECTRICAL, ENV, ETC, FASHION, IEE, IT, MANUFACT,
MECH, MME, PLASTIC, TEXTILE

QUESTION CODE : G 484

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.



1. Answer the following questions :

2 × 10

- Compare the merits and demerits of silicon diodes and germanium diodes.
- What is peak inverse voltage (PIV) of rectifier circuits ? What is PIV of bridge rectifier and center-tapped rectifier diode circuits ?
- What do you mean by digital logic invertors ? Mention two ICs used as digital logic invertors in electronics.
- What will appear at the screen of CRO when time base voltage is given to Y-plate and a square wave is given to X-plate ?
- What is the closed loop gain of an operational amplifier when unit gain –ve feedback is used ?
- Perform the following subtraction using 2's compliment method :

$$(47)_{16} - (68)_{10}$$

- Construct an AND gate using NOR gate.

P.T.O.

- (h) What is the difference between flip-flop and latch ?
- (i) Mention two conditions that must be fulfilled in oscillator circuits.
- (j) What is the difference between ROM and RAM ?
2. Express the necessary derivation for ripple factor of a full wave bridge silicon diode rectifier. If a $50\ \Omega$ load resistance is connected across a full wave rectifier. The input supply voltage is 230 V (rms) at 50 Hz, then find ripple factor of the circuit. 10
3. (a) Explain, how amplitude and frequency of a signal is measured using CRO ? 5
- (b) What is input impedance of an ideal CRO ? Explain CRO as voltmeter. 5
4. (a) Give comparison between common base, common emitter and common collector amplifier. Mention their applications. 5
- (b) What is α and β of a bipolar transistor. Establish the relation between them. 5
5. (a) Simplify the following Boolean function using Boolean algebra identities :

$$F(A, B, C, D) = \sum m(0, 1, 4, 5, 7, 9, 11, 12).$$
 And then, realize the simplified functions using logic gates. 5
- (b) What is POS in Boolean expressions ? Implement the following function in POS : 1+4
- $$F(A, B, C) = (AB + C)(B + AC).$$
6. (a) With a neat diagram establish the gain of a negative feedback amplifier. How distortion is effected by negative feedback in analog circuits ? 5
- (b) Explain the principle of an oscillator circuit. Mention the requirements to be filled up to built a oscillator circuit. 5
7. (a) What is an differentiator circuits circuit ? Draw and find the transfer function of OPAMP based differentiator circuit. Also draw the output wave form when a 4 V peak to peak square wave voltage is given. 5

(b) What is MUX ? Design the following Boolean function using MUX : 5

$$F = A'B'C' + ABC + AB'C + A'BC'$$

8. Write short notes on any **two** : 5×2

- (a) Full adder
- (b) Characteristic of ideal electronics instruments
- (c) Slew rate (SR) and common mode rejection ratio (CMMR) of OPAMP
- (d) Small signal analysis of transistor.

