

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 2

B. Tech  
BENG 1105

First Year Special Examination – 2014

**BASIC ELECTRONICS**

**BRANCH(S) : AEIE, BIOTECH, CSE, EC, EEE, IT**

**QUESTION CODE : G 485**

**Full Marks – 70**

**Time : 3 Hours**



Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2 × 10
- What is the significance of acceptor and donor ions in semiconductors ? How these ions effect the charge of the semiconductor ?
  - What is zenor and avalanche breakdown of diode ? Which mechanism occurs at lower voltage of application ? Justify.
  - Under what condition transistors act as a clipper circuits ?
  - What is operating point of a transistor ? How operating point effect the output collector current of transistor amplifier ?
  - What is the significance of emitter resistance of a transistor amplifier ? Why a capacitor called emitter bypass capacitor is generally connected across it ?
  - What is a binary counter ? Design a MOD-2 binary counter.
  - Why +ve feedback is called regenerative feedback ? Justify by necessary mathematical expression.
  - What is the need of carrier signal in communication system ?
  - What is CMRR ? What is its value for ideal OPAMP ?
  - What are three states in a tri-state buffer ? Mention its physical significance.

P.T.O.

2. (a) What is a diode clipper ? Explain a diode clipper circuits which will double the dc level of a input square wave signal ? Explain with necessary mathematical expression. 5
- (b) Explain the cut-off, saturation and active region of transistor. How these parameters affect the performance of a transistor ? 5
3. (a) What are emmitter follower circuits ? Draw a emitter follower circuit using FET. Derive the voltage gain of an emitter follower circuits. 5
- (b) What do you mean by logic inverter circuit ? Explain with diagram the principle operation of a C-MOS logic inverter. 5
4. (a) What are the demerits of a negative feedback amplifier ? How –ve feedback affect the bandwidth and distortion of an amplifier circuits ? 5
- (b) What is Barkhausen criterion ? How this condition is used in a oscillator ? Explain the principle of RC phase shift oscillator. 5
5. (a) Draw a substractor circuits using a single OPAMP. Derive its voltage gain in terms of resistor you have used. 6
- (b) What do you mean by modulation in communication ? Discuss the basic three modulation systems used in analog communication. 4
6. (a) Write characteristics equation and table for a full adder circuit. Then, implement the full adder with half adder and OR gates. 5
- (b) Express the following Boolean function into POS. Then realize the function using logic gate. 5
- $$F = A'B'C' + ABC + AB'C + A'BC'$$
7. (a) What are Flip-flop circuits ? Explain RS and JK flipflops. 5
- (b) What is basic principle of signal communication using optical fiber ? Explain the advantages of optical fiber communication system. 5
8. Write short notes on any **two** : 5×2
- (a) AD Converters
- (b) Demodulation
- (c) CRO
- (d) Electronics voltmeter.

