

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech.
BE2102

2nd Semester Back Examination 2017-18
BASIC ELECTRICAL ENGINEERING
BRANCH : AEIE, AERO, AUTO, BIOMED,
BIOTECH, CHEM, CIVIL, CSE, ECE, EEE, EIE, ELECTRICAL, ENV, ETC, FASHION, FAT,
IEE, IT, ITE, MANUFAC, MANUTECH, MARINE, MECH, METTA, METTAMIN, MINERAL,
MINING, MME, PE, PLASTIC, TEXTILE

Time : 3 Hours

Max Marks : 70

Q.CODE : C1173

Answer Question No.1 which is compulsory and any five from the rest.

The figures in the right hand margin indicate marks.

Answer all parts of a question at a place.

Q1 Answer the following questions:

(2 x 10)


- A resistor of 5Ω is connected across a potential difference of 50V. Calculate the power dissipated and energy transferred to heat in 2 minutes ?
- Explain the term 'Permeability' & 'coercivity' ?
- Define R.M.S value of an alternating quantity?
- Two impedances of $0.5 \angle -90^\circ$ & $3+j4 \Omega$ are connected in series .Find out the resultant impedances in polar form?
- What is back emf in a DC motor, explain?
- Find the frequency of the induced emf of an alternator having six pole rotating at 1500 rpm?
- Differentiate between active and reactive power ?
- What is the value of starting torque in case of a single phase induction motor?
- What is the relation between phase and line current in three phase star connected circuit ?
- Why the transformer core is laminated ?

Q2 a) A 50 Hz sinusoidal voltage; $V=141 \sin \omega t$ is supplied to a series R-L circuit comprising of $R =5 \text{ ohm}$, and $L=0.015 \text{ Henry}$. Calculate:

(5)

- The effective value of the steady state current as well as the relative phase angle?
- The instantaneous current (time equation) ?

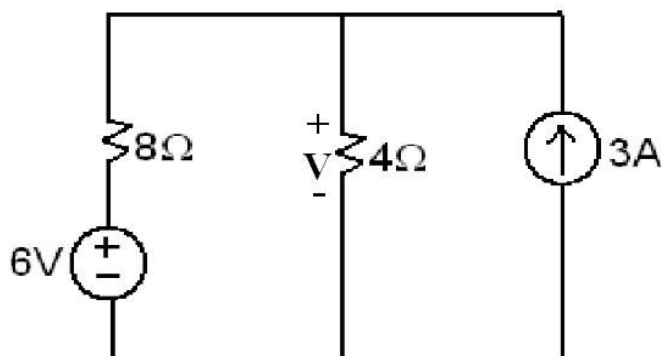- b) Using Super position theorem Find V in the circuit shown in Fig (1)? (5)



- Q3 a) State & explain Thevenin's theorem by giving a suitable example? (5)

- b) The voltage applied to a circuit is $V = 230 \sin(\omega t + 30^\circ)$ and the current through the circuit is $i = 10 \sin(\omega t - 30^\circ)$. Determine the parameter of the circuit, power consumed in the circuit and also the power factor of the circuit? (5)

- Q4 a) Draw the analogy between electric circuits & magnetic circuits? (5)

- b) An iron ring has a mean diameter of 25cm and a cross sectional area of 4cm^2 . It is wound with a coil of 1200 turns. An air gap 1.5 mm width is cut in the ring. Determine the current required in the coil to produce a flux of 0.48 m Wb in the air gap. If the relative permeability of iron is 800? (neglect magnetic leakage and fringing) (5)

Given $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

- Q5 a) An inductance of 0.5 H in series with a capacitance of $100\mu\text{F}$. Find the impedance of the circuit for the condition given below: (5)

- i. At a frequency 60Hz
- ii. At a frequency 1kHz

- b) A balanced star connected load has resistance of 10Ω & inductance of 50mH per phase is connected to a three phase supply of 440V & 50Hz. (5)

Find the

- i. Line Current.
- ii. Phase current
- iii. Power Factor.

- Q6 a) Explain in brief various losses occurred in a DC machine? (5)

- b) A 220/20V transformer has 50 turns on its low voltage side. (5)

Calculate

- i. The number of turns on the high voltage side?
- ii. The turn ratio when it is used as step down transformer?
- iii. The turn ratio when it is used as step up transformer?

- Q7 a) Name the series and shunt methods of excitation provided in DC machines? (5)

- b) Describe the Principle of alternator? Also write names of various parts Of a rotating electrical machine? (5)

- Q8 ANSWER ANY TWO : (5 x 2)

- a) Voltage sources & Current Sources
- b) Laws of magnetic circuits
- c) AC power distribution.
- d) Measurement Systems