

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 7

B. Tech.
BE 2101(N) / BENG 1105(O)

First Semester Examination – 2010

**BASIC ELECTRONICS
(New and Old Course)**

Full Marks – 70

Time : 3 Hours

*(Students are required to give their answer any one Course
according to the Syllabus)*

(NEW COURSE)


*Answer Question No. 1 which is compulsory and any **five** from the rest.*

The figures in the right-hand margin indicate marks.


1. Answer the following questions: 2×10
- (a) What do you mean by frequency spectrum ? Calculate the frequency and time period of the following sinusoidal signal.
 $f(t) = 5 \sin (500t)$
 - (b) What is Avalanche breakdown ?
 - (c) What is significance of Virtual ground in an Op-Amp ?
 - (d) Why is meant by small signal analysis of transistor?
 - (e) What is Barkhausen criterion ?
 - (f) How a waveform is displayed in a Cathode Ray Oscilloscope?
 - (g) Why Biasing is done in a Bipolar Junction transistor ?

P.T.O.

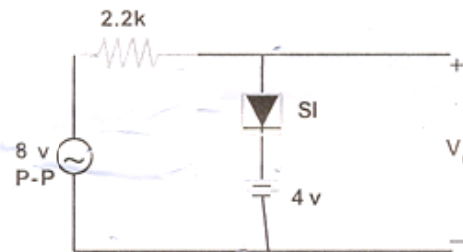- (h) Write the Truth table for a 3-input Ex-OR logic gate.
- (i) Convert the decimal number $(201.32)_{10}$ into its equivalent Binary number.
- (j) A Lissajous pattern on a CRO has 4 horizontal tangencies and 2 vertical tangencies. The frequency of horizontal input is 1 KHz. What is the frequency of the vertical input ?
2. (a) Explain the operation of a P-N Junction diode with V-I characteristics. 5
- (b) Explain how the Op-Amp can be used as a summing amplifier with a neat circuit diagram. 5
3. (a) How the transistor can be used as an amplifier in CE configuration. Explain with proper diagrams. 6
- (b) Determine the output voltage V_0 and its wave form for the following network. 4



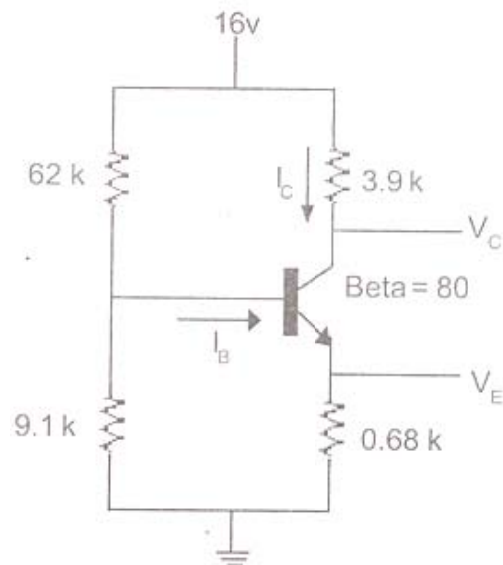4. (a) Explain the operation of a full wave rectifier with input –output waveforms. 4
- (b) Calculate I_{CQ} , V_{CEQ} , V_C , V_E for the following BJT biasing circuit. 6



- 5 (a) Draw the Block diagram of Function Generator and explain its operation. 5
- (b) What are the advantages of negative feedback? Explain the operation of Op-Amp phase shift Oscillator. 5
6. (a) Simplify the following Boolean expression and realize it using only NAND gate 5
- $ABC [AB + C' (BC + AC)]$
- (b) Convert the following SOP expression into its standard POS form and write its truth table. 5
- $A B' C + A' B' + ABC' D$
- 7 (a) Explain the operation of a full adder with its truth table and logic circuit. 7
- (b) Write and prove Demorgan's theorem. 3

- 8 (a) Classify different types of RAM's. Explain the operation of SRAM. 5
- (b) Explain the operation of S-R Latch in detail. 5
-


(OLD COURSE)

*Answer Question No. 1 which is compulsory and any **five** from the rest.*


The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2×10
- (a) Define Mobility and Conductivity.
 - (b) What is the difference between Avalanche breakdown and Zener breakdown? Which is used in voltage regulator application?
 - (c) What do you mean by frequency spectrum? Calculate the frequency and time period of the following sinusoidal signal.
 $f(t) = 5 \sin(300t)$
 - (d) What is meant by small signal analysis of a transistor?
 - (e) Explain how enhancement type MOSFET is different from depletion type MOSFET.
 - (f) Define CMRR. If the CMRR of an Op-Amp is 80dB and the common mode gain is -0.5 , what is the differential mode gain of the Op-Amp?
 - (g) What is modulation index? How it affects the performance of an AM communication system?
 - (h) What is quantization?
 - (i) Convert the Hexadecimal number $(2AB.32)_{16}$ into its equivalent Binary number.
 - (j) Why Time base is used in a Cathode Ray Oscilloscope?
2. (a) How a P-type semiconductor is formed? Explain the operation of a P-N junction under forward and reverse bias condition. 5

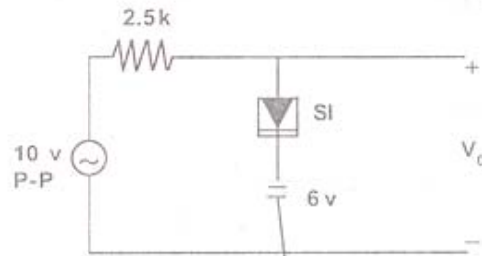- (b) Determine the output voltage V_o and its wave form for the following circuit. 5



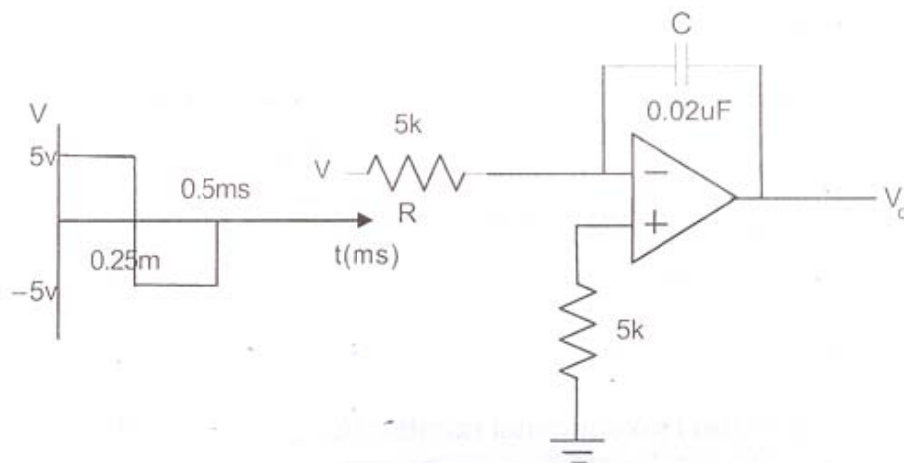3. (a) Explain how transistor is used as an amplifier in CE configuration. 5
 (b) Explain the DC analysis of Depletion type MOSFET's. 5
4. (a) Draw the CMOS- common source amplifier and explain its operation. 5
 (b) Sketch the output waveform of the following circuit for the given input waveform. 5



- 5 (a) Discuss different types of Feedbacks and write the advantages of negative Feedback. 5
 (b) Simplify the following Boolean expression and draw its logic circuit. 5
 $A'BC + AB'C' + A'B'C' + AB'C + ABC$

6. (a) Design a combinational logic circuit which adds three binary bits and implement using NAND gates. 6
- (b) An AM transmitter radiates 10kW with an unmodulated carrier and 15kW when it is amplitude modulated. Calculate the percentage of modulation. 4
- 7 (a) Explain the advantages of Fiber optic communication system over other modes of communication. 5
- (b) Describe the operation of S-R and J-K flip-flops. 5
- 8 Write short notes on any *two* of the following : 5×2
- (a) Digital Multimeter
- (b) Digital Modulation
- (c) Displaying a waveform in CRO.