

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
15BE2101

1st Semester Back Examination 2018-19

BASICS OF ELECTRONICS

BRANCH : AEIE, AERO, AUTO, BIOMED, BIOTECH, CHEM, CIVIL, CSE, ECE, EEE, EIE, ELECTRICAL, ENV, ETC, FASHION, FAT, IEE, IT, ITE, MANUFAC, MANUTECH, MARINE, MECH, METTA, METTAMIN, MINERAL, MINING, MME, PE, PLASTIC, TEXTILE

Time : 3 Hours

Max Marks : 100

Q.CODE : E949

Answer Question No.1 (Part-1) which is compulsory, any EIGHT from Part-II and any TWO from Part-III.

The figures in the right hand margin indicate marks.

Part- I


Q1 Short Answer Type Questions (Answer All-10) (2 x 10)

- What is the slew rate of OP-AMP? What is its importance?
- Is JFET is more advantageous than the BJT? Justify
- Convert decimal number 151.75 to binary.
- Calculate I_c , I_e and β_{dc} for a transistor that has $\alpha_{dc}=0.98$ and $I_B= 100\mu A$
- Define virtual ground concept of an op-amp.
- Differentiate between enhancement type MOSFET and depletion type MOSFET and write down shockley's equation
- Perform $(15)_{10}-(5)_{10}$ in binary.
- What is ripple factor ? Mention its value for full-Wave rectifier.
- Implement AND gate using NOR gates.
- Draw a binary adder using logic gates.

Part- II

 Q2 Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- What is a DC load line? Explain with a fixed bias circuit diagram. Also explain the importance of the Q-point or operating point.
- Draw the waveform V_o for $V_i= 10 \sin \omega t$, $V_B=2V$ and D_1 as silicon diode.




- Design an integrator circuit using OP-AMP.
- Draw the circuit diagram of the bridge type full-wave rectifier and explain how it works?
- Distinguish between Zener breakdown and Avalanche breakdown
- Convert the Boolean function in sum of products(SOP) form and minimize it.
 $F(A,B,C,D)=\Sigma(2,3,8,10,11,12,14,15)$
- With the help of a diagram, describe the basic structure an n- channel MOSFET. Give the biasing arrangement.
- Explain BJT as an amplifier with example.
- Write short note on CMOS.
- Determine the diode current at $20^{\circ}C$ for a silicon diode with a reverse saturation current of $50nA$ and an applied forward bias voltage of $0.6 V$.
- What is a clamper circuit? Explain a positive clamper circuit with neat diagram.
- With a neat diagram explain a voltage-Divider DC biasing circuit.

Part-III

Long Answer Type Questions (Answer Any Two out of Four)

 - Q3** a) Define I_{CBO} , I_{CEO} . Derive an expression to find the relation between them. (8)
 b) Determine the values of I_C , V_{CC} , R_B and β for the biasing circuit in Fig. where $R_C=2.2k\Omega$, $V_{CE} = 7.2 V$, $I_e=4mA$, $I_b= 20\mu A$. (8)



- Q4** a) With neat diagram, explain Input and Output characteristics of common emitter configuration. (8)
 b) Using NAND logic gates derive all the other logic gates. (8)

- Q5** a) Find out the expression for the rms voltage, dc voltage, and peak inverse voltage (PIV) for the full wave center-tapped rectifier (8)
 b) Briefly discuss the operation of a n channel JFET and its output characteristic. (8)

- Q6** a) Write properties of Ideal OP-AMP. Explain the output of a inverting OP-AMP circuit with neat diagram. (8)
 b) Draw the output waveform for the given circuit with explanation.

