

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
PET31104

3rd Semester Regular / Back Examination 2018-19

DIGITAL ELECTRONICS

BRANCH : ECE, ETC

Time : 3 Hours

Max Marks : 100

Q.CODE : E891

Answer Question No.1 (Part-1) which is compulsory, any EIGHT from Part-II and any TWO from Part-III.

The figures in the right hand margin indicate marks.

Part- I

Q1 Short Answer Type Questions (Answer All-10)

(2 x 10)

- An 8-bit 2's complement numeral system can represent integers in the range _____ to _____.
- $(24)_b + (17)_b = (40)_b$. Determine b.
- 46-25. Perform the operation using 2's complement method.
- Implement X-NOR using NOR gates only.
- Find the total propagation delay time of a conventional 4-bit adder and a 4-bit adder with carry look ahead with the given data.
Propagation delay of exclusive-OR, AND and OR gate is 10ns, 5ns and 5ns respectively.
- Design $Y=AB$ using multiplexer.
- How error can be detected and corrected in received binary bits?
- Differentiate between asynchronous and synchronous sequential circuits.
- What do you mean by figure of merit of a logic family?
- Write the VHDL code for the Boolean expression of a 2-input NAND gate. Assume the delay of gate is 6ns.

Part- II

Q2 Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve)

(6 x 8)

- Simplify the following expression in POS. Implement using NOR only.
 $F(A, B, C, D) = \pi(0, 1, 2, 3, 4, 10, 11)$
- Simplify the following Boolean function F, together with the don't care condition 'd'. Implement the simplified expression using NAND only.
 $F(A, B, C, D) = \sum(0, 6, 8, 13, 14)$
 $d(A, B, C, D) = \sum(2, 4, 10)$
- Implement a two bit magnitude comparator circuit using 2to4 size decoders.
- Explain the operation of Full-subtractor circuit. Derive and Implement a Full-subtractor circuit using Half-subtractor.
- Implement the following function with the help of 4:1 multiplexers.
 $F = \sum(1, 2, 3, 5, 11, 12, 15)$
- The content of a 4-bit shift register is initially 1101. The register is shifted six times to the right with the serial input being 110101. Show the content of the register after each shift.
- Design a MOD-12 counter using MOD-4 and Mod-3 counter. Explain the operation.

- h) The three stage Johnson counter with initial state of $Q_2Q_1Q_0 = 101$ as shown in figure-1 is clocked at a constant frequency of ' f_c '. If the circuit is triggered for six pulses, then draw the corresponding output waveforms of Q_2, Q_1 and Q_0 in each pulse.

 


Figure-1

- i) Describe the performance parameters considered in digital integrated circuits.
- j) Using VHDL, design a binary UP counter that counts 0 to 7.
- k) With neat circuit diagram, explain a RAM consisting of 4 words of 3bits each.
- l) With neat diagram, explain TTL inverter.

Part-III

Long Answer Type Questions (Answer Any Two out of Four)

- Q3** a) Explain the rules of 1's complement addition and subtraction with suitable example. (8)
- b) Design a 2-bit BCD adder circuit. (8)
- Q4** a) Design a four-bit combinational circuit 2's complementer. Show that the circuit can be constructed with exclusive-Or gates. (8)
- b) Assuming two numbers of 4-bit each, mention the overflow rules in addition and subtraction operation. Hence, design and explain a 4-bit adder-subtractor circuit. (8)
- Q5** a) What is race-around condition? How does it get eliminated in a Master-slave configuration? Explain with neat diagrams. (8)
- b) Design a 4-bit synchronous counter using J-K flip-flops. Use K-maps. (8)
- Q6** a) Explain in brief the three modeling styles in VHDL. (8)
- b) Explain the working of basic TTL NAND gate with a neat diagram. Describe Open collector and Totem-pole output. (8)