

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
PEL31102

3rd Semester Regular/Back Examination 2018-19

ANALOG ELECTRONIC CIRCUITS

BRANCH : EEE

Time : 3 Hours

Max Marks : 100

Q.CODE : E664

Answer Question No.1 (Part-1) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part- I

Q1 Short Answer Type Questions (Answer All-10) (2 x 10)

- Prove that FET is a voltage controlled device.
- Compare fixed bias and self-bias of BJT.
- Derive an expression for total collector current in CE configuration.
- Give the load line of BJT amplifier if $V_{CC} = +9V$ and $R_C = 1.8k$
- Write Shockley's equation. How it is used to design d.c biasing of JFET?
- Differentiate between FET and BJT.
- An amplifier is burst into oscillation when the loop gain $A\beta=1$, but for sustained oscillation $A\beta>1$, Why so?
- What is linear amplification factor of a transistor if its gain is 100 ?
- What do you mean by CMRR? How it affects the performance of Op-Amp
- What do you mean by distortion in a power amplifier? Which power amplifier gives least amount of distortion?

Part- II

Q2 Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- Explain the characteristics of a JFET. With diagram, explain the self-biasing scheme used in JFET.
- Sketch the hybrid π -model of CB amplifier. Derive the relations of gain, input and output impedances.
- Explain the frequency response of BJT amplifier.
- Consider a general feedback system with parameters $A=10^6$ and $A_f = 100$. If the magnitude of A decreases by 20%, what is the corresponding % change in A_f ?
- Explain how operating is selected in a self-bias configuration of JFET.
- Draw the cascade configuration and explain its operation.
- Find the input resistance, output resistance of an amplifier that employs voltage series feedback.
- Derive the conditions of oscillation in a Wein-bridge oscillator.
- Draw the Op-amp phase shift oscillator and derive the expression for frequency of oscillation.
- Explain how Op-Amp can be used for voltage summing amplifier.
- Draw an emitter follower circuit. What is the type of feedback observed? Find the feedback factor. Determine the voltage gain with and without feedback.
- The pinch-off voltage of a p-channel JFET is $V_p = -5V$ and $I_{DSS} = -10mA$. The drain source voltage V_{DS} is such that a saturated drain current $I_{DS} = -15mA$ is maintained. Find the gate source voltage V_{GS} .

Part-III

Long Answer Type Questions (Answer Any Two out of Four)

Q3 a) Explain the frequency response of BJT amplifier. **(8)**

b) Sketch the CE and CB hybrid equivalent model, given $I_{E(dc)}=1.2\text{ mA}, \beta=120$ and $r_0=40\text{ K}\Omega$. **(8)**

Q4 Briefly explain the principle and operation of N-channel and P-channel MOSFET with its transfer characteristics. **(16)**

Q5 a) State and explain the Barkhausen criterion for sustained oscillation. Discuss its importance in operation of an oscillator circuit. **(8)**

b) Describe Miller's effect and derive an equation for Miller input and output capacitance. **(8)**

Q6 Draw the circuit diagram of a class-A transformer coupled power amplifier using an npn transistor. This amplifier drives a 16 ohm speaker through a 4:1 transformer, using a power supply of $V_{CC}=36\text{V}$, the circuit delivers 2 watts to the load. Calculate **(16)**
a) AC power across transformer primary
b) AC voltage across the load
c) the RMS value of load current