

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
BEES2211

3rd Semester Back Examination 2018-19

NETWORK THEORY

BRANCH : AEIE, AERO, CSE, ECE, EEE, EIE, ELECTRICAL, ETC, IEE, IT, ITE

Time : 3 Hours

Max Marks : 70

Q.CODE : E993

Answer Question No.1 which is compulsory and any five from the rest.

The figures in the right hand margin indicate marks.


Q1 Answer the following questions : (2 x 10)

- Define Kirchoff's current and voltage laws.
- State the maximum power transfer theorem.
- Write an expression for resonance frequency and band width of series RLC circuit.
- Write two properties of Laplace Transform.
- Convert a star connection to delta. $R_a = 1K\Omega$, $R_b = 5K\Omega$, $R_c = 100\Omega$
- Check Whether the polynomial is stable or not
 $P(s) = 6s^6 + 8s^5 + 3s^4 + 4s^3 + 9s^2 + 12s + 5$
- State the necessary conditions for driving point functions.
- What is the Initial & Final value of the function? $F(s) = \frac{0.24}{s(s^2 + 0.53s + 0.617)}$
- What is the difference between oriented graph and incident graph?
- What is the efficiency and power produced by the network at maximum power transfer condition?

Q2 a) A series RL circuit with $R=100\Omega$ and $L= 20H$ has a DC voltage of 200V applied through a switch at $t=0$. Find (5)


- The equation for current and voltage across L and R
- The current at $t=0.5\text{sec}$

b) (5)

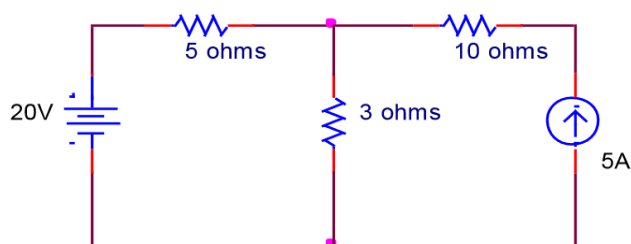

Find the current through 3Ω register using superposition theorem.

Q3 a) (5)

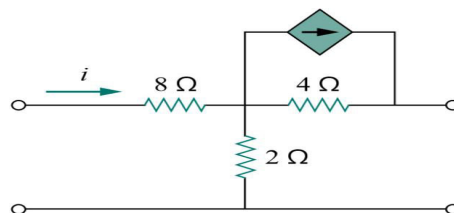

Obtain h- parameter of given circuit.

b) Sketch the waveform that is represented by (5)

- $I(t) = r(t) + 2r(t-1) - u(t+2) - 2r(t-2) + r(t-3) + u(t-4)$
- $v(t) = 3u(t) + 3u(t-1) - 3u(t-2) + 2u(t-3)$

- 210 210 210 210 210 210 210 210
- Q4** a) Derive the condition of symmetricity and reciprocity condition in terms of y-parameter. **(5)**
 b) Derive the condition of resonance for a circuit having a RL branch in parallel with a RC branch. **(5)**

- 210 210 210 210 210 210 210 210
- Q5** a) Explain the following term with example **(5)**
 i. Incidence matrix
 ii. Tie-set matrix
 b) With neat diagram explain about series connection of two port network. How it is different from cascade connection. **(5)**

- 210 210 210 210 210 210 210 210
- Q6** a) A function is given by $Z(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$ **(5)**
 Find the positive realness of the function.

- b) A current transfer function is given by **(5)**

$$I(s) = \frac{5s}{(s + 2)(s^2 + 2s + 2)}$$

Obtain its time domain response from pole zero plot.

- Q7** Find the First and second Foster form of the driving point impedance function **(10)**

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- Q8** Write short answer on any TWO : **(5 x 2)**

- a) Image impedance
 b) Hurwitz polynomial
 c) Transient analysis of Series resonant circuit.
 d) Time domain behavior of pole zero plot