

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech  
PEEE5409

**7<sup>th</sup> Semester Back Examination 2018-19**  
**FLEXIBLE AC TRANSMISSION SYSTEM**  
**BRANCH : EEE, ELECTRICAL**  
**Time : 3 Hours**  
**Max Marks : 70**  
**Q.CODE : E447**

**Answer Question No.1 which is compulsory and any FIVE from the rest.**  
**The figures in the right hand margin indicate marks.**

- Q1** Answer the following questions : **(2 x 10)**
- a) Write two uses of Facts technology in HVDC?
  - b) Explain the thermal capability of an overhead line?
  - c) Discuss the stability issues that limit the transmission capability?
  - d) State the objectives of voltage and phase angle regulators?
  - e) What are the objectives of series compensation?
  - f) Compare thyristor and GTO?
  - g) What are the types of FACTS controller?
  - h) Compare the conventional series controller with the advanced series controller(IPFC)?
  - i) What is the best location for SVC? Justify.
  - j) What are the advantages of IPFC over UPFC?
- Q2**
- a) Explain the active and reactive A.C power flow control and dynamic stability with phasor diagram for a transmission line? **(5)**
  - b) Write down the benefits from FACTS controllers in terms of control attributes? **(5)**
- Q3**
- a) What are the objectives of shunt compensation? Explain how the transient stability improves using equal area criterion? **(5)**
  - b) Explain the working of single phase Thyristor -switched capacitor(TSC) with associated waveforms? **(5)**
- Q4**
- a) What are the objectives of shunt compensation? Explain the midpoint voltage regulation for line segmentation? **(5)**
  - b) Explain the Basic GTO Thyristor-controlled series capacitor? **(5)**
- Q5**
- a) Explain with necessary diagrams how the transient stability can be improved with a series FACTS controller? **(5)**
  - b) Explain the operating principles of power flow control by phase angle regulators with a neat diagram of power vs angle characteristics? **(5)**

**Q6 a)** Explain the principle of operation of interline power flow controllers (IPFC) with a neat diagram? **(5)**

**b)** Draw and explain briefly the generalized and multifunctional IPFC module with comprehensive real and reactive power flow control capabilities for a multilane transmission system? **(5)**

**Q7** Draw the diagram of a UPFC and discuss the detail purpose of the two back to back voltage source converters, and also discuss the transmission control capabilities of UPFC using phasor diagrams? **(10)**

**Q8 Write short answer on any TWO :** **(5 x 2)**

- a) STATCOM with its V-I Characteristic
- b) Compare SVC and STATCOM with V-I and V-Q Characteristic
- c) Application of UPFC
- d) Switching Converter Type Series Compensators (SSSC)

