



Registration No:

--	--	--	--	--	--	--	--	--	--

M.TECH

Total Number of Pages : 1

M.TECH 1ST SEMESTER SUPPLE EXAMINATIONS, DECEMBER 2018

POWER CONVERSION DEVICES AND DRIVES

Branch: PE, Subject Code:MPEPC1030

(Regulations 2017)

Time: 3 Hours

Max Marks : 70

Question Code: SD18002048

PART-A (10 X 2=20 Marks)

1. Answer the following questions.

- A single phase full converter, connected to 230V,50 Hz source, is feeding a load $R=10\Omega$ in series with a large inductance that makes the load current ripple free. For a firing angle of 45° , calculate the input and output performance of this converter.
- Why stator voltage control is more suitable for speed control of induction motor in fan type load than constant type load?
- What are the voltage equations in the rotor's dq0 reference frame for Synchronous motor
- Draw the basic Two-pole Machine representation of Commutator machines
- Draw the approximate transient torque characteristics of Synchronous machine
- Write the voltage and current equations of Kron's Primitive machine
- What is meant by two reaction theory?
- What is meant by slip power recovery scheme
- What is principle of Polyphase Induction machine?
- Define CSI and VSI.

PART-B (5 X 10=50 Marks)

Answer any five questions from the following.

- Draw the equivalent circuit for a single phase induction motor based on the two revolving Field theory and identify the various parameters involved in it. [5]
 - Derive the expressions for various self and mutual inductances of a three phase synchronous machine [5]
- Explain the steady state analysis with equivalent circuit of 3-phase induction motor [5]
 - Explain the two-axis representation of a synchronous machine [5]
- Explain how a differential equation for an A.C. circuit or machine can be converted to a phasor equation [5]
 - Explain with neat sketch the magnetically coupled circuits [5]
- Describe the basic principle of working of single phase to single phase step down Cyclo converter for both continuous and discontinuous conductions for a bridge type Converter with circuit and waveforms. [5]
 - Evaluate the input power factor and harmonic factors for a Three-Phase half controlled converters [5]
- What is an inverter? What help of circuit and waveforms explain the operation of single Phase bridge inverter. [5]
 - Draw the waveforms and discuss the performance of Sinusoidal PWM control used in inverters. [5]
- Explain the 3-phase synchronous machine with and without damper bars [5]
 - With neat diagram describe the static Kramer's method for slip recovery power for three-Phase induction motor. What are the drawbacks seen [5]
- Write short notes on
 - Two-axis model of 3phase induction motor. [5]
 - Four Quadrant Chopper ==0== [5]