



GIET Main Campus (Autonomous)

Gunupur-765 022

Reg.No.:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.TECH. DEGREE EXAMINATION-NOV-DEC.2018

End Semester Examination

BELPC3020/BEEPC3030-Analog and Digital Circuits

(Regulations 2017)(Common to EE and EEE Branches)

Time : 3 Hours


Maximum : 100 Marks

Question Code:301012

Answer ALL Questions

PART A - (10 X 2 = 20 Marks)

 1. (a) Calculate minority current I_{CO} if $I_C = 20.002$ mA and I_C majority = 20 mA [CO1][PO2]
A. 20 A
B. 0.002 A
C. 2 nA
D. 2 A
- (b) For normal operation of a pnp BJT, the base must be.....with respect to the emitter and.....with respect to the collector. [CO1][PO1]
A. positive, neg B. positive, positive
C. negative, positive
D. negative, negative
- (c) Refer to the given figure. A square-wave input is applied to this amplifier. The output voltage is most likely to be [CO2][PO2]



- A. a square wave.
B. a triangle wave.
C. a sine wave.
D. no output.
- (d) In which of the following are operational amplifiers (op-amps) used? [CO2][PO1]
A. Oscillators
B. Filters



GIET Main Campus (Autonomous)

Gunupur-765 022

- C. Instrumentation circuits
- D. All of the above

- (e) Why an integrator cannot be made using low pass RC circuit? [CO2][PO1]
A. It require large value of R and small value of C
B. It require large value of C and small value of R
C. It require large value of R and C
D. It require small value of R and C
- (f) In the decimal numbering system, what is the MSD? [CO3][PO1]
A. The middle digit of a stream of numbers
B. The digit to the right of the decimal point
C. The last digit on the right
D. The digit with the most weight
- (g) Convert hexadecimal value 16 to decimal. [CO3][PO2]
A. 2210
B. 1610
C. 1010
D. 2010
- (h) How many bits are in an ASCII character? [CO3][PO1]
A. 16
B. 8
C. 7
D. 4
- (i) How much storage capacity does each stage in a shift register represent? [CO4][PO1]
A. One bit
B. Two bits
C. Four bits
D. Eight bits
- (j) Latches constructed with NOR and NAND gates tend to remain in the latched condition due to which configuration feature? [CO4][PO1]
A. Low input voltages
B. Synchronous operation
C. Gate impedance
D. Cross coupling

PART B - (10 X 2 = 20 Marks)


2. (a) Explain why an ordinary junction transistor is called bipolar? [CO1][PO1]



- (b) What is the difference between BJT and FET? [CO1][PO1]
- (c) Define slew rate. [CO2][PO1]
- (d) Define CMRR [CO2][PO1]
- (e) Calculate the output voltage of a non inverting amplifier for values of $V_1 = 2\text{ V}$, $R_f = 500\text{ k}\Omega$, and $R_1 = 100\text{ k}\Omega$. [CO2][PO2]
- (f) Convert the hexadecimal number 4AC7. 4B into its equivalent octal number [CO3][PO2]
- (g) Find the gray equivalent of the following binary numbers: 100010111 [CO3][PO2]
- (h) Write the expression in SOP form, $y = AB + C$ [CO3][PO2]
- (i) If an 8-bit ring counter has an initial state 10111110, what is the state after the fourth clock pulse? [CO4][PO2]
- (j) Write the excitation table for JK and SR flip flop. [CO4][PO1]

PART C - (4 X 15 = 60 Marks)

 3. (a) (i) Determine the quiescent levels of I_{CQ} and V_{CEQ} for the network of Fig [10][CO1][PO2]




- (ii) Write short note on working principle of photovoltaic cell [5][CO1][PO1]

(or)

(b) (i) Determine R_B and R_C for the transistor inverter of Fig. if $I_{Csat} = 10\text{mA}$.


[7][CO1][PO2]

 

(ii) For the emitter bias network of Fig., determine:

[8][CO1][PO2]

 - (a) I_B .
- (b) I_C .
- (c) V_{CE} .
- (d) V_C .
- (e) V_E .
- (f) V_B .
- (g) V_{BC} .



4. (a) (i) Determine the output voltage of an op-amp for input voltages of $V_{i1} = 150\text{ }\mu\text{V}$, $V_{i2} = 140\text{ }\mu\text{V}$. The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is: [8][CO2][PO2]

(a) 100. (b) 10 5 15 Marks CO2 PO2 8

(ii) Derive an expression for op-amp as differentiator with an example.

[7][CO2][PO2]


(or)



GIET Main Campus (Autonomous)

Gunupur-765 022

 - (b) (i) For the summing amplifier shown in fig., estimate the values of resistors R_1, R_2 and R_3 so that the output V_θ is, $V_\theta = -(3V_1 + V_2 + 0.2V_3)$ What is the approximate value of the compensating resistor R ? [8][CO2][PO2]



- (ii) Derive an expression for op-amp as integrator with an example. [7][CO2][PO2]

5. (a) (i) Design a logic gate for BCD to binary code conversion. [8][CO3][PO3]

- (ii) Design a full adder using 1:8 DMUX. [7][CO3][PO2]

(or)

- (b) (i) Design a 8:1 mux using two 4:1 mux and one 2:1 mux [7][CO3][PO3]

- (ii) Design the following three variable expression $F(A,B,C)=\Sigma(0,1,5,7,13,14)$ Using 1:8 DMUX [8][CO3][PO3]

6. (a) (i) Represent T flip flop in terms of JK flip flop [7][CO4][PO2]

- (ii) Write the working principle of universal shift register [8][CO4][PO2]

(or)

- (b) (i) Explain about serial input serial output shift register [8][CO4][PO3]

- (ii) Design a asynchronous MOD-10 counter [7][CO4][PO3]