



Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages :2

**B.TECH. DEGREE EXAMINATION-NOV-DEC.2018**

**End Semester Examination-III Semester**

**BECPC3010 Analog Electronics Circuits**

**(Regulations 2017)(Common to AEIE and ECE Branches)**

**Time : 3 Hours**

**Maximum : 100 Marks**

**Question Code:281712**

**Answer ALL Questions**

**PART A - (10 X 2 = 20 Marks)**

1. (a) A transistor has a  $\beta_{DC}$  of 250 and a base current,  $I_B$ , of 20  $\mu$  A. The collector current,  $I_C$ , equals  
A) 500  $\mu$  A B.5 mA C.50 mA D.5 A [CO1][PO2]
- (b) Junction Field Effect Transistors (JFET) contain howmany diodes?  
A.4 B.3 C.2 D.1 [CO1][PO1]
- (c) When  $V_{GS} = 0.5 V_p$  gm is ..... the maximum value. [CO2] [PO3]  
A) one-fourth B) one-half C) three-fourths D) two-thirds
- (d) Transconductance is the ratio of changes in ..... [CO2] [PO1]  
A)  $I_D$  to  $V_{GS}$  B)  $I_D$  to  $V_{DS}$  C)  $V_{GS}$  to  $I_G$  D)  $V_{GS}$  to  $V_{DS}$
- (e) An amplifier has an input signal voltage of 0.054 mV. The output voltage is 12.5 V.  
The voltage gain in dB is [CO3] [PO2]  
A) 53.6 dB. B) 107.3 dB. C) 231 dB. D) 116 dB.
- (f) Halving the power corresponds to a.....dB..... [CO3] [PO2]  
A) 3, decrease B) 10, decrease C) 3, increase D) 10, increase
- (g) .....is the unit for the slew rate, SR. [CO2] [PO1]  
A) V/ms B) ms/V C) V D). V/s
- (h) Negative feedback in an amplifier: [CO4] [PO4]  
A)Causes oscillation. B. Increases sensitivity. C) Reduces the gain.  
D) Is used in an Armstrong oscillator.
- (i) A feedback circuit usually employs.....network. [CO4] [PO3]  
1. Resistive 2. Capacitive 3.Inductive 4.None of the above
- (j) The main features of a large-signal amplifier is the circuit's..... [CO2] [PO1]  
a) power efficiency b)maximum power limitations  
c) impedance matching to the output device d).All of the above

**PART B - (10 X 2 = 20 Marks)**

2. (a) What is load line? Explain its significance. [CO4] [PO1]
- (b) Write the difference between BJT and FET [CO1] [PO1]
- (c) State an application of emitter follower circuit. [CO2] [PO1]
- (d) Explain how  $g_m$  is determined graphically in a JFET. [CO2] [PO3]
- (e) Define the frequency response of Amplifier? [CO3] [PO1]
- (f) What is the significance of gain bandwidth product? [CO3][PO1]
- (g) What do you mean by CMRR? [CO2] [PO1]
- (h) What is a virtual ground? What is its effect on op-amp operation? [CO2] [PO1]
- (i) Draw the electrical equivalent circuit of a crystal. [CO4] [PO4]
- (j) What is the advantage of using a crystal oscillator? [CO4] [PO3]


**PART C - (4 X 15 = 60 Marks)**

3. (a) (i) Explain the comparison of CB, CC and CEtransistor amplifiers. [5][CO1] [PO1]
- (ii) Give the dc load line for a fixed bias circuit with  $V_{CC} = 9$  V,  $\beta = 100$   
and  $R_B = 20$  K $\Omega$  that uses a silicon transistor [10][CO1] [PO2]
- (or)
- (b) (i) Design a voltage-divider bias network using a supply of 24 V, a transistor  
with a beta of 110, and an operating point of  $I_{CQ} = 4$  mA  
and  $V_{CEQ} = 8$  V. Chose  $V_E = \frac{1}{8} V_{CC}$  [5][CO1] [PO2]



(ii) Determine  $V_C$  and  $V_B$  for the network

[10][CO1] [PO2]

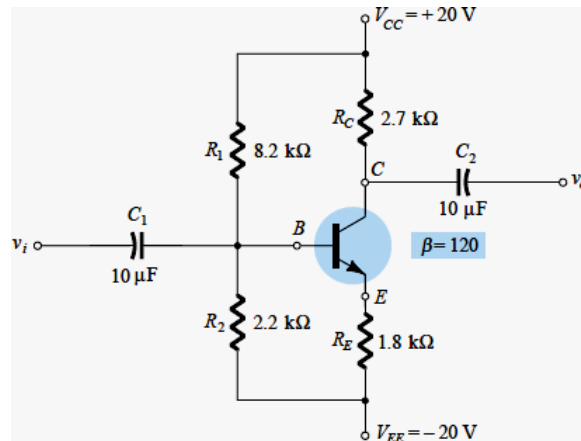

4. (a) (i) Determine the following for a common-emitter amplifier if  $\beta = 80$ ,  $I_E(\text{dc}) = 2 \text{ mA}$ , and  $r_o = 40 \text{ K}\Omega$ .

[10][CO2][PO1]

- $Z_i$
- $I_b$
- $A_i = I_o / I_i = I_L / I_b$  if  $R_L = 1.2 \text{ K}\Omega$
- $A_v$  if  $R_L = 1.2 \text{ K}\Omega$


(ii) Derive the voltage gain for a Common Base configuration using its  $r_e$  equivalent circuit.

(or)

[5][CO2][PO1]

- (b) (i) Determine  $Z_i$ ,  $Z_o$ , and  $V_o$  for the network of Fig. if  $V_i = 20 \text{ mV}$ .

[10][CO2] [PO4]

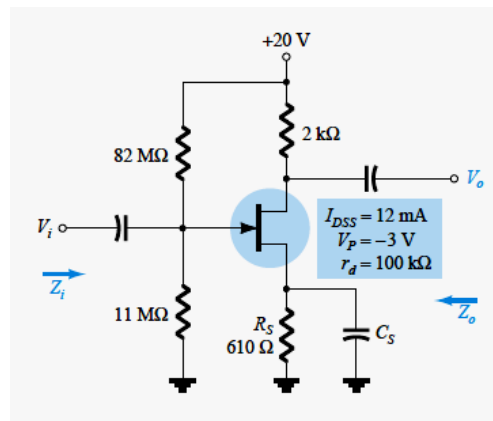

- (ii) An n-channel FET has  $V_P = -2.0 \text{ V}$  and  $I_{DSS} = 1.65 \text{ mA}$ . It is desired to bias the circuit at  $I_D = 0.8 \text{ mA}$  at  $V_{DD} = 24 \text{ V}$ . Find  $V_{GS}$ ,  $g_m$ ,  $R_S$  and  $R_D$ .

[5]CO2] [PO3]

- (i) Write short notes on Miller effect capacitance.
  - (ii) Derive an expression for the upper 3-dB cut off frequency for a CE amplifier. State your assumptions clearly.

[7][CO3] [PO1]

[8][CO3][PO2]

(or)

- (i) Explain frequency response of BJT amplifiers.
- (ii) Explain frequency response of JFET.

[7][CO3] [PO1]

[8][CO3] [PO1]

- (i) What do you mean by power amplifier? Draw circuit diagram of push pull amplifier using a pair of complementary transistors and explain its operation.
  - (ii) An amplifier with negative feedback has voltage gain of 120. It is found that with feedback, an input signal of 60 mV is required to produce a particular output, where as with feedback the input signal must be 0.5 V to get the same output. Find the  $A_v$  and  $\beta$  of the amplifier.

[10][CO4] [PO1]

[5][CO4] [PO4]

(or)

- (i) Write various advantages of negative feedback? Draw the block diagrams of different topologies?
- (ii) For the voltage-series feedback configuration, find out the expression for voltage gain, input impedance, and out impedance.

[5][CO4] [PO3]

[10][CO4] [PO4]