



Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages :2

B.TECH. DEGREE EXAMINATION-Nov-Dec.2018

End Semester Examination-III Semester

**BBSBS3030-DIGITAL LOGIC DESIGN**

**(Regulations 2017)(Common to CSE & IT Branches of Engineering)**

Time : 3 Hours

Maximum : 100 Marks

Question Code:271412

Answer ALL Questions

**PART-A (10 X 2=20 Marks)**

1. (a) Give the decimal value of binary 10010. [CO1][PO2]  
A. 610 B. 910 C. 1810 D. 2010
- (b) Which of the following is the most widely used alphanumeric code for computer input and output? [CO1][PO1]  
A. Gray B. ASCII C. Parity D. EBCDIC
- (c) Which of the following expressions is in the sum-of-products (SOP) form? [CO2][PO1]  
a.  $(A + B)(C + D)$  b.  $(A)B(CD)$  c.  $AB(CD)$  d.  $AB + CD$
- (d) What logic function is the sum output of a half-adder? [CO2][PO1]  
A. OR B. NOR C. exclusive-OR D. exclusive-NOR
- (e) A flip-flop has..... [CO3][PO1]  
A. one stable state B. no stable states C. two stable states D. none of the above
- (f) The terminal count of a modulus-11 binary counter is..... [CO3][PO1]  
A. 1010 B. 1000 C. 1001 D. 1100
- (g) Which of the following is a type of shift register counter? [CO3][PO1]  
A. Decade B. Binary C. Ring D. BCD
- (h) How many address bits are needed to select all memory locations in the 16K X 1 RAM? [CO4][PO2]  
A. 10 B. 12 C. 14 D. 18
- (i) A type of digital circuit technology that uses bipolar junction transistors is..... [CO4][PO1]  
A. TTL B. CMOS C. LSI D. NMOS
- (j) Which of the following is the fastest logic? [CO5][PO1]  
A. TTL B. ECL C. CMOS D. LSI

**PART-B (10 X 2=20 Marks)**

- 2.(a) Find the radix of the number system where  $24 + 17 = 40$ . [CO1][PO2]
- (b) State De Morgan's law? [CO1][PO1]
- (c) Draw the truth tables of 3-input Universal Logic Gates. [CO1][PO1]
- (d) Implement the following Boolean expression with X-OR and AND gates. [CO2][PO3]  
 $F = AB'CD' + A'BCD' + AB'C'D + A'BC'D$
- (e) Convert the following expression in canonical sum of products: [CO2][PO1]  
 $Y = AC + AB + BC$
- (f) What is a shift register? Explain the principle of 4-bit parallel-in parallel-out shift register. [CO3][PO1]
- (g) If the initial counts of a Ring counter is 0110. What are the sequences of the counter? [CO3][PO1]
- (h) What is the difference between Mealy and Moore models? [CO3][PO1]
- (i) Explain how a single 2 x 4 decoder can be used to construct a 4 x 4 RAM. [CO4][PO3]
- (j) What is 'Fan in' and 'Fan out' of the integrated logic circuits? [CO5][PO1]



PART-C (4 X 15=60 Marks)

3. (a) (i) Convert In a tabular form, write the "2421" code and "excess-3" code of decimal digit "0 to 9". What are the special properties of these codes? [7][CO1][PO1]  
(ii) Carry out the following additions : [8][CO1][PO2]  
(i) (+13, -11) using 1's complement notation. (ii) (-15, +9) using 2's complement notation.  
(or)  
(b) (i) Convert the decimal number  $4.532 \times 10^7$  to a single-precision floating-point binary number. [7][CO1][PO2]  
(ii) Establish the following identities of Boolean algebra [8][CO1][PO1]  
(i)  $A + AB = A$  (ii)  $(A + B)(A + C) = A + BC$
4. (a) (i) Obtain the truth table of the following function  $(xy + z)(y + xz)$  and express in Sum-of-minterms and Product-of-maxterms. [7] [CO2][PO1]  
(ii) Simplify the following function using Boolean algebra identity. [8][CO2][PO1]  
 $F(A, B, C, D) = \sum m(4, 5, 6, 7, 12, 13, 14)$ . And then, write the simplified functions in POS and SOP form.  
(or)  
(b) (i) Simplify the following Boolean function using a four variable K-map : [7][CO2][PO3]  
 $F(A, B, C, D) = \sum m(0, 1, 3, 4, 5, 7, 9, 11, 15)$ . And then, realize the simplified functions using logic gates.  
(ii) Simplify  $F(A, B, C, D) = ABC + BCD + AD$  using K-map. [8][CO2][PO1]
5. (a) (i) What is race around conditions? How it is avoided [7][CO3][PO1]  
(i) Using master slave Flipflop? (ii) Using edge triggering?  
(ii) Write short notes on Master slave JK flipflop. [8][CO3][PO1]  
(or)  
(b) (i) Explain how a JK and SR flipflop can be constructed using D flipflop. [7][CO3][PO3]  
(ii) Design a sequential circuit with two D flipflops A and B and one input X. [8][CO3][PO3]  
When  $X = 0$ , the state of the circuit remains same. When  $X = 1$ , the circuit goes through the state transition from 00 to 01 to 11 to 10 and back to 00 and repeats.
6. (a) (i) Describe the techniques used in Address Multiplexing in DRAM. [7][CO4][PO1]  
(ii) How many 32K x 8 RAM chips are needed to provide a memory capacity of 256 K bytes? How many lines of the address must be used to access 256K bytes? How many of these lines are connected to the address inputs of all chips? [8][CO4][PO2]  
(or)  
(b) (i) Draw the diagram of the 4 x 4 RAM. [7][CO4][PO3]  
(ii) A 3-input majority circuit produces the output as '1' when the number of 1's are more than the number of 0's at the input. Implement it using ROM. [8][CO4][PO3]