

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

**B. Tech**  
**BE 2102**

**Second Semester Regular Examination – 2015**

**BASIC ELECTRICAL ENGINEERING**

**BRANCH (S) : AEIE, AERO, AUTO, BIOMED, BIOTECH, CIVIL,  
CSE, EC, EEE, EIE, ELECTRICAL, ETC, IT, MECH, MINING  
MM, PLASTIC, TEXTILE**

**QUESTION CODE : J 367**

**Full Marks – 70**

**Time : 3 Hours**

*Answer Question No. 1 which is compulsory and any five from the rest.  
The figures in the right-hand margin indicate marks.*



1. Answer the following questions : 2 × 10
- (a) Differentiate between an ideal voltage source and practical voltage source.
  - (b) Explain the significance of power factor.
  - (c) What do you understand by retentivity ?
  - (d) Write down the equation of a sinusoidal source voltage of 60 Hz frequency having a r.m.s value of 250 V.
  - (e) What is the time constant of a RL circuit having  $R=10\ \Omega$  and  $L=10\ H$  ?
  - (f) Two impedances of value  $(2 + j6)\ \Omega$  and  $(8 - j12)\ \Omega$  are connected in series. What would be the resulting impedance in polar form ?
  - (g) Describe Constant losses occurring in a DC machine.
  - (h) A 3 phase, 50Hz, 415V, six pole induction motor runs at 960 rpm .What is the slip speed and slip ?
  - (i) What is noise and write various sources of noise ?
  - (j) What is a transducer ?

**P.T.O.**

2. (a) In an AC single phase circuit three impedances of value  $5 \angle 30^\circ \Omega$ ,  $10 \angle 60^\circ \Omega$  and  $4 - j8 \Omega$  are connected in series with a 230 V, 50 Hz supply. 5
- (i) Find the total combined impedance in Rectangular form ?
- (ii) Magnitude of the current flowing in the circuit ?
- (b) Using Super position theorem, find the voltage across  $10 \Omega$ , resistor as shown in Fig (1). 5

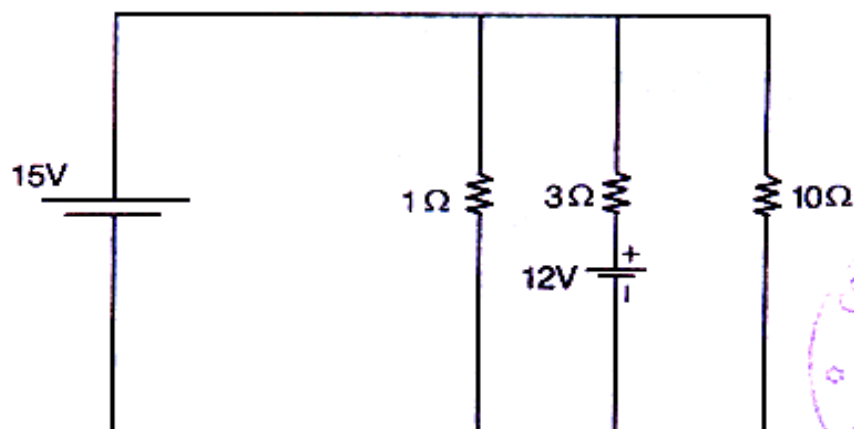


Fig (1)

3. (a) An iron ring with a circular cross section of 4cm diameter and a mean circumference of 100 cm is wound with a coil of 500 turns. For an exciting current of 3 amp in the coil, the flux is found to be 2mWb. Calculate the relative permeability of iron. (Assume  $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ ) 5
- (b) Explain the significance of B-H curve in magnetic materials. What are the various methods adopted in practice for reducing hysteresis and eddy current losses ? 5
4. (a) The potential drop  $V$  across a circuit is represented in rectangular form is  $(40 + j25)$  Volts with reference to the circuit current. The power absorbed by the circuit is 160 Watts. Determine the 5
- (i) Magnitude of current.
- (ii) The complex impedance.
- (iii) Power factor.
- (b) State and Explain Maximum Power transfer Theorem by giving a suitable example. 5

5. (a) A resistance of  $1\text{ M}\Omega$  and a capacitor of  $50\text{ }\mu\text{F}$  connected in series across a  $200\text{ V}$  DC Supply. The fully charged capacitor is then disconnected from the supply and discharged by connecting a  $100\text{ }\Omega$  resistance across its terminal. Calculate the initial values of the charging current and the discharging current and also find the time constants. 5
- (b) A 6 pole DC shunt generator the flux per pole is  $8\text{ mWb}$ . There are 96 conductors lap connected. Find out the induced voltage if the armature rotates at a speed of 25 revolutions / second ? 5
6. (a) The primary of a single phase transformer is connected to a  $220\text{ V}$ ,  $50\text{ Hz}$  supply. If the peak flux in the core is  $10\text{ mWb}$ , what is the no of turns in the primary ? How many no. of turns required in the secondary to obtain a voltage of  $110\text{ V}$  ? 5
- (b) What do you understand by rotating magnetic field ? Also explain the operating principle of a three phase induction motor. 5
7. (a) What is a thermocouple ? How the temperature measurement can be done by it ? 5
- (b) A balanced three phase star load has load impedance of  $(8 + j6)\text{ ohm}$  per phase and is supplied from a balanced three phase  $440\text{ V}$ ,  $50\text{ Hz}$  supply. Determine the values of 5
- (a) Line Voltages and phase voltages ?
- (b) The Phase current and the line current ?
- (c) Total power consumed ?
8. Answer any **two** of the following : 5 × 2
- (a) Controlled Voltage Sources
- (b) Principle of operation of DC Motor
- (c) Measurement System.