

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
BE 2101

Second Semester Back Examination – 2015

BASIC ELECTRONICS

BRANCH(S) : AEIE, AERO, AUTO, BIOMED, BIOTECH, CHEM, CIVIL, CSE, EC, EEE, EIE, ELECTRICAL, ETC, FASHION, FAT, IEE, IT, MANUFACT, MANUTECH, MECH, MINERAL, MINING, MM, MME, PLASTIC, TEXTILE

QUESTION CODE : M 289

Full Marks – 70

Time : 3 Hours

*Answer Question No. 1 which is compulsory and any five from the rest.
The figures in the right-hand margin indicate marks.*



1. Answer the following questions :

2×10

- Draw the equivalent circuit of a transistor using diode.
- What is the need of DC biasing of transistor ?
- What are the three states of the tristate logic gate ? What is its importance ?
- What is a time base voltage ? What is the need of time-base voltage in CRO ?
- How gain of an amplifier can be increased without changing the component values of the amplifier ?
- Perform the following subtraction using 2's complement method :
 $(17)_{16} - (26)_{10}$
- Construct a EX-OR gate using NAND gate only.
- Draw the block diagram of 4X1 MUX. Why it is called a data selector ?

P.T.O.

- (i) Mention two conditions that must be fulfilled in oscillator circuits.
- (j) What is CMRR ? What are the disadvantages of an OPAMP with low CMRR value ?
2. Express the necessary derivation for the efficiency of a half wave silicon diode rectifier. If a $100\ \Omega$ load resistance is connected across a half wave rectifier. The input supply voltage is 230 V (rms) at 50 Hz, then find ripple factor and efficiency of the circuit. 5+5
3. (a) What are the characteristics of an ideal electronics voltmeter ? Explain with suitable diagram, how loading error can be minimized during measurement with voltmeter. 5
- (b) With suitable block diagram explain the basic principle of a triangular wave generator. 5
4. (a) What is emitter follower circuit ? With a neat diagram explain transistor based emitter follower circuit. Mention its importance in electronics circuits. 5
- (b) In the Fig.1, if $R_1 = 470\ \text{K}\Omega$, $R_2 = 270\ \text{k}\Omega$, $R_C = 6.2\ \text{K}\Omega$, $R_E = 1.5\ \text{K}\Omega$, $C_{in} = C_o = 10\ \mu\text{F}$, $C_b = C_E = 5\ \mu\text{F}$, then find V_c , V_E , I_C , and V_{CE} when $\beta = 100$ and $V_i = 0\text{V}$ 5

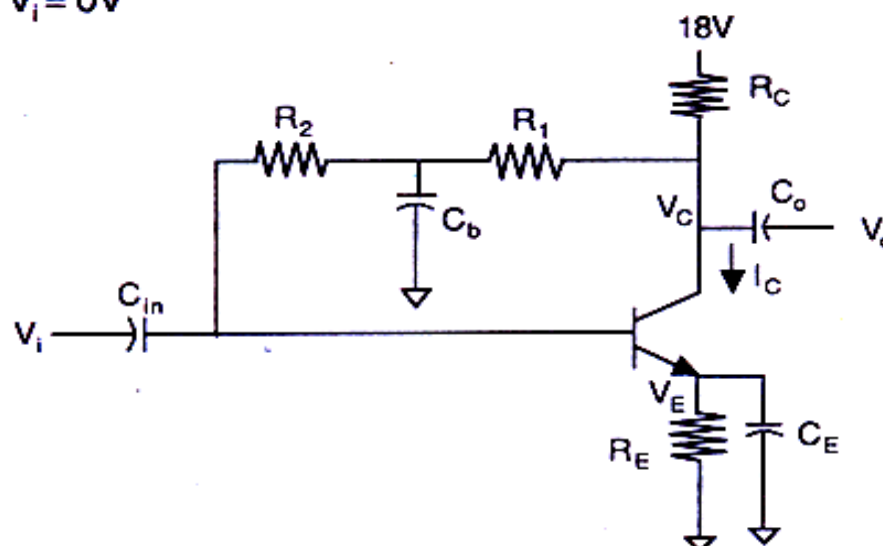


Fig. 1

5. (a) What is MUX ? Design the following Boolean function using MUX. 5
- $$F = A'B'C' + ABC + AB'C + A'BC'$$

- (b) What is POS in Boolean expressions ? Implement the following function in POS. 1+4

$$F(A, B, C) = (AB + C)(B + AC).$$

6. (a) Simplify the following Boolean function using Boolean algebra identities. 5

$$F(A, B, C, D) = \sum m(0, 2, 4, 7, 8, 9).$$

And then, realize the simplified functions using logic gates.

- (b) Explain the principle of an oscillator circuit. Mention the requirements to be filled up to built a oscillator circuit. 5

7. (a) What is an integrator circuit ? Draw and find the transfer function of OPAMP based integrator circuit. Also draw the output wave form when a 4 V peak to peak square wave voltage is given. 5

- (b) The open loop gain of an amplifier changes by 5 percents. If 10 dB negative feedback is applied, calculate percentage change of the closed loop gain. 5

8. Write short notes on any **two** : 5×2

- (a) Full adder
- (b) Universal logic gates
- (c) ROM and RAM
- (d) DC biasing.

