

BACK PAPER

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 4

B.Tech
BE 2102

Second Semester Examination – 2012

BASIC ELECTRICAL ENGINEERING

Full Marks – 70


Time : 3 Hours

*Answer Question No. 1 which is compulsory and any **five** from the rest.
The figures in the right-hand margin indicate marks.*

1. Answer the following questions : 2 × 10
- (a) State Norton's Theorem.
 - (b) Two impedances $40 \angle 30^\circ$ and $25 \angle 45^\circ$ are connected in parallel. Find out the resultant impedances in rectangular form.
 - (c) Three resistances 5Ω , 10Ω , 15Ω , are connected in Series across 120V, DC Source. Compute the Voltage across 10Ω resistor.
 - (d) Define RMS value of an alternating quantity.
 - (e) Explain various classification of transformer on the basis of placement of its core.
 - (f) Define Permeability and retentivity with reference to Magnetis.
 - (g) Write the emf equation of DC generator and explain each term associated with it.
 - (h) Write the speed equation of a DC motor and explain each term.


P.T.O.

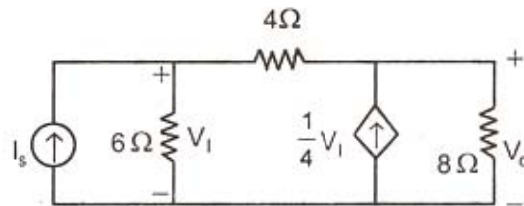- (i) Write four important parts of a nuclear power station.
- (j) Write four the measuring instruments you know for electrical measurement
2. (a) State and Explain the principle of Superposition by giving suitable example
- (b) Applying Kirchhoff's current law, determine current I_s in the electric circuit shown in Fig (1) below. Take $V_0 = 16V$.



Fig(1)

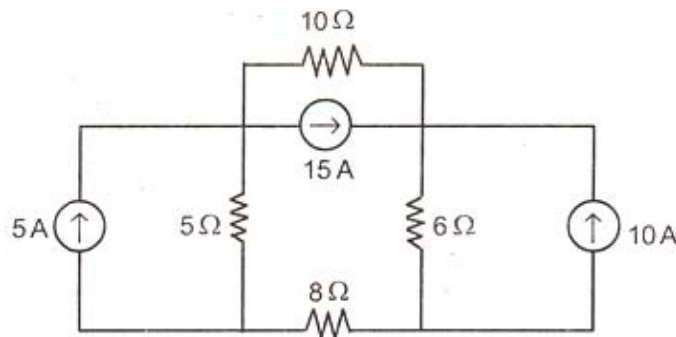3. (a) Explain the Hysteresis loss by drawing B-H curve.
- (b) Find the current through 8Ω resistor in the given circuit below Fig applying Superposition Principle.



Fig(2)

4. (a) Briefly explain few similarities between magnetic circuit and electric circuit

- (b) Find the number of ampere turns required to produce a flux of 0.44 milli weber in an iron ring of 100 cm mean circumference and 4cm^2 in cross section. B versus μ_r test result for iron given in following table :

B(wb/m ²)	0.8	1.0	1.1	1.2	1.4
μ_r	2300	2000	1800	1600	1000

If a saw cut of 2 mm wide is made in the above ring, how many extra ampere turns required to maintain the flux ? 6

5. (a) A balanced three phase AC sinusoidal having line voltage 440V is fed to a balanced three phase star load having resistance per phase 50Ω . What would be the
- The line Voltage & phase voltage ?
 - power factor & power consumed ? 4
- (b) Explain the growth of capacitor voltage in an RC series circuit when excited suddenly by a DC source. Find the time constant. 6
6. (a) Explain the laws which are used to generate voltage in a DC generator. 4
- (b) The current in a circuit is given by $4 + j12$ when the voltage is $100 + j150$
- Determine :
- The complex expression for the impedance, state whether inductive or capacitive.
 - Power factor of the circuit.
 - The real and reactive power consumed in the circuit. 6
7. (a) Explain in brief the principle of operation of a three phase alternator. 4

(b) A 4 pole DC shunt generator with lap connected armature having field and armature resistance of $50\ \Omega$ and $0.1\ \Omega$ respectively, supplying 60 Nos. of 100 W bulbs. Calculate 6

(i) The total armature current

(ii) The current per armature path

(iii) The generated emf allowing a contact drop of 1V per brush.

8. Write short notes in any two : 5×2

(a) Controlled Sources

(b) Principle of maximum power transfer

(c) Operation principle of single phase transformer

(d) Transducers.