

BACK PAPER

Registration No. :

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

Total number of printed pages – 4

B.Tech  
BE 2101

## Second Semester Examination – 2012

### BASIC ELECTRONICS

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.  
The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2 × 10
- (a) Explain the difference between analog, digital and discrete-time signal.
  - (b) What is meaning of CMRR of an OPAMP ? How it affects the performance of the OPAMP ?
  - (c) Compare the advantages and disadvantages of center-tapped and bridge type full wave rectifiers.
  - (d) An amplifier has an open loop gain of 1000 and a feedback ratio of 0.04. If the open loop gain changes by 10% due to temperature, find the %change in gain of the amplifier with feedback.
  - (e) Derive the expression for collector current for a CE transistor.
  - (f) Determine the number of cycles of 1 kHz sinusoidal signal as viewed on an Oscilloscope when the sweep frequencies are (a) 2 kHz and (b) 500 Hz.
  - (g) A Periodic digital waveform has pulse width of 25  $\mu$ S and a period of 150  $\mu$ S. Determine the frequency and duty cycle.
  - (h) Convert  $(0.65625)_{10}$  and  $(10.625)_{10}$  to equivalent base 2 numbers by repeated division-by-2 or multiplication-by-2 methods.
  - (i) Distinguish between Multiplexer and Demultiplexer and mention one application of each.

P.T.O.

(j) Simplify the following Boolean expressions :

(i)  $Y = 1 + A(B.\bar{C} + B.C + \bar{B}.\bar{C}) + A\bar{B}C + AC$

(ii)  $Y = \overline{(A + \bar{B} + C) + B + \bar{C}}$

2. A crystal diode having an internal resistance  $r_f = 10 \Omega$  is used for center tapped full wave rectification. If the applied voltage is  $V = 50 \sin(\pi t)$  and the load resistance is  $R_L = 1 \text{ k}\Omega$ , determine the followings :

(a) Draw the input and output voltage and current waveforms. 4

(b) The efficiency of the circuit. 3

(c) The Ripple factor. 3

3. (a) What is a clipper circuit ? Explain with an example. 4

(b) Analyze and draw the output waveform of the circuit shown in Figure Q3 when  $V_i = 5 \sin(100 \pi t)$ . 6

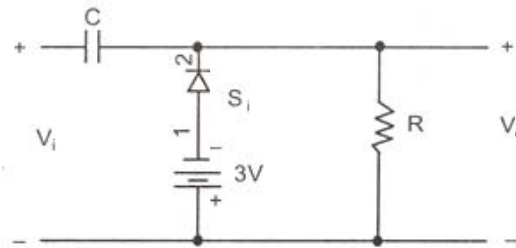


Figure Q3

4. (a) Describe the use of an opamp as a Differentiator and derive the expression of the output voltage. 5

(b) Draw and scale the output waveform  $V_o$  of the circuit shown in the Figure Q4 below for the input waveform  $V_s$  as shown in the Figure. 5

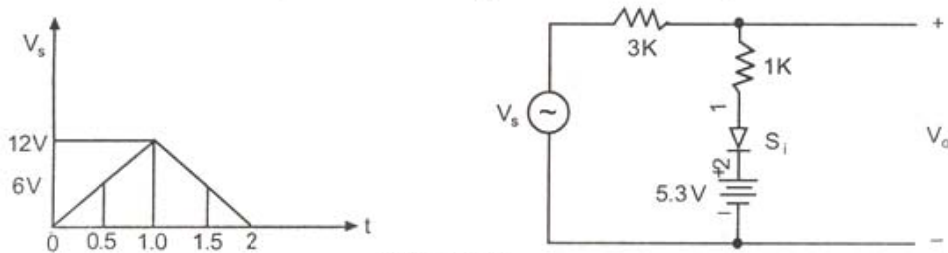


Figure Q4

5. (a) Find  $I_{CQ}$  and  $V_{CEQ}$  of the circuit shown in Figure Q5 (a) below when  $R_1 = 10\text{ k}\Omega$ . 5

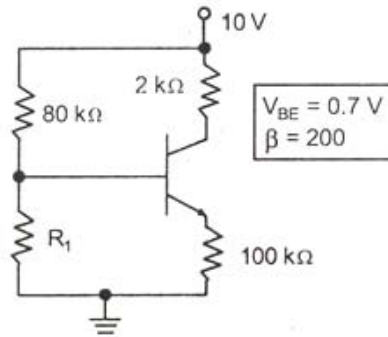


Figure Q5(a)

- (b) Find  $V_{CC}$ ,  $R_B$ , and  $R_E$  in the circuit shown in Figure Q5(b) above using the dc load line given. Assume  $\alpha \approx 1$ . 5

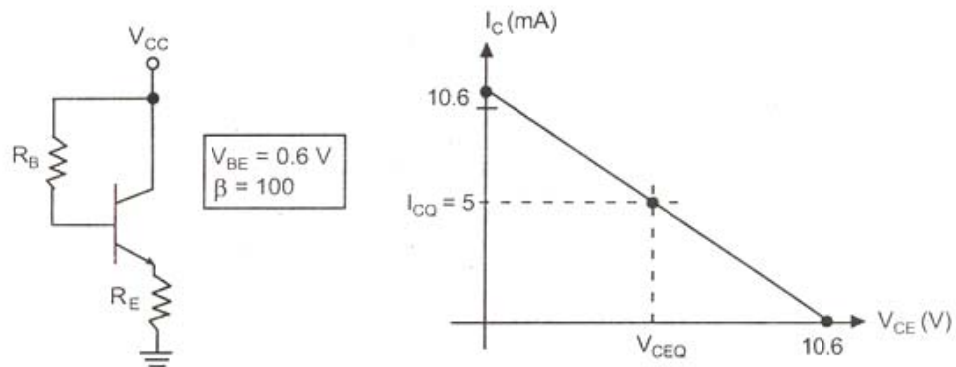


Figure Q5(b)

6. (a) Draw AC equivalent circuit of a CC amplifier using h-parameter and then find voltage gain, current gain, output and input impedances. 5

- (b) Find the bias point and AC amplifier parameters of the circuit shown in Figure Q6. The Manufacturers' specification sheets give :  $h_{fe} = 200$ ,  $h_{ie} = 5 \Omega$ ,  $h_{oe} = 10 \mu\text{Moh}$ . 5

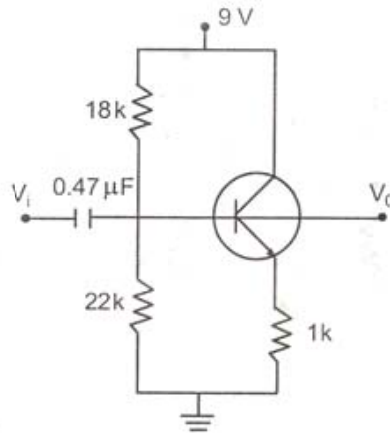


Figure Q6

7. (a) Write the truth table of half adder and full adder and draw their logic diagrams? 5
- (b) Implement the full adder using two half adders and an OR gate. 2
- (c) Draw the block diagram of a 4 bit adder. 3
8. (a) Explain the operation of a gated S-R latch with suitable sketches. 4
- (b) Implement the following Boolean functions with a multiplexer : 6
- (i)  $f(A, B, C, D) = \sum (0, 1, 3, 4, 8, 9, 15)$
- (ii)  $f(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$