

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B.Tech
BE 2101

Second Semester Examination – 2011

BASIC ELECTRONICS

Full Marks – 70


Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.
Symbols carry their usual meaning.

The figures in the right-hand margin indicate marks.


1. Answer the following questions :

2 × 10


- 
- (a) PN junction diode made up of which material (Si, Ge, GaAs) has highest barrier potential ?
- (b) Calculate the shift of forward characteristic of a silicon diode if temperature increases from 293 K to 383 K.
- (c) Why open loop op-amp configurations are not used in linear applications ? Explain with reasons.
- (d) Determine the DC resistance of a diode at $V_D = -20$ V if its reverse saturation current is $1 \mu\text{A}$.
- (e) What is a load-line ? How it is used to calculate the operating point ?
- (f) The CMRR of a differential amplifier is 55dB. If its gain in differential mode (A_d) is 1200 then calculate its gain in common mode (A_{cm}).
- (g) What is the virtual short circuit and virtual ground concept in OP-AMP ?
- (h) Write down the DeMorgan's theorem. Also show the corresponding logic diagram.
- (i) What is a Lissajous pattern ? Write down its uses.
- (j) Find the percentage increase in reverse saturation current of a PN junction diode if the temperature is increased from 25°C to 50°C .

P.T.O.

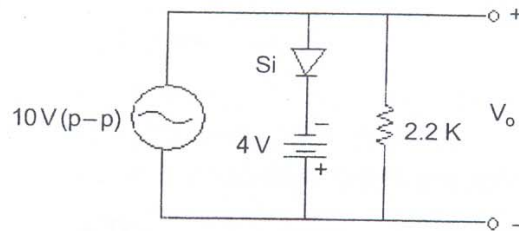2. (a) What is the condition of oscillation? Derive the expression of frequency of oscillation and also the condition of oscillation in a RC-phase shift oscillator. 5
- (b) Implement the function $F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$ using a MUX. Also implement the function into NAND only logic after simplifying the expression. 5
3. (a) Calculate the output of the diode circuit shown below. Input is a sinusoidal signal. 5




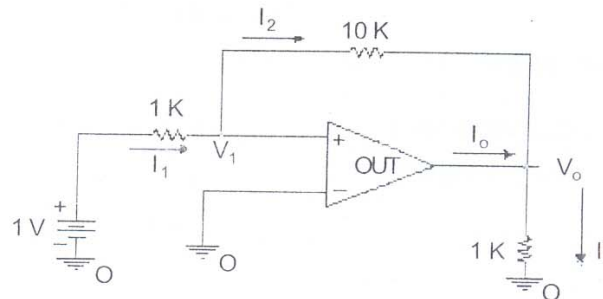- (b) For the circuit shown in figure, determine the values of v_1, i_1, i_2, v_o, i_L and i_o . Also determine the voltage gain v_o/v_i , current gain i_L/i_i and power gain P_o/P_i . 5



4. (a) A crystal diode having an internal resistance $r_f = 20 \Omega$ is used for full-wave rectification. If the applied voltage is $V = 50 \sin 2t$ and the load resistance is $R_L = 800 \Omega$, determine the following: 5
- I_m, I_{dc}, I_{rms} of output
 - AC power input and DC power output
 - Ripple factor.
- (b) The output power of an amplifier is 100 W when the load resistance is 10 ohm. The harmonic distortion in the output is 4%. Determine the voltage gain if the input is 2 Volts. What is the required feedback ratio if the harmonic distortion is to be restricted to 0.02 %. 5

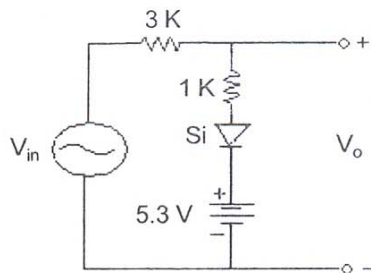5. (a) A particular diode, for which $n = 1$, is found to conduct current 3 mA with a junction voltage of 0.7 V. 5
- (i) What is saturation current I_s ?
- (ii) What change in junction voltage will increase the diode current by a factor of 10 ?
- (b) Sketch the output waveform of V_o when a 10 V (peak) triangular wave with period T is applied at input of the circuit given in the figure below : 5



6. (a) A transistor has $i_B = 100 \mu\text{A}$ and $i_C = 2 \text{ mA}$, find α and β of the transistor. If i_B changes by $+25 \mu\text{A}$ and i_C changes by $+0.6 \text{ mA}$, find the new value of β . 5
- (b) Why biasing circuits are required for a transistor ? Discuss different biasing techniques. 5
7. (a) Derive an expression for sum and carry output of a full adder circuit. Also implement the full adder using two half adders and an OR gate. 5
- (b) What is a difference amplifier ? Derive an output voltage expression for the difference amplifier. 5
8. Write short notes on any **two** of the following : 5×2
- (a) Working principle of CRT display
- (b) Function generator
- (c) Clipper and Clamper
- (d) Instrumentation amplifier.