

Registration no:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 03

**B.TECH**  
**BEES2211**

**3<sup>rd</sup> Semester Back Examination 2016-17**

**NETWORK THEORY**

**BRANCH(S): AEIE, CSE, ECE, EEE, EIE, ELECTRICAL, ETC, IT, ITE**

**Time: 3 Hours**

**Max Marks: 70**

**Q.CODE: Y644**

**Answer Question No.1 which is compulsory and any five from the rest.  
The figures in the right hand margin indicate marks.**


**Q1 Answer the following questions:**

**(2 x 10)**


- a) State Compensation theorem.
- b) Test the positive realness.

$$F(s) = \frac{s^2 + 8s + 5}{s + 2}$$


- c) Find  $V_{xy}$ .

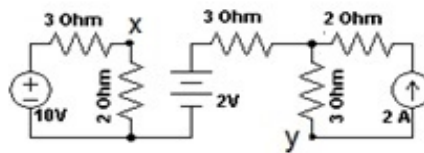

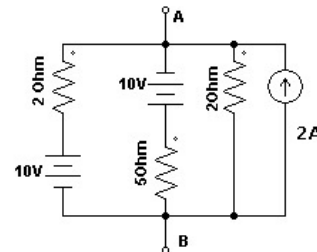
- d) Define coefficient of coupling? What are their possible maximum & minimum values?
- e) Convert the circuit to a single source network across A & B.



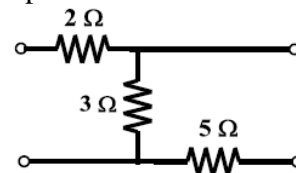
- f) What do you mean by Reciprocity & Symmetry of two port network?
- g) If two of such 2-port networks shown in figure are connected in series find the Z parameters of the equivalent circuit.



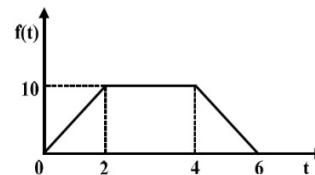- h) What do you mean by the term "S" used in Laplace transform?
- i) Find the Laplace of the wave form.




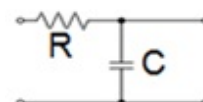- j) Which type of filter the following circuit may be and why?



**Q2**

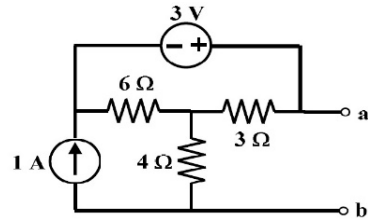
- a) Find the Thevenin equivalent circuit of the circuit shown across a-b. (5)



- b) State & explain Reciprocity theorem with examples. What are the limitations of this theorem? (5)

**Q3**

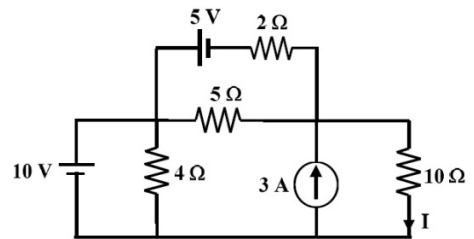
- (a) Find the current I using superposition theorem (5)




- (b) Derive the condition of resonance for a circuit having a RL branch in parallel with a RC branch. (5)

**Q4**

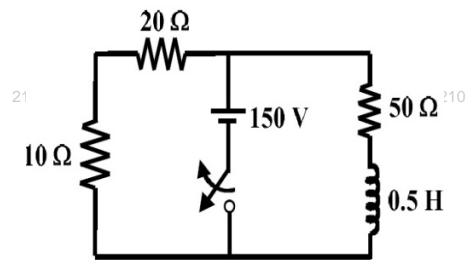
- a) At  $t=0$  switch is opened. What is the current  $i(t)$  through the 50ohm resistor for the circuit shown in figure. (5)



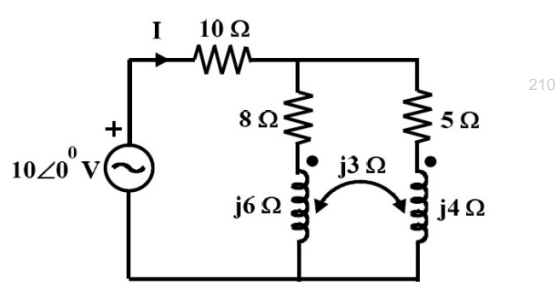- b) Find I of the circuit shown in figure (5)



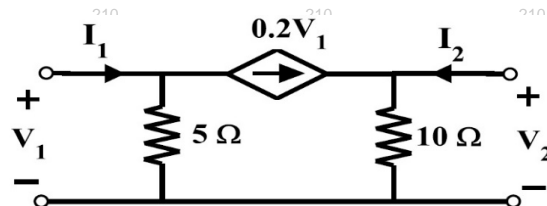- Q5** a) Find Z parameters of the two port network. (5)



- b) Derive the condition of reciprocity & symmetry for a two port network in terms of hybrid parameters. (5)

- Q6 a)** Design a constant K-type HPF filter (both T &  $\pi$ ) having nominal impedance of  $700\Omega$  and cut-off frequency of  $6000\text{Hz}$ . Also determine the characteristic impedance, attenuation constant and Phase shift at  $4000\text{Hz}$  &  $10000\text{Hz}$ . **(5)**

- b)** A current transfer function is given by **(5)**

$$I(s) = \frac{5s}{(s + 2)(s^2 + 2s + 2)}$$


Obtain its time domain response from pole zero plot.

- Q7 a)** Synthesize the given network function in the first form of Foster and 2nd form of Cauer. **(5)**
- $$Z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)}$$

- b)** What are the properties of LC impedance or admittance function? **(5)**

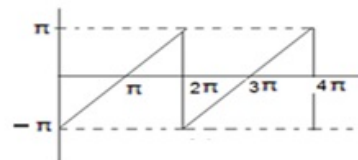**Q8**

- a)** Find the trigonometric Fourier series representation of the wave shown below. **(5)**



- b)** For an electrical network voltage & current are given below. Find the power consumed & power factor in the circuit. **(5)**

$$v = 100 \sin(\omega t + 30^\circ) - 50 \sin(3\omega t + 60^\circ)$$

$$i = 20 \sin(\omega t - 30^\circ) + 15 \sin(3\omega t + 30^\circ)$$