

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 1

M.TECH

M.TECH 2ND SEMESTER (AR 18) REGULAR EXAMINATIONS, APRIL/MAY 2019
 DIGITAL CONTROL OF POWER ELECTRONIC AND DRIVE SYSTEM

Branch: PE, Subject Code:MPEPC2020

Time: 3 Hours

Max Marks : 70

(10 X 2=20 MARKS)

PART-A**1. Answer the following questions.**

- Write two applications of numerical methods?
- What are the different elements of gate/base drive circuit?.
- What is Power Transistors in simulation?
- Why modeling of a particular circuit required?
- What is the application of simulation circuit?
- Why commutation required?
- What is Extension to AC circuits?
- What is TRIAC?
- Write two application of 3-phase inverter
- What is latching current and holding current?

PART-B

(5 X 10=50 MARKS)

Answer any five questions from the following.

- Q2. a. Explain with neat sketch Modelling of diode in simulation. [5]
 b. Explain the the different blocks of simulation of snubber circuits. [5]
- Q3. a. Explain the Current and load commutation schemes. [5]
 b.Explain the Simulation of converter fed DC motor drives. [5]
- Q4. a. Explain the Simulation of single phase thyristors circuit with RL-load. [5]
 b. Explain the state space analysis of linear systems [5]
- Q5. a. Explain the operation of 3-phase invertor with resistive and resistive Inductive loads with the help of neat circuit diagram and current wave forms. [5]
 b.Explain the Space vector representation of 6-pulse converter in rectifier mode with resistive load. [5]
- Q6. a. A single phase semi converter is operated from 230V,50Hzsupply. The load current is continuous and ripple free with an average value of 10A.For a firing angle of 30° Determine [5]
 i. Average Voltage
 ii. RMS Voltage
 iii. Form factor
 iv. Rectification Efficiency
 b. Explain the Modelling of IGBT, Power Transistors in simulation. [5]
- Q7. a. Explain the Simulation of single phse self commutated devices. [5]
 b. Explain the State space modelling and simulation of linear systems [5]
- Q8. Write short notes on: [5]
 a. Explain the different components of IGBT and Power Transistors in simulation [5]
 b. Compare the characteristics of SCR, TRIAC.

==0==