

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 1

M.TECH

M.TECH 2ND SEMESTER (AR 18) REGULAR EXAMINATIONS, APRIL/MAY 2019
SWITCHED MODE AND RESONANT CONVERTERS

Branch: PE, Subject Code:MPEPE2031

Time: 3 Hours

Max Marks : 70

(10 X 2=20 MARKS)

PART-A

1. Answer the following questions.

- What are the advantages of SMPS over factors controlled rectifiers
- Give the uses of resonant switching.
- What is the disadvantage of FM scheme compared to PWM scheme?
- What are the limitations of basic series resonant inverter?
- How to select the inductor for the buck converter?.
- What is effect of having more duty cycle and less duty cycle?
- Obtain the boundary conditions between continuous and discontinuous conduction mode of operation for boost converter
- Discuss flux imbalancing problem
- Define voltage mode control of smps
- What is meant by state space averaging ?

PART-B

(5 X 10=50 MARKS)

Answer any five questions from the following.

Q2.

- Illustrate the operation of Step down converter in continuous conduction mode and derive an expression [5]
for the ripple voltage
- Explain the bipolar and unipolar PWM switching schemes used in full bridge dc-dc converter [5]

Q3.

- Design a Buck-Boost converter circuit having parameters, input voltage =24 V, D=0.4, load resistance [5]
=5 ohm, L=20 micro H,C=80 micro F. Determine the output voltage, average inductor current, Maximum and minimum value of inductor current and the output voltage ripple. Assume a switching frequency of 100 kHz.
- With the help of neat diagram explain the three phase inverter operation, also discuss the effect of [5]
blanking time on voltage in PWM inverters

Q4.

- Explain square wave switching scheme in inverter and how to achieve the programmed harmonic [5]
elimination technique used in square wave pulse switching
- Write short note on resonant switch converters [5]

Q5.

- Explain the operation of ZCS resonant switch converters [5]
- List the various classification of resonant converters [5]

Q6.

- Explain the principle operation of a fly back converter [5]
- Explain power line disturbances caused by switching power converts [5]

Q7.

- Explain frequency characteristics of series and parallel resonant circuit [5]
- Explain the operation of zero current switching Quasi-resonant boost converter with neat circuit and [5]
waveforms

Q8. Write Short notes on :

- Current mode PWM control of SMPS [5]
- Effect of EMI filter on SMPS control [5]