

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 1

M.TECH

M.TECH 2ND SEMESTER (AR 17) SUPPLEMENTARY EXAMINATIONS, APRIL/MAY 2019

ADVANCED ELECTRIC DRIVES

Branch: PE, Subject Code:MPEPC2020

Time: 3 Hours

Max Marks : 70

PART-A

(10 X 2=20 MARKS)

1. Answer the following questions.

- What are the basic components of Electrical Drive?
- Write basic torque equation for a motor load system.
- What is the standard voltage of AC traction and DC traction in India.
- Write different speed control methods for Induction motor.
- Compare A.C drives and D.C drives.
- Why is starting current high in a DC Motor?
- Draw speed-time, distance-time & speed-time curve for traction.
- What are the main features of V/f control?
- What is meant by Voltage control in induction motor? And where it is applicable?
- Write the classifications of PWM techniques.

PART-B

(5 X 10=50 MARKS)

Answer any five questions from the following.

- Explain how an induction motor is brought to stop by (i) Plugging and (ii).dynamic braking. [5]
 - A motor drives two loads, One has rotational motion it is coupled to the motor through a reduction gear with $a=0.1$ and efficiency of 90%.The load has a moment of inertia of 10 kg-m^2 and a torque of 10 N-m . Other load has translational motion and consists of 1000kg weight to be lifted up at an uniform speed of 1.5 m/s . Coupling between this load and motor has an efficiency of 85% .Motor has an inertia of 0.2 kg-m^2 and runs at a constant speed of 1420 rpm .Determine the equivalent inertia referred to the motor shaft and power developed by the motor. [5]
- Explain synchronous motor variable speed drives [5]
 - Explain chopper controlled DC motor drive for motoring and braking operation. [5]
- Explain speed-time, distance-time & speed-time curve for traction [5]
 - Explain the typical control circuits for DC Series and Shunt motors [5]
- Explain with neat sketch the operation of chopper fed DC Series Motor drive. Also, derive the expression for average motor current. [5]
 - A 200 V , 10.5 A , 2000rpm .shunt motor has the armature and field resistance of 0.50Ω and 400Ω respectively. Its drives a load whose torque is constant at rated motor torque. Calculate the motor speed if the source voltage drops to 175 V [5]
- Explain the working of following methods with neat circuit diagram. [5]
 - Kramer system
 - Scherbius system.
 - Discuss the speed control of AC motors by using three phase AC Voltage regulators [5]
- A 3 phase.4 pole, 415 V , 50 HZ induction motor has a star connected stator. The rotor impedance at standstill is $0.1+j0.9\Omega$.The stator to rotor turns ratio is 1.75 .calculate the external resistance per phase required in the rotor to limit starting rotor current to 60 A , using rotor resistance starter [5]
 - Explain AC traction for PWM VSI squirrel cage IM drive. [5]
- Write short notes on
 - Drives for Sugar mill [5]
 - Regenerative braking in DC motor [5]