

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech  
PCEC4201

Third Semester Examination – 2013

ANALOG ELECTRONICS CIRCUIT

BRANCH : EIE, IT, BIOMED, CSE, EC, ELECTRICAL, AEIE, EEE, ETC, IEE

QUESTION CODE : C- 474

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2 × 10
- What are the basic characteristics of an instrumentation amplifier ?
  - Why square wave is chosen for determining the bandwidth of an amplifier ?
  - The output waveform of an operational amplifier as seen in CRO is 4 V peak to peak with 0.04 microsecond rise time (t<sub>r</sub>). What is its slew rate ?
  - What are the small signal h-parameters that are determined from input characteristics of a transistor amplifier ?
  - Draw the electrical equivalent circuit of a crystal. Why an oscillator circuits using crystal gives stable frequency ?
  - Calculate the second harmonic distortion when the peak to peak V<sub>CE</sub> as seen from oscilloscope is 21 Volts and V<sub>CEQ</sub> is 12 volts.
  - What is the bandwidth of the amplifier when the rise time is 0.1 m sec ? What should be the rise time of an ideal voltage amplifier ?
  - Why OPAMP is generally used in non-inverting configuration ? Justify.
  - How FET is used as a voltage dependent resistor (VDR) ?
  - Why a constant current source is used in place of R<sub>E</sub> in the differential amplifier stage of the OPAMP ?

P.T.O.

2. (a) In the Fig. 1, if  $R_1 = 470 \text{ k}\Omega$ ,  $R_2 = 270 \text{ k}\Omega$ ,  $R_C = 6.2 \text{ k}\Omega$ ,  $R_E = 1.5 \text{ k}\Omega$ ,  $C_{in} = C_o = 10 \text{ }\mu\text{F}$ ,  $C_b = C_E = 5 \text{ }\mu\text{F}$ , then find  $V_C$ ,  $V_E$ ,  $I_C$ , and  $V_{CE}$  when  $\beta = 100$  and  $V_i = 0 \text{ V}$ . 7

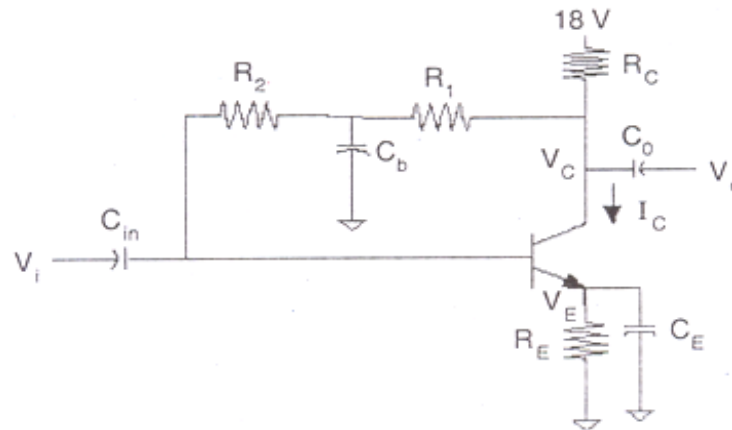


Fig. 1

- (b) What is the function of  $C_b$  and  $C_E$  in the above biasing circuit? 3
3. (a) Derive voltage gain, current gain, input impedance and output impedance of a CE transistor amplifier circuits in terms of h-parameter. 7
- (b) Explain the importance of source resistance  $R_s$  in a transistor amplifier circuits. 3
4. (a) What is Barkhausen criterion? How this condition is used in oscillator? Explain. 4
- (b) What are the primary requirements to obtain steady oscillation at a fixed frequency? 2
- (c) The open-loop gain of an amplifier changes by 5 per cents. If 10 dB negative feedback is applied, calculate percentage change of the closed-loop gain. 4
5. (a) With a neat diagram derive the efficiency of a transformer coupled Class - A power amplifier when a square wave signal of peak amplitude  $V_m$  is given as the input. 5
- (b) For a Class - B amplifier providing a 22 V peak to an  $8\text{-}\Omega$  load and a power supply of  $V_{CC} = 25 \text{ V}$ , then determine input power, output power and circuit efficiency. 5

6. (a) Derive the expression for the bandwidth of N no. of identical amplifiers connected in cascaded when individual amplifier stages have bandwidth,  $BW = F_{CH} - F_{CL}$  and  $F_{CH}$ ,  $F_{CL}$  are the higher and lower 3-dB frequencies respectively. 5
- (b) Draw an emitter follower circuit using n-p-n transistor. Derive its voltage gain. 5
7. (a) Draw a three OPAMP based instrumentation amplifier circuits and derive its voltage gain in terms of circuit components. 5
- (b) Design a OPAMP circuits in non-inverting configuration which will give an output voltage,  $V_0 = 0.5V_1 - 2V_2 + 0.25V_3$ , where  $V_1$ ,  $V_2$  and  $V_3$  are three input voltages. 5
8. Write short notes on any **two** : 5×2
- (a) Stability of transistor biasing
- (b) Push-pull power amplifier
- (c) Current mirror circuit
- (d) Depletion type MOSFET.