

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
CPES 5202

Third Semester (Special) Examination – 2013

ANALOGUE ELECTRONICS CIRCUIT

BRANCH : AEIE, BIOMED, CSE, EC, EEE, EIE, ELECTRICAL, ETC, IEE, IT

QUESTION CODE : D 214

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any five from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2×10
- What is the typical value of gain-bandwidth product of an OPAMP ? What is its significance in analog circuits ?
 - What is the difference between cascade and cascade amplifier ? Mention their importance in electronics circuits.
 - The output waveform of an operational amplifier as seen in CRO is 4V peak to peak with 0.04 micro second rise time (t_r). What is its slew rate ?
 - What is Miller capacitance ? What is its impact on input and output stage of a transistor amplifier ?
 - What is Barkhausen Criterion of Oscillation ?
 - Calculate the second harmonic distortion when the peak to peak V_{CE} as seen from oscilloscope is 21 volts and V_{CEQ} is 12 volts.
 - What is the bandwidth of the amplifier when the rise time is 0.1 msec ? What should be the rise time of an ideal voltage amplifier ?
 - The input resistance of a OPAMP in non-inverting configuration is more than OPAMP inverting configuration ? Justify.

P.T.O.

- (i) Why low beta (β) is generally preferred in power amplifiers ?
- (j) Why emitter resistance (R_E) in the differential amplifier is generally taken high value ?
2. (a) In the Fig.1, if $R_{b1} = 470 \text{ K}\Omega$, $R_{b2} = 270 \text{ K}\Omega$, $R_c = 6.2 \text{ K}\Omega$, $R_e = 1.5 \text{ K}\Omega$, $C_b = C_c = 10 \mu\text{F}$, then find V_c , V_E , I_C , and V_{CE} when $\beta = 100$ and $V_{in} = 0\text{V}$ and $V_{CC} = 18 \text{V}$. 7

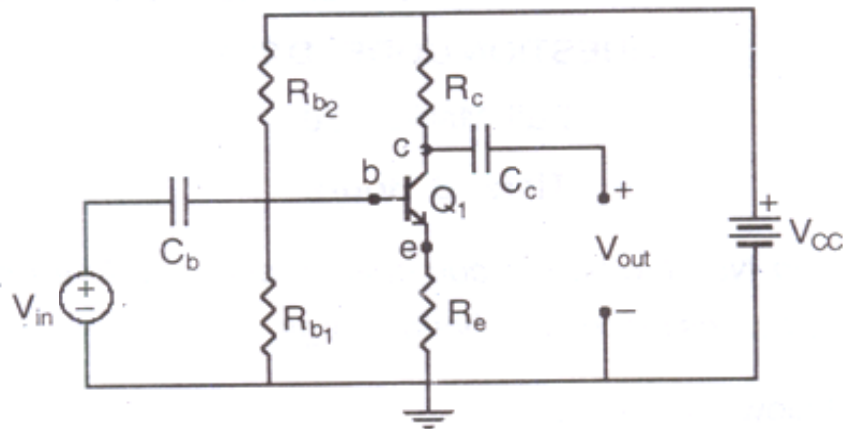


Fig. 1

- (b) What is the function of C_b and C_c in the above biasing circuit ? 3
3. (a) Explain the four h-parameter of a transistor. How these parameters are found from the characteristics of the transistor amplifier ? 7
- (b) Explain the importance of source resistance (R_S) and load resistance (R_L) in a transistor amplifier circuits. Justify with necessary mathematical expressions. 3
4. (a) Why +ve feedback is generally used in oscillator circuits ? 2
- (b) What are the primary requirements to obtain steady oscillation at a fixed frequency ? 3
- (c) Derive the input impedance (Z_i) and output impedance (Z_o) of a unit feedback voltage series -ve feedback amplifier in terms of its open-loop parameters. 5
5. (a) With a neat diagram derive the maximum efficiency of Class-B power amplifier when a sinusoidal wave signal of peak amplitude V_m is given as the input. 5

- (b) For a class-B amplifier with $V_{CC} = 20\text{ V}$ driving a $16\text{-}\Omega$ load and provides an output of 10 volt rms . Then, determine the input power, output power and circuit efficiency. 5
6. (a) A transistor has a value of $\alpha = 0.99$ in a CB amplifier. Its load resistance is $4.5\ \Omega$ and dynamic resistance at the emitter junction is $50\ \Omega$. Find its voltage gain and power gain. 5
- (b) Draw an emitter follower circuit using $n\text{-}p\text{-}n$ transistor. Derive its voltage gain using $\beta\text{-}r_e$ model. 5
7. (a) Establish a condition for applying maximum signal frequency to an OPAMP which has finite slew rate 'r' 5
- (b) Draw a non-inverting amplifier circuit of OPAMP whose open loop voltage gain is finite and its value A_d . Derive closed-loop voltage gain of the circuit. 5
8. Write short notes on any **two** of the following : 5×2
- (a) High frequency effects in a transistors
- (b) Nonlinear distortions in amplifier
- (c) Current mirror circuit
- (d) Depletion type MOSFET.

